

# **ECE 329 – Fall 2022**

**Prof. Ravaioli – Office: 2062 ECEB**

Lecture 29

# Lecture 29 – Outline


- **Transient on a transmission line**
- **Reflection coefficient**
- **Impulse response**
- **Bounce diagram**
- **Examples**

## **Reading assignment**

**Prof. Kudeki's ECE 329 Lecture Notes on Fields and Waves:  
29) Bounce Diagram examples**
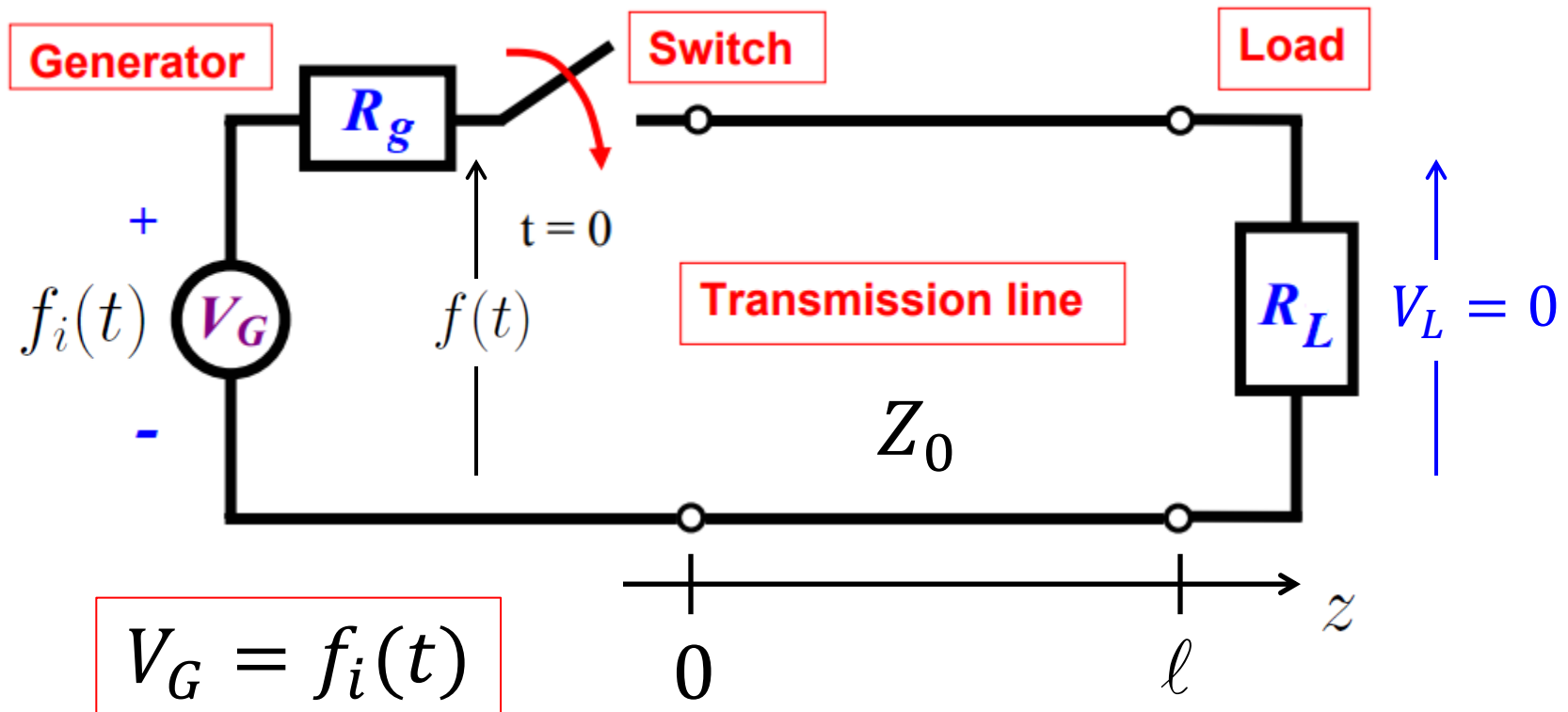
## Transient in a Transmission Line


We look for the voltage and current,  $V(z, t)$  and  $I(z, t)$  after the switch is closed and a certain input signal  $f_i(t)$  is injected



Remember: for a lossless line, the characteristic impedance  $Z_0$  is Real
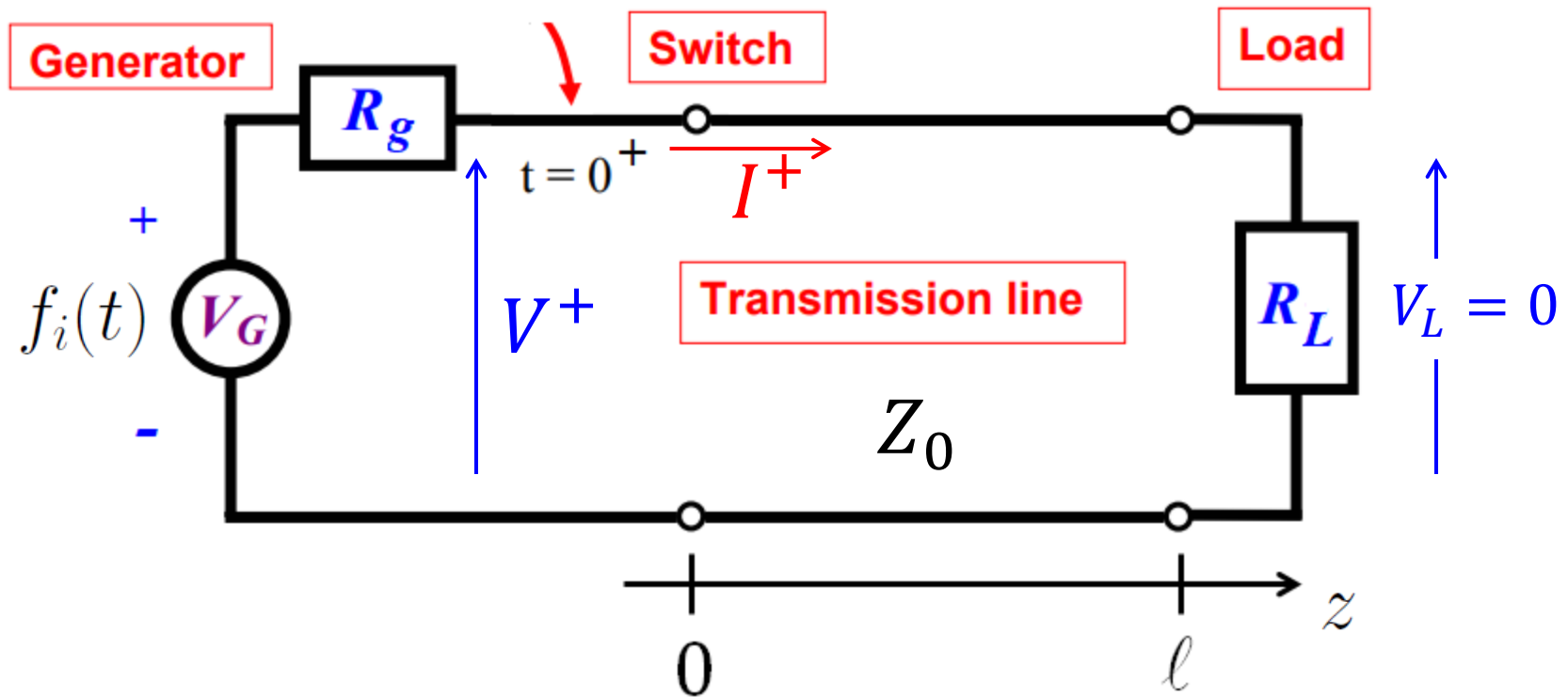
## Close the Switch


After the switch is closed, the voltage at the input of the TL varies to a value  $V^+$  and a current  $I^+$  begins to flow into the line.



The load voltage remains zero until the wavefront reaches the end of the line
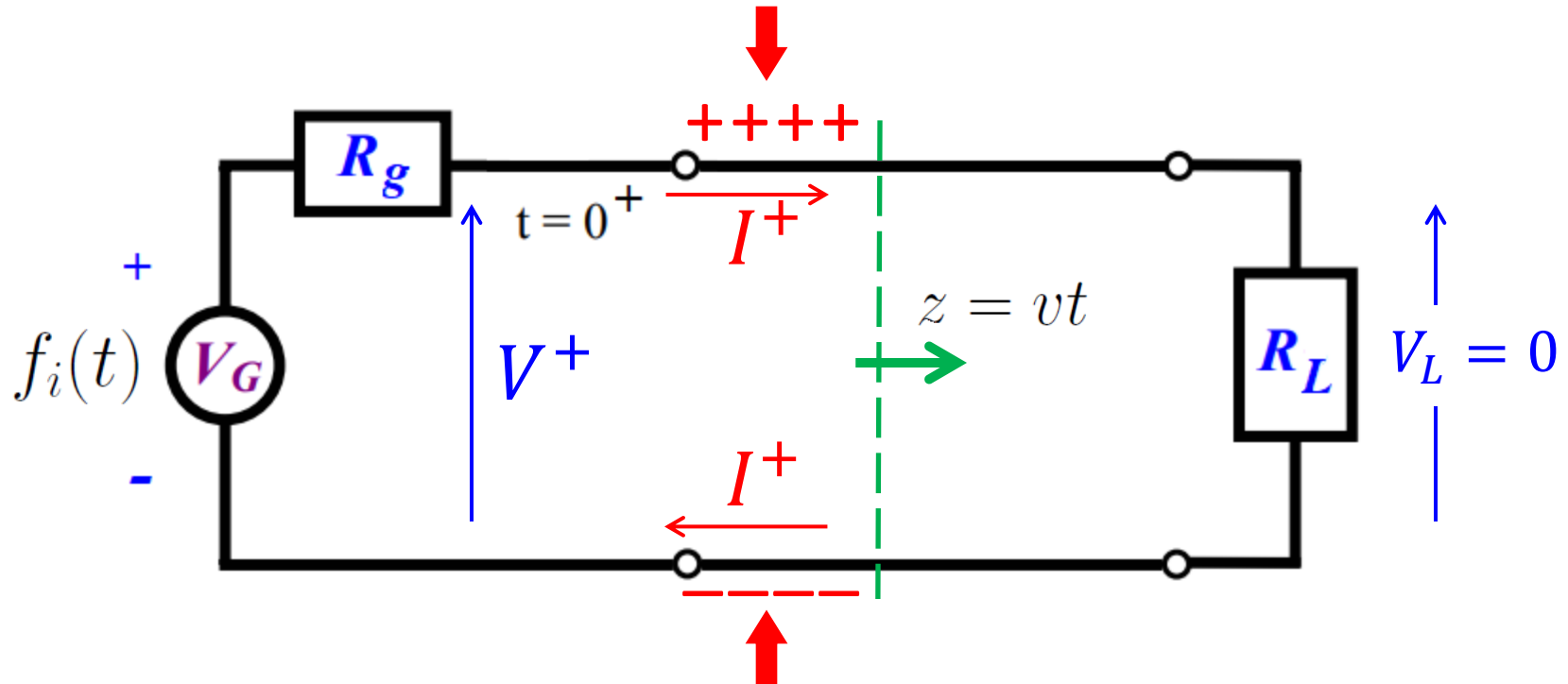
# Current Flow

After the switch is closed, positive charges start flowing into the top wire (that is, electrons are being pulled in by the generator).



Electrons are pushed into the bottom wire (as if positive charges are entering the generator), so that the same current flows.

## Propagation toward the load

Until the wavefront reaches the load, the **input impedance** of the transmission line appears to be the same as the **characteristic impedance**  $Z_0$  because the current cannot yet sense the load.

The voltage front  $V^+$  propagates with current  $I^+$  where

$$V^+ = Z_0 I^+ = V_G \frac{Z_0}{R_g + Z_0}$$

$$I^+ = \frac{V^+}{Z_0} = \frac{f_i(0)}{R_g + Z_0}$$

The wave fronts travel with a phase velocity equal to the speed of light for the dielectric medium surrounding the wires.

## The wavefront has reached the load

If the load does not match exactly the characteristic impedance of the line, the voltage  $V^+$  and the current  $I^+$  are not compatible with the load  $R_L$  because

$$V^+ \neq R_L I^+$$

Voltage and current adjust themselves to the load by reflecting back a wavefront with voltage  $V^-$  and current  $I^-$  such that

$$V^+ + V^- = (I^+ + I^-)R_L$$


Since also the reflected front encounters an impedance  $Z_0$ , we have

$$V^+ = Z_0 I^+$$

$$V^- = -Z_0 I^-$$

$$V^+ + V^- = (I^+ + I^-)R_L$$
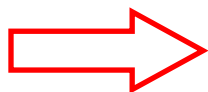
$$V^+ + V^- = \left( \frac{V^+}{Z_0} - \frac{V^-}{Z_0} \right) R_L$$



$$V^- = V^+ \frac{R_L - Z_0}{R_L + Z_0}$$

Solve for the unknown  $V^-$

where we have the **Load Reflection Coefficient**  $\Gamma_L$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$




# Load Reflection Coefficient $\Gamma$ – Analogy with EM waves

Transmission Line

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$

EM wave at an interface
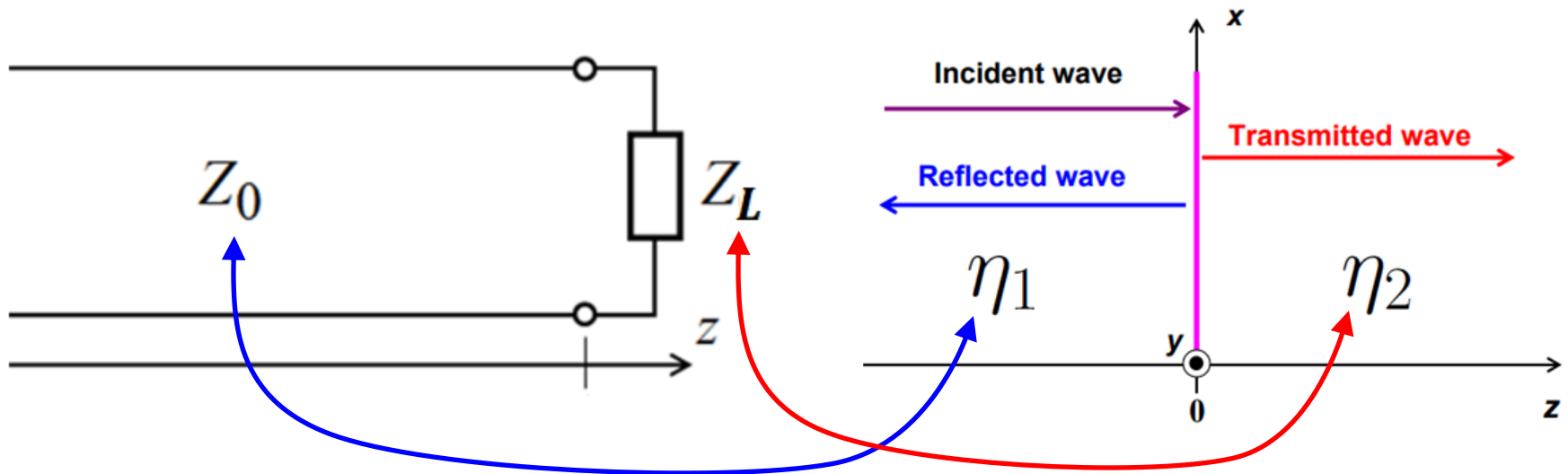
$$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1}$$



## Reflected wavefront

The wave reflected by the **load** propagates in the negative direction and **interferes** with voltage and current found along the transmission line, which continue to be injected by the generator.

When the reflected wave reaches the input of the transmission line, it terminates on the generator impedance  $R_g$ .

If  $R_g$  does not match the line characteristic impedance  $Z_0$ , reflection back into the line occurs, generating an additional **forward wave**

$$V_2^+ = V^- \frac{R_G - Z_0}{R_G + Z_0}$$

and the cycle repeats, while the generator may continue to inject a forward wave...

Remember, the ideal voltage source part of the generator behaves simply as a short for the reflected wave attempting to exit the line from the input.

# Special case: Load Matched to the Transmission Line

Assume that the load is **matched** to the TL:  $R_L = Z_0$

At the load

$$z = \ell$$

$$\frac{V(\ell, t)}{I(\ell, t)} = \frac{V_L}{I_L} = R_L = Z_0$$

$$V(\ell, t) = f\left(t - \frac{\ell}{v}\right) + g\left(t + \frac{\ell}{v}\right)$$

$$I(\ell, t) = \frac{f\left(t - \frac{\ell}{v}\right) - g\left(t + \frac{\ell}{v}\right)}{Z_0}$$

$$\frac{V(\ell, t)}{I(\ell, t)} = Z_0 \quad \text{only if} \quad g\left(t + \frac{\ell}{v}\right) = 0 \quad \text{No Reflection}$$

$$V(z, t) = f\left(t - \frac{z}{v}\right)$$

$$I(z, t) = \frac{1}{Z_0} f\left(t - \frac{z}{v}\right)$$

## Transient in a Transmission Line


At the input

$$z = 0$$

$$V(0, t) = f(t)$$

$$I(0, t) = \frac{1}{Z_o} f(t)$$

$$Z_o = \frac{V(0, t)}{I(0, t)}$$

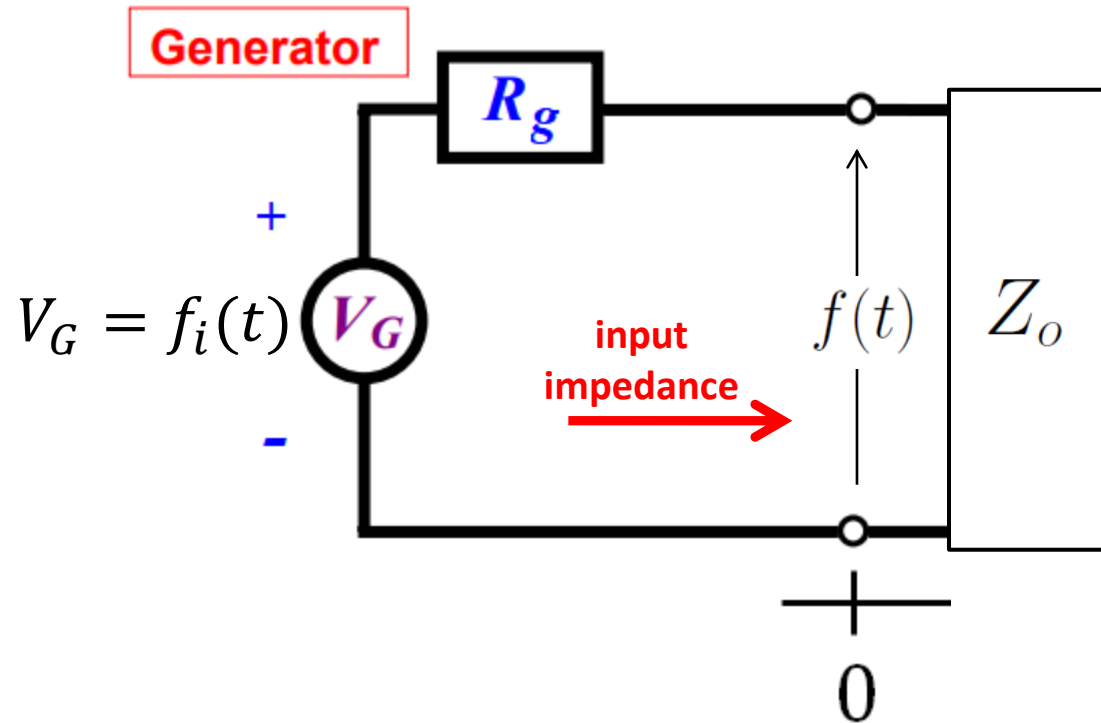

Voltage Divider

$$f(t) = \frac{Z_o}{R_g + Z_o} f_i(t)$$

injection coefficient  $\tau_g$

$$f(t) = \tau_g f_i(t)$$

## Transient in a Transmission Line

Therefore, the distribution of voltage and current along a transmission line circuit **terminated by a matched load** is

$$V(z, t) = \tau_g f_i\left(t - \frac{z}{v}\right)$$

$$I(z, t) = \frac{\tau_g}{Z_o} f_i\left(t - \frac{z}{v}\right)$$

**There are no interference patterns caused by load reflections, because there is only one forward wave propagating.**

## Impulse response for the matched case

A delta function input

$$f_i(t) = \delta(t)$$

generates the **impulse response**

$$V(z, t) = \tau_g \delta\left(t - \frac{z}{v}\right) \equiv h_z(t)$$

(From ECE 210) Convolution of a system's impulse response with any input function provides the system's response to that function

$$Y(t) = \int_{-\infty}^{+\infty} X(t)h(t - \tau) d\tau$$

## Arbitrary Load $R_L$

The impulse response needs to be obtained again when the load is changed, with the new constraint

$$\frac{V(\ell, t)}{I(\ell, t)} = \frac{V_L}{I_L} = R_L$$

from which a new reflection coefficient is obtained each time

$$\Gamma_L = \frac{R_L - Z_o}{R_L + Z_o}$$

In principle, one can construct the impulse response by adding the forward and reflected pulses, going back and forth in a series.

## Arbitrary Load $R_L$

For the first roundtrip  $0 < t < \frac{2\ell}{v}$   
the load voltage and current expressions are

$$\begin{aligned} V(\ell, t) &= \tau_g \left[ \delta\left(t - \frac{\ell}{v}\right) + \Gamma_L \delta\left(t + \frac{\ell}{v} - \frac{2\ell}{v}\right) \right] \\ &= \tau_g \delta\left(t - \frac{\ell}{v}\right) [1 + \Gamma_L] \end{aligned}$$


Written as for generic  $z$  for convenience

$$\begin{aligned} I(\ell, t) &= \frac{\tau_g}{Z_o} \left[ \delta\left(t - \frac{\ell}{v}\right) - \Gamma_L \delta\left(t + \frac{\ell}{v} - \frac{2\ell}{v}\right) \right] \\ &= \frac{\tau_g}{Z_o} \delta\left(t - \frac{\ell}{v}\right) [1 - \Gamma_L] \end{aligned}$$



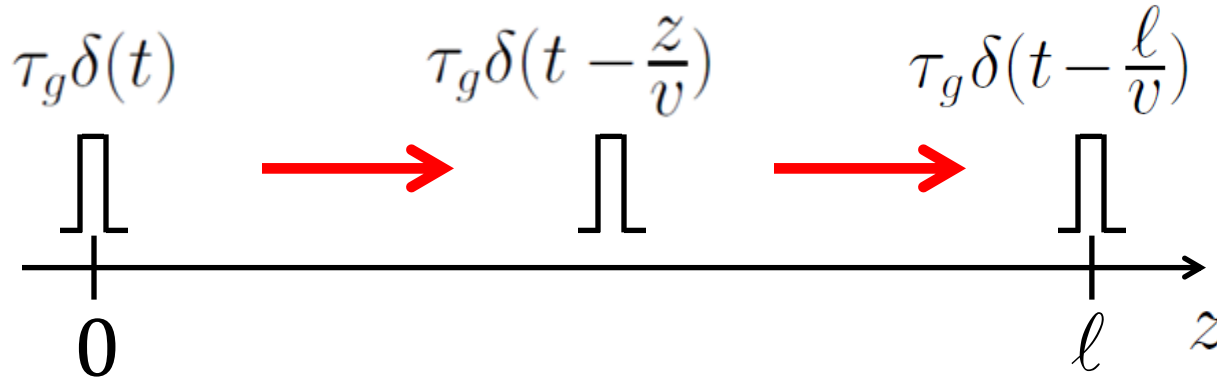
## Bookkeeping of pulses


The first pulse starts at  $t = 0$  from the input and it arrives to the load after a time  $\ell/v$



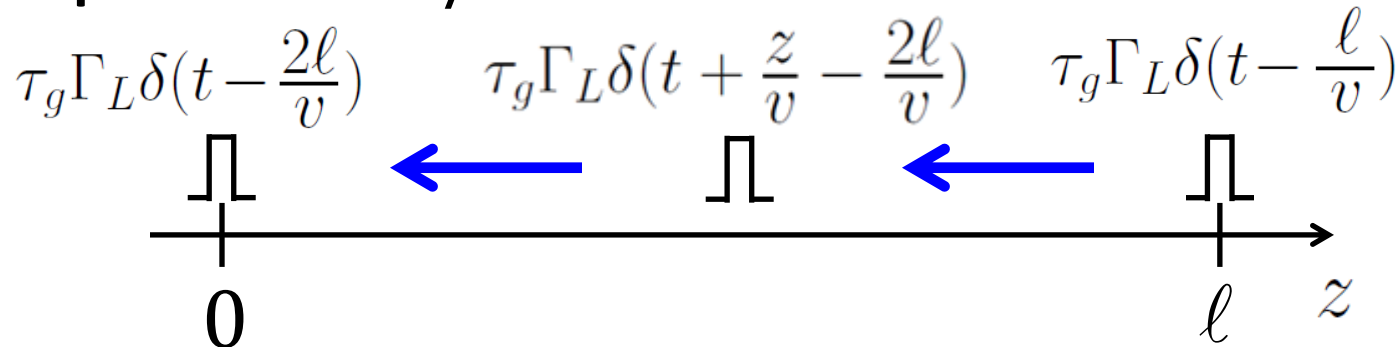The first reflected pulse starts at  $t = \ell/v$  from the load and returns to the input at time  $2\ell/v$



and then

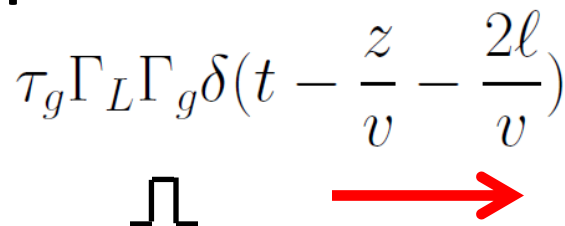

and so on...

## Bookkeeping of pulses

The complete process can be written formally with summations. In many practical cases the series converges rapidly.

$$V(z, t) = \tau_g \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t - \frac{z}{v} - n \frac{2\ell}{v}\right) \\ + \tau_g \Gamma_L \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t + \frac{z}{v} - (n+1) \frac{2\ell}{v}\right)$$

$$I(z, t) = \frac{\tau_g}{Z_o} \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t - \frac{z}{v} - n \frac{2\ell}{v}\right) \\ - \frac{\tau_g}{Z_o} \Gamma_L \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t + \frac{z}{v} - (n+1) \frac{2\ell}{v}\right)$$

## Bookkeeping of pulses

For  $n = 0$  we have the first forward wave

$$\tau_g \delta\left(t - \frac{z}{v}\right)$$

reflected by generator

$$V(z, t) = \tau_g \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t - \frac{z}{v} - n \frac{2\ell}{v}\right)$$

reflected by load


$$+ \tau_g \Gamma_L \sum_{n=0}^{\infty} (\Gamma_L \Gamma_g)^n \delta\left(t + \frac{z}{v} - (n + 1) \frac{2\ell}{v}\right)$$

For  $n = 0$  we have the first reflected wave

$$\tau_g \Gamma_L \delta\left(t + \frac{z}{v} - \frac{2\ell}{v}\right)$$
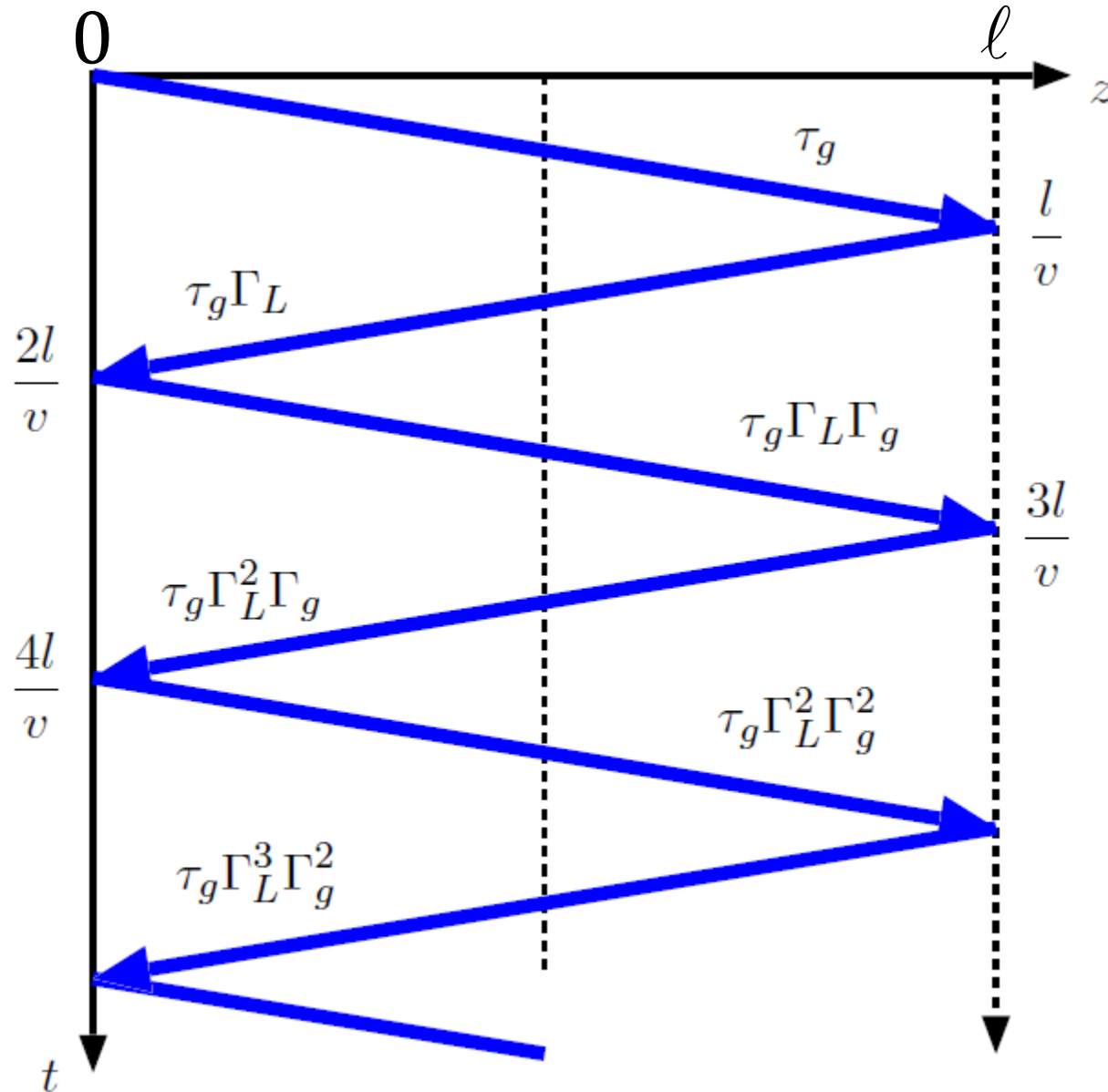
# Bounce diagram

Analysis is often done in graphical form. Each bounce adds a  $\Gamma$ .



# Example 1

## Transmission Line

Length = 900 m

phase velocity  $v = c$


Load  $R_L = 2Z_0$

## Generator

$$f_i(t) = \sin(\omega t)u(t)$$

$$R_g = Z_0$$

Frequency = 1 MHz

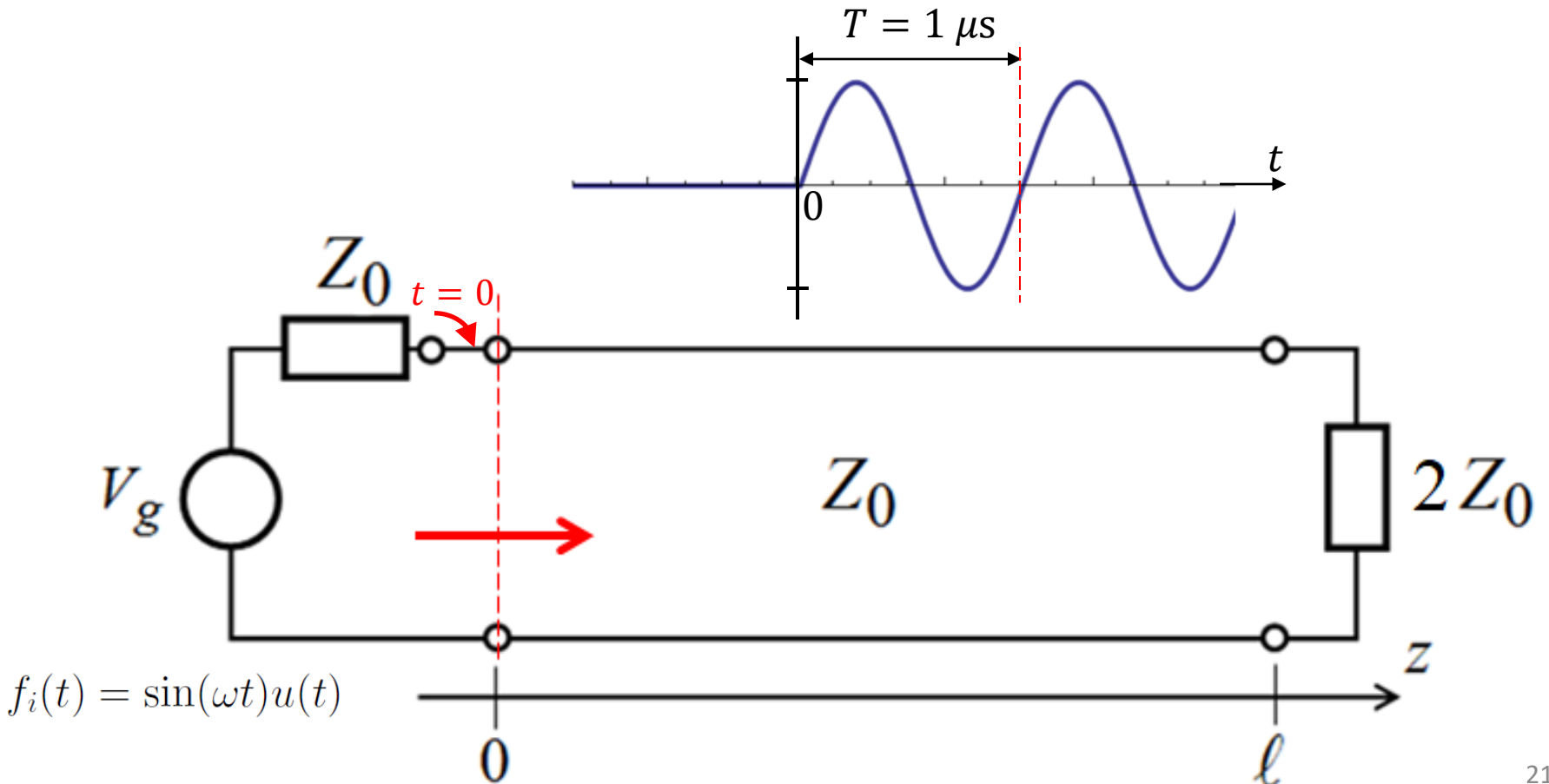

## Example 1

### Transmission Line

Length = 900 m

phase velocity  $v = c$

Load  $R_L = 2Z_0$

### Generator

$$f_i(t) = \sin(\omega t)u(t)$$

$$R_g = Z_0$$

Frequency = 1 MHz

Injection coefficient

$$\tau_g = \frac{Z_0}{R_g + Z_0} = \frac{Z_0}{Z_0 + Z_0} = \frac{1}{2}$$

Reflection coefficients

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{2Z_0 - Z_0}{2Z_0 + Z_0} = \frac{2 - 1}{2 + 1} = \frac{1}{3}$$

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

time-delay (roundtrip)


$$\frac{2\ell}{v} = \frac{2 \cdot 900 \text{ m}}{300 \text{ m}/\mu\text{s}} = 6 \mu\text{s}$$

## Example 1

$$\tau_g = \frac{1}{2}$$

$$\Gamma_L = \frac{1}{3}$$

$$\Gamma_g = 0$$

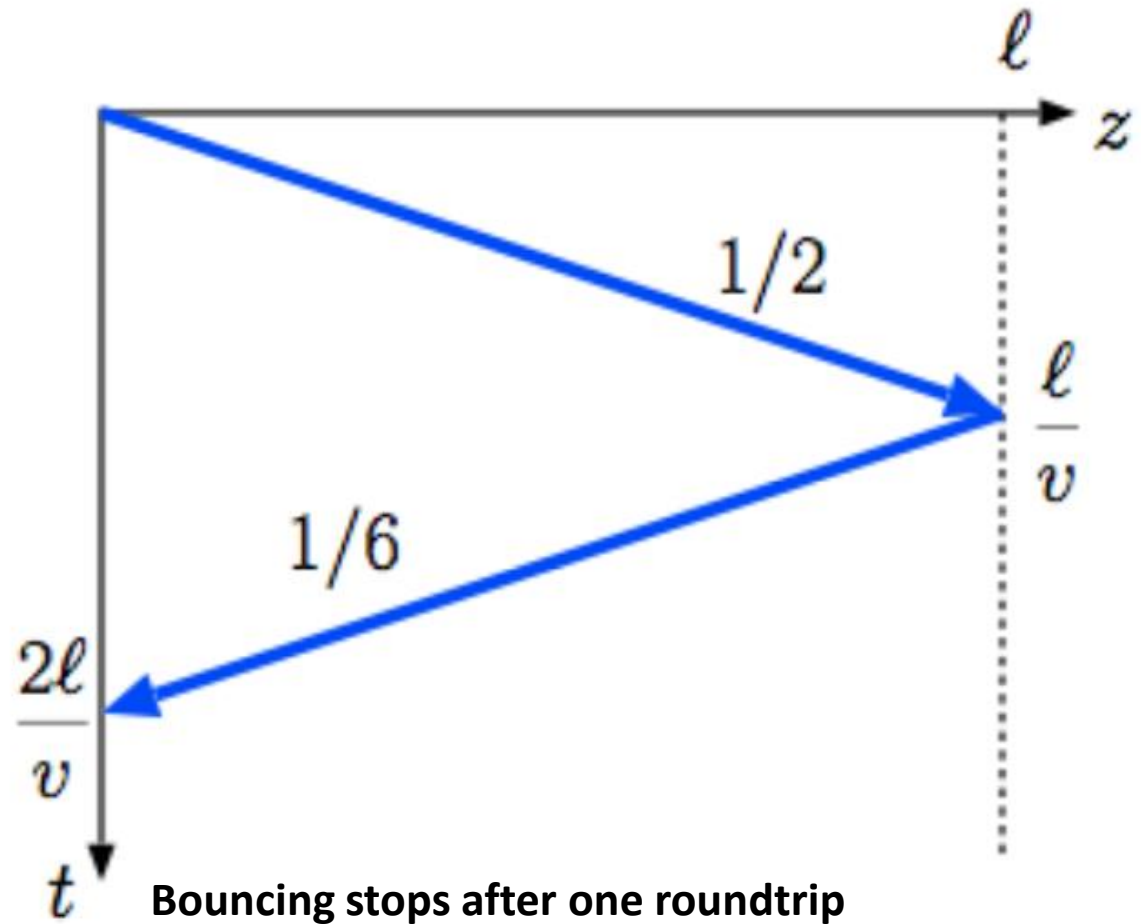

impulse response

$$h_z(t) = \frac{1}{2}\delta\left(t - \frac{z}{c}\right) + \frac{1}{6}\delta\left(t + \frac{z}{v} - 6\mu\right)$$

## Example 1

input signal



$$f_i(t) = \sin(\omega t)u(t)$$

impulse response

$$h_z(t) = \frac{1}{2}\delta(t - \frac{z}{v}) + \frac{1}{6}\delta(t + \frac{z}{v} - 6\mu)$$

voltage wave from convolution
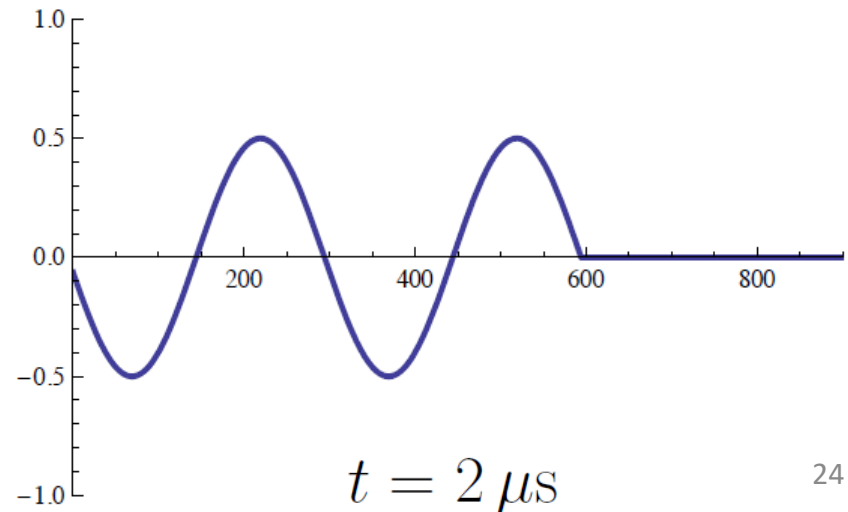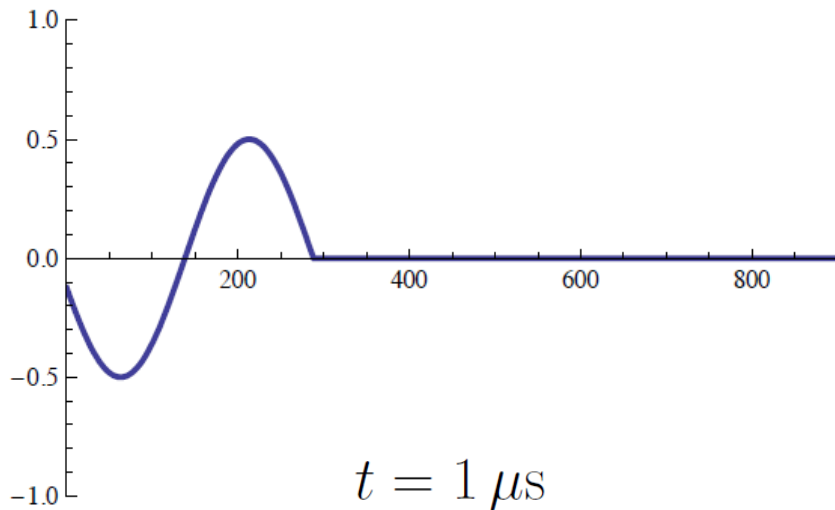
$$\begin{aligned} V(z, t) &= h_z(t) * \sin(\omega t)u(t) \\ &= \frac{1}{2} \sin \omega(t - \frac{z}{v})u(t - \frac{z}{v}) + \frac{1}{6} \sin \omega(t + \frac{z}{v} - 6)u(t + \frac{z}{v} - 6) \end{aligned}$$





## Example 2

### Transmission Line

Length = 2400 m

phase velocity  $v = c$

Load  $R_L = 100 \Omega$


$Z_0 = 50 \Omega$

### Generator

$f_i(t) = u(t)$  (unit step function)

$R_g = 0$

Determine and plot  $V(1200, t)$

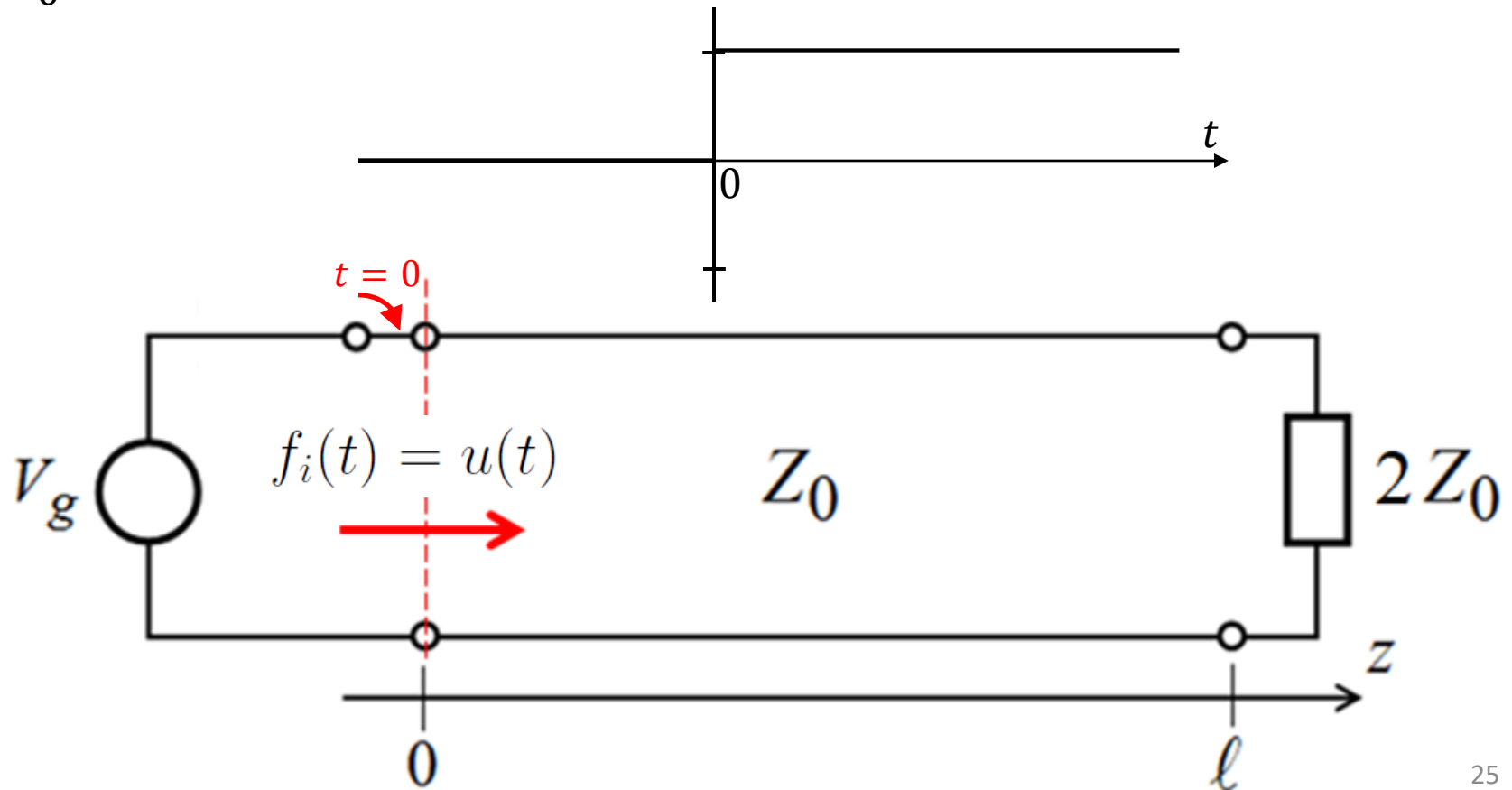

## Example 2

### Transmission Line

Length = 2400 m

phase velocity  $v = c$

Load  $R_L = 100 \Omega$

### Generator

$f_i(t) = u(t)$  (unit step function)

$R_g = 0$

Determine and plot  $V(1200, t)$

Injection coefficient

$$\tau_g = \frac{Z_o}{R_g + Z_o} = 1 \quad (\text{ideal source})$$

Reflection coefficients


$$\Gamma_g = \frac{R_g - Z_o}{R_g + Z_o} = -1 \quad (\text{like a short circuit})$$

$$\Gamma_L = \frac{R_L - Z_o}{R_L + Z_o} = \frac{1}{3}$$

time-delay (one way)

$$\frac{\ell}{v} = \frac{2400 \text{ m}}{300 \times 10^6 \text{ m/s}} = 8 \mu\text{s}$$

## Example 2

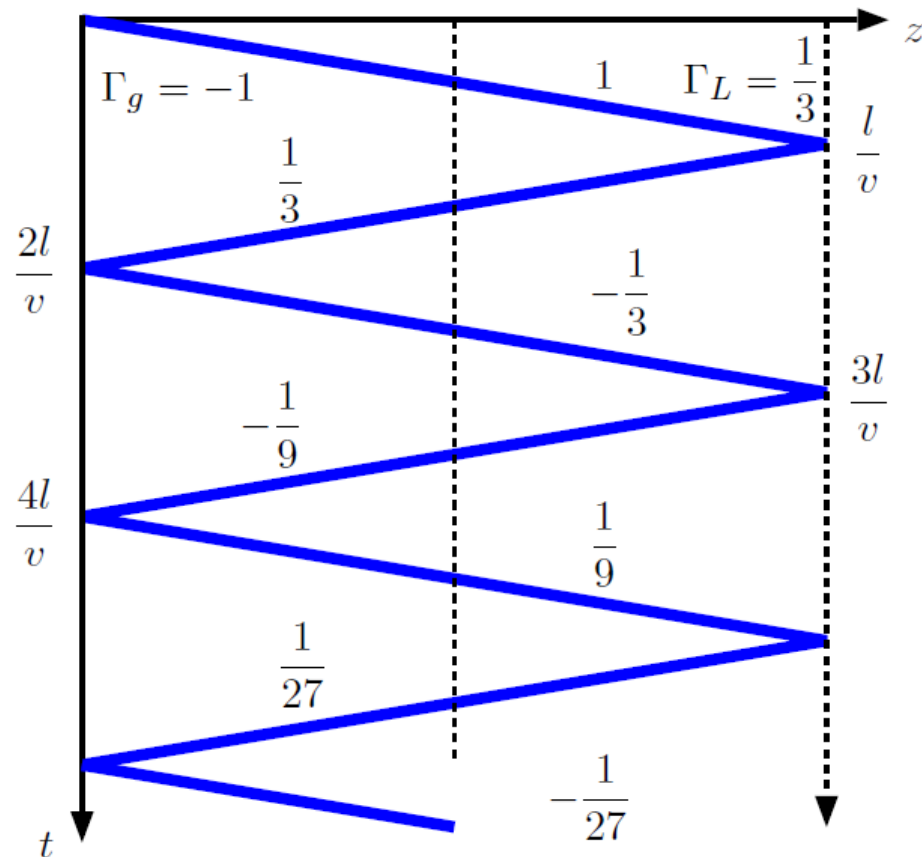


### Impulse response

$$V(1200, t) = \delta(t - 4) + \frac{1}{3}\delta(t - 12) - \frac{1}{3}\delta(t - 20) - \frac{1}{9}\delta(t - 28) + \frac{1}{9}\delta(t - 36) + \dots$$
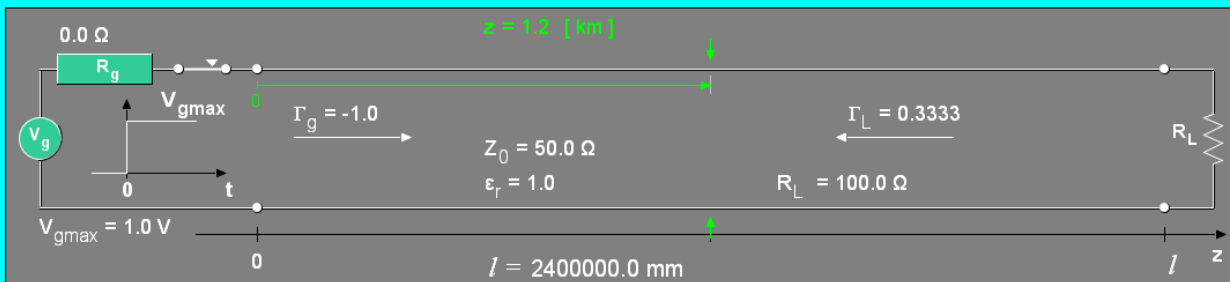
### Unit-step response

$$V(1200, t) = u(t - 4) + \frac{1}{3}u(t - 12) - \frac{1}{3}u(t - 20) - \frac{1}{9}u(t - 28) + \frac{1}{9}u(t - 36) + \dots$$



Set Line Parameters


$Z_0 =$   [ $\Omega$ ]  
 $\epsilon_r =$    
 $l =$   [mm]

Transient Plots

Step

Pulse

Voltage  $V(t)$

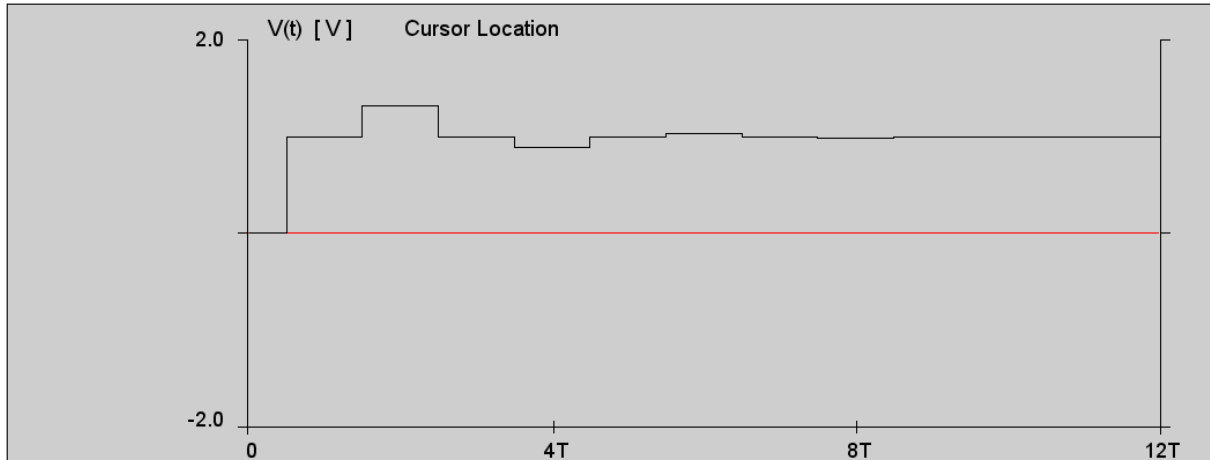

Data

Step Input

**Cursor**  $z = 1.2$  [km]

**Transit Time: input to load**  
 $T = 8.0$  [ $\mu\text{s}$ ]



**Transit Time: input to cursor position**  
 $T_C = 4.0$  [ $\mu\text{s}$ ]

**Transit Time: input to load and back to cursor**  
 $T_{LC} = 12.0$  [ $\mu\text{s}$ ]

**Phase velocity**  $u_p = 3.0$  [ $10^8$  m/s]

Reflection coefficients

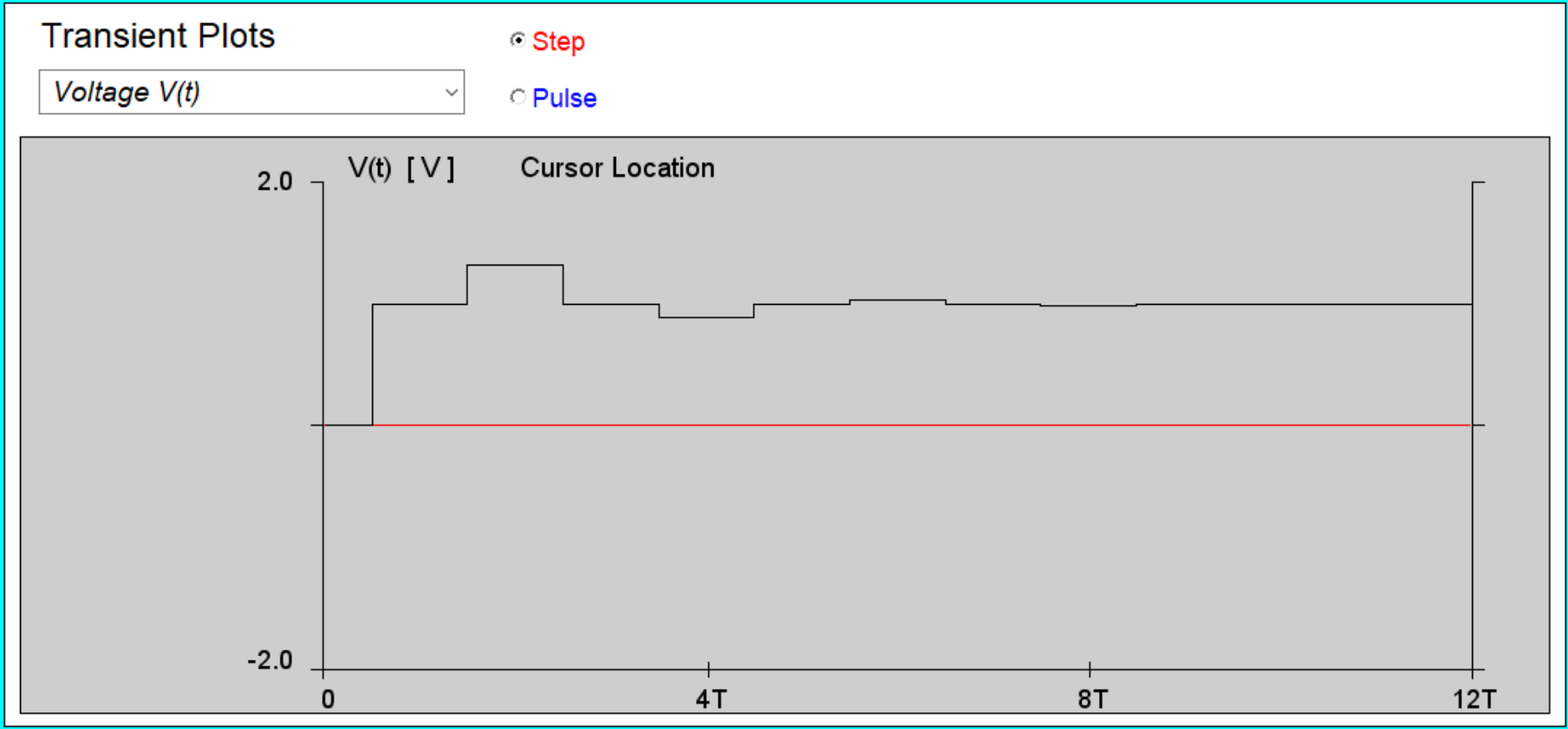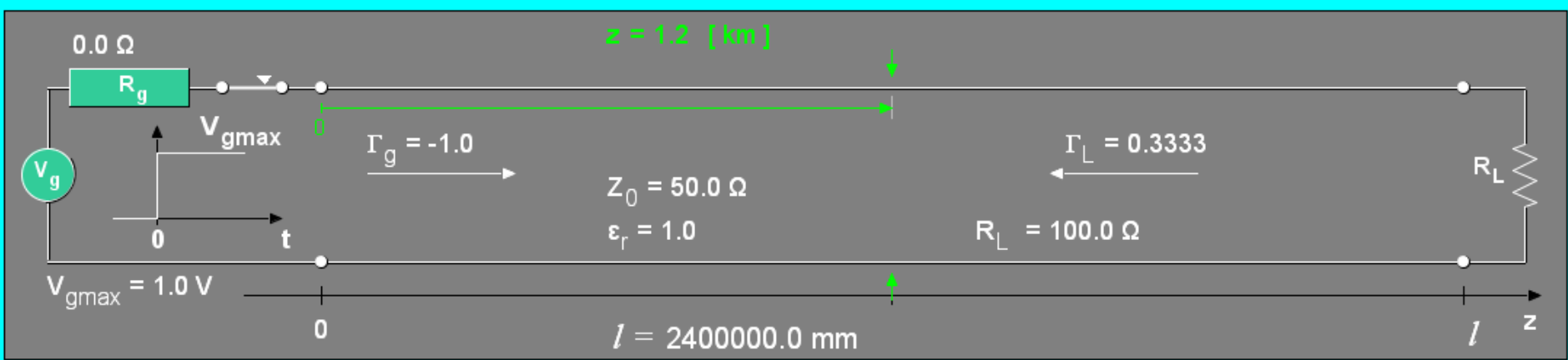$\Gamma_g = -1.0$        $\Gamma_L = 0.3333$




# Transient Animation Snapshot

Transient Response

Step

Pulse


Transient Voltage

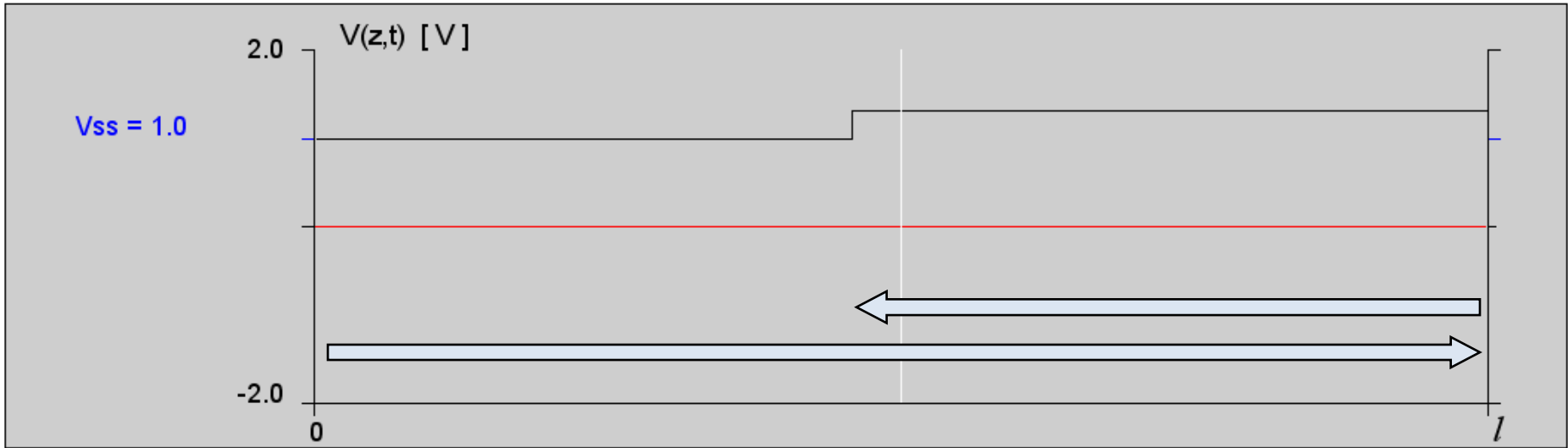

START

STOP

RESET

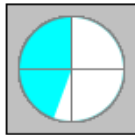


<< SLOW

FAST >>

1.54 T

12.33  $\mu$ s

## Example 3

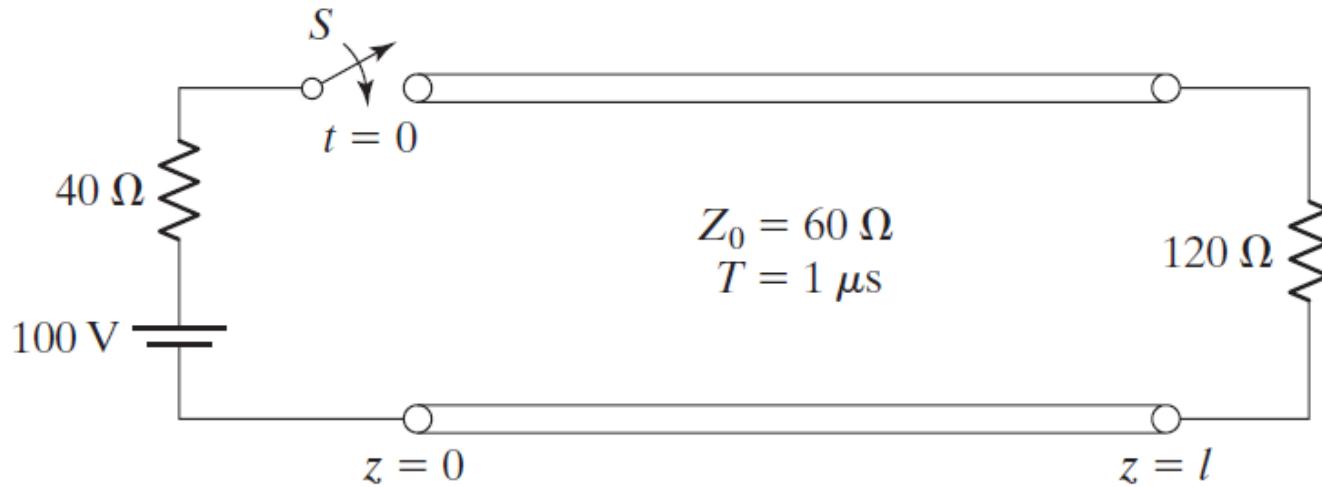

Current

Injection coefficient

$$\tau_g = \frac{Z_0}{R_g + Z_0} = 0.6$$

$$I(t = 0) = 1A$$

Reflection coefficients

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = -\frac{1}{5}$$

$$\Gamma_{gc} = \frac{1}{5}$$



$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{1}{3}$$

$$\Gamma_{Lc} = -\frac{1}{3}$$

time-delay (one way)



$$\frac{\ell}{v} = 1 \mu s$$

### Example 3

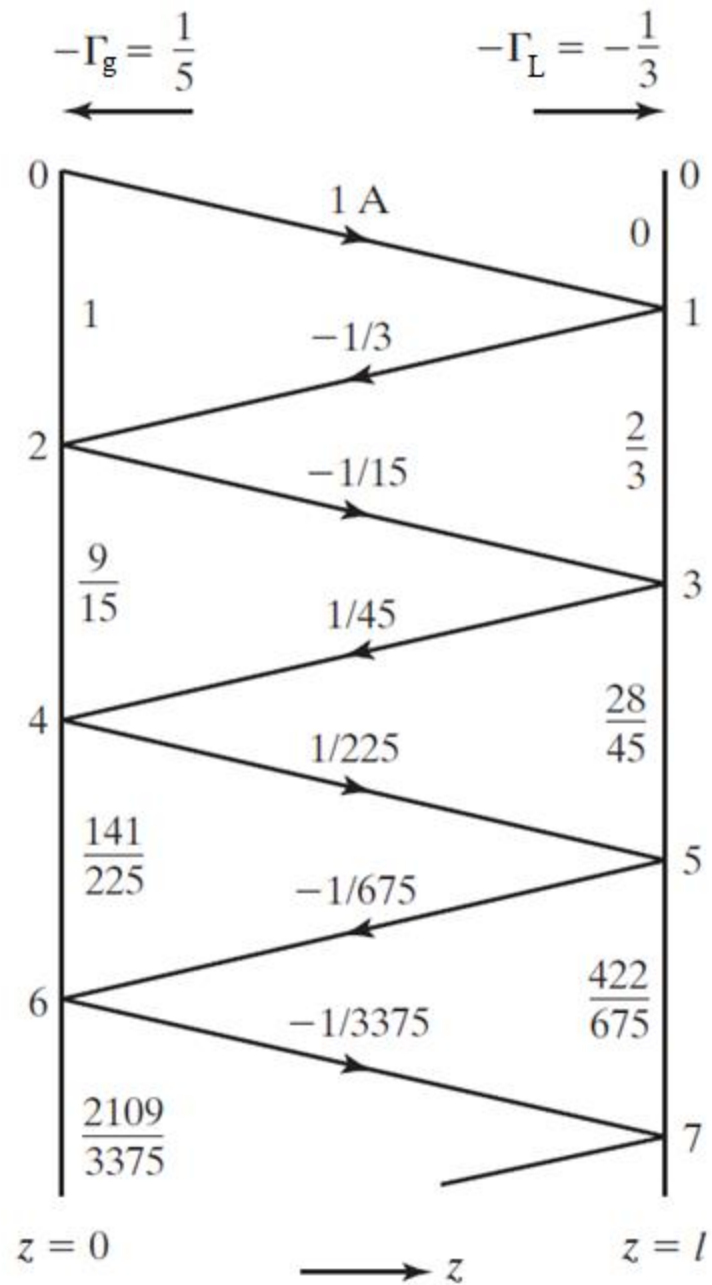
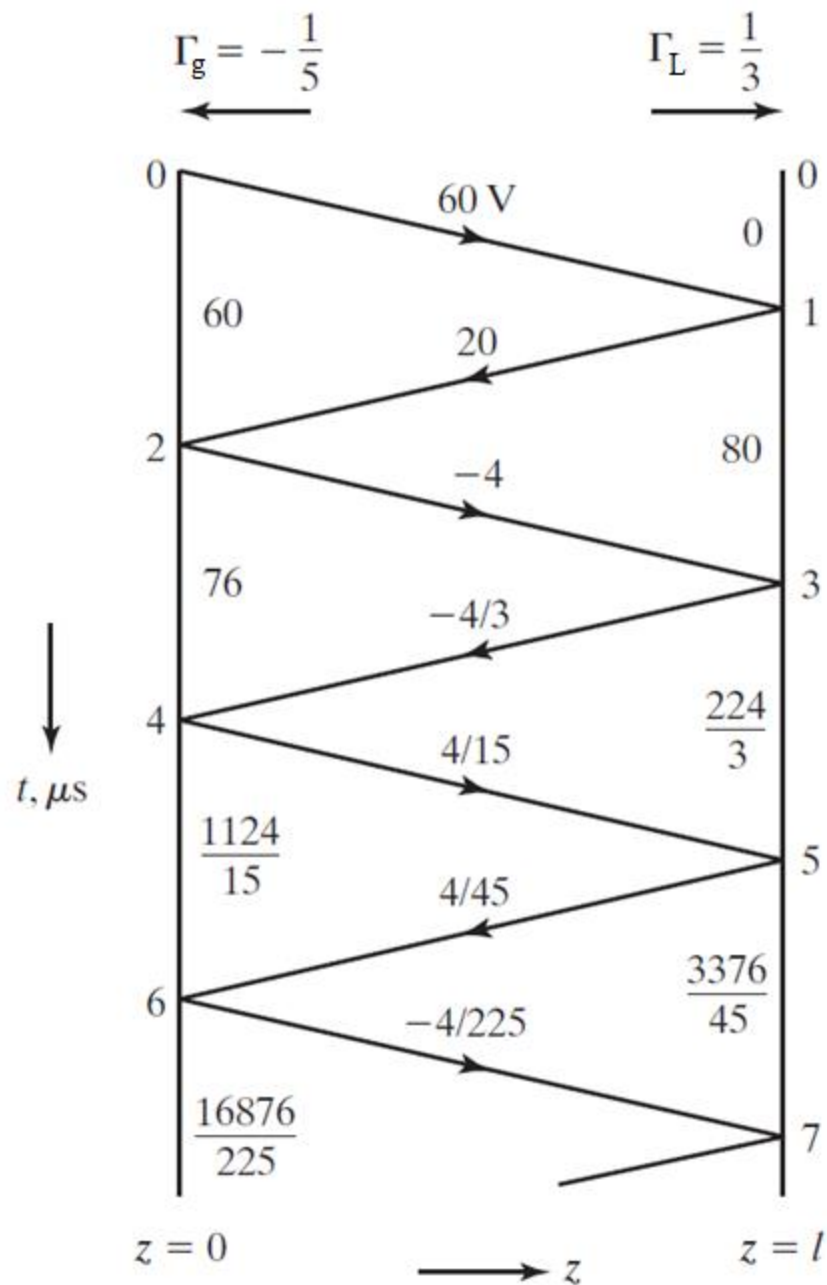






### Example 3

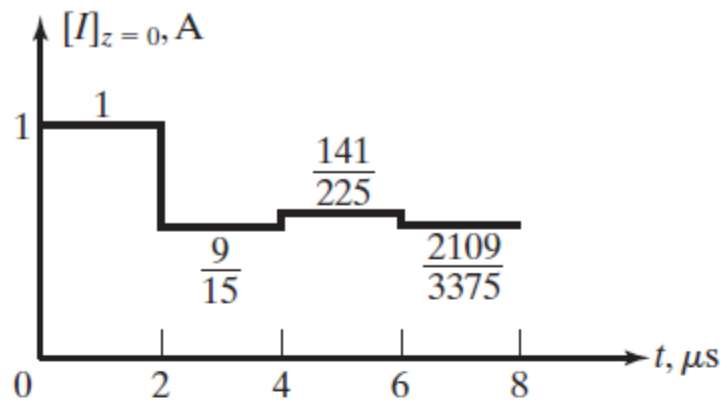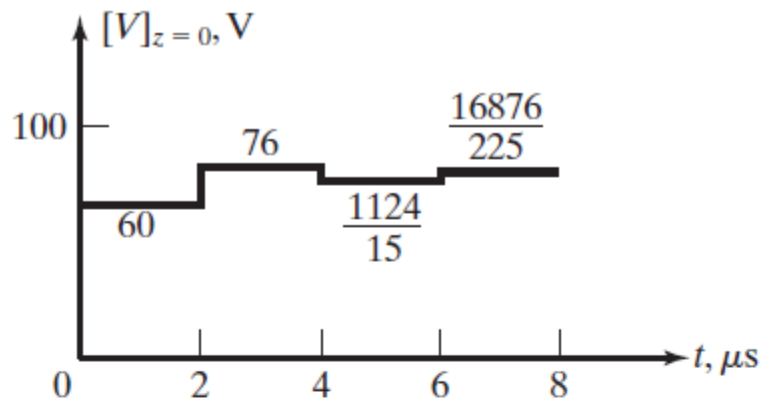

$$z = 0$$

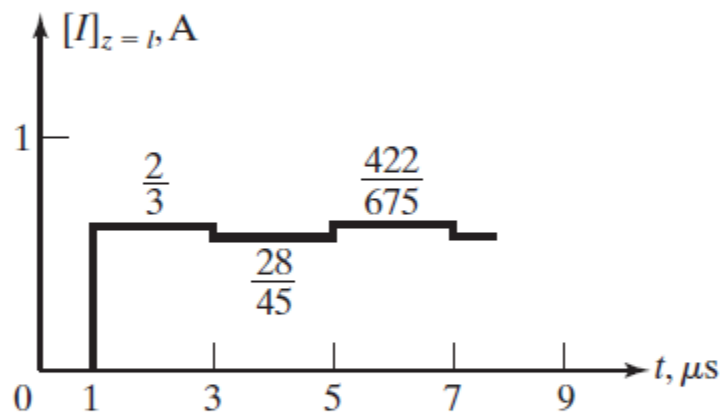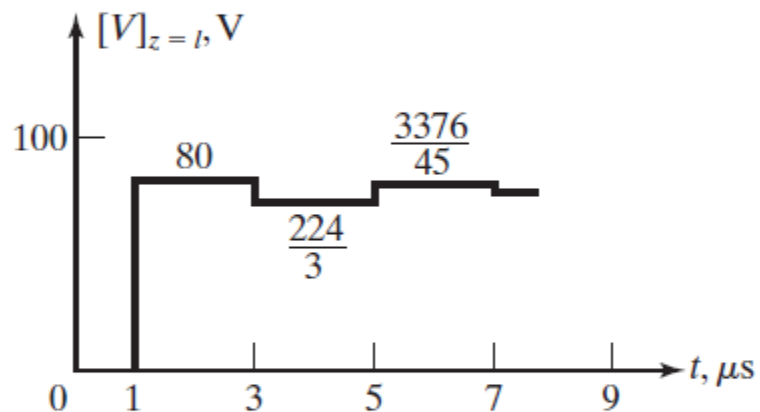



$$z = l$$

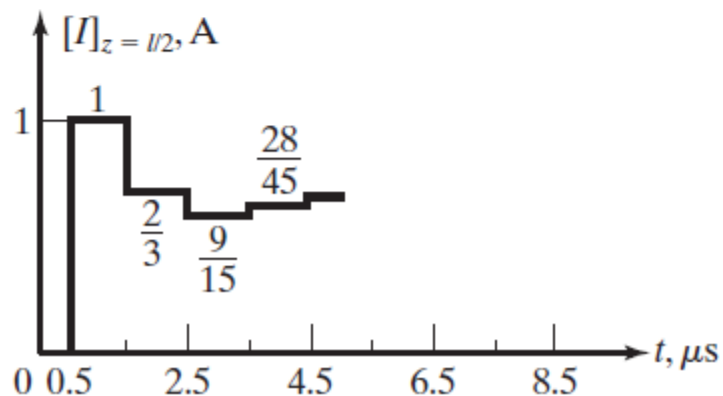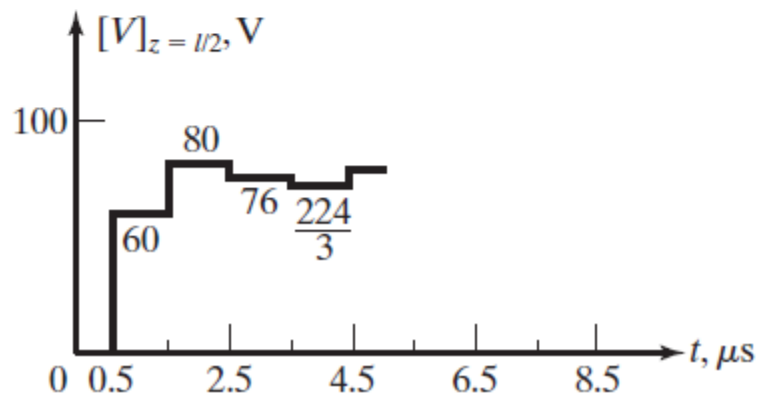

$$z = \frac{l}{2}$$

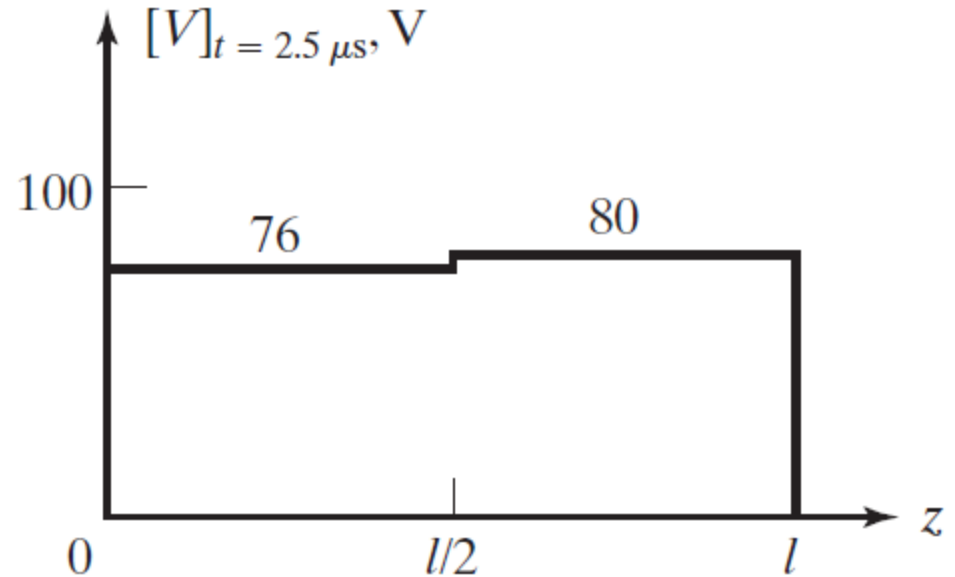
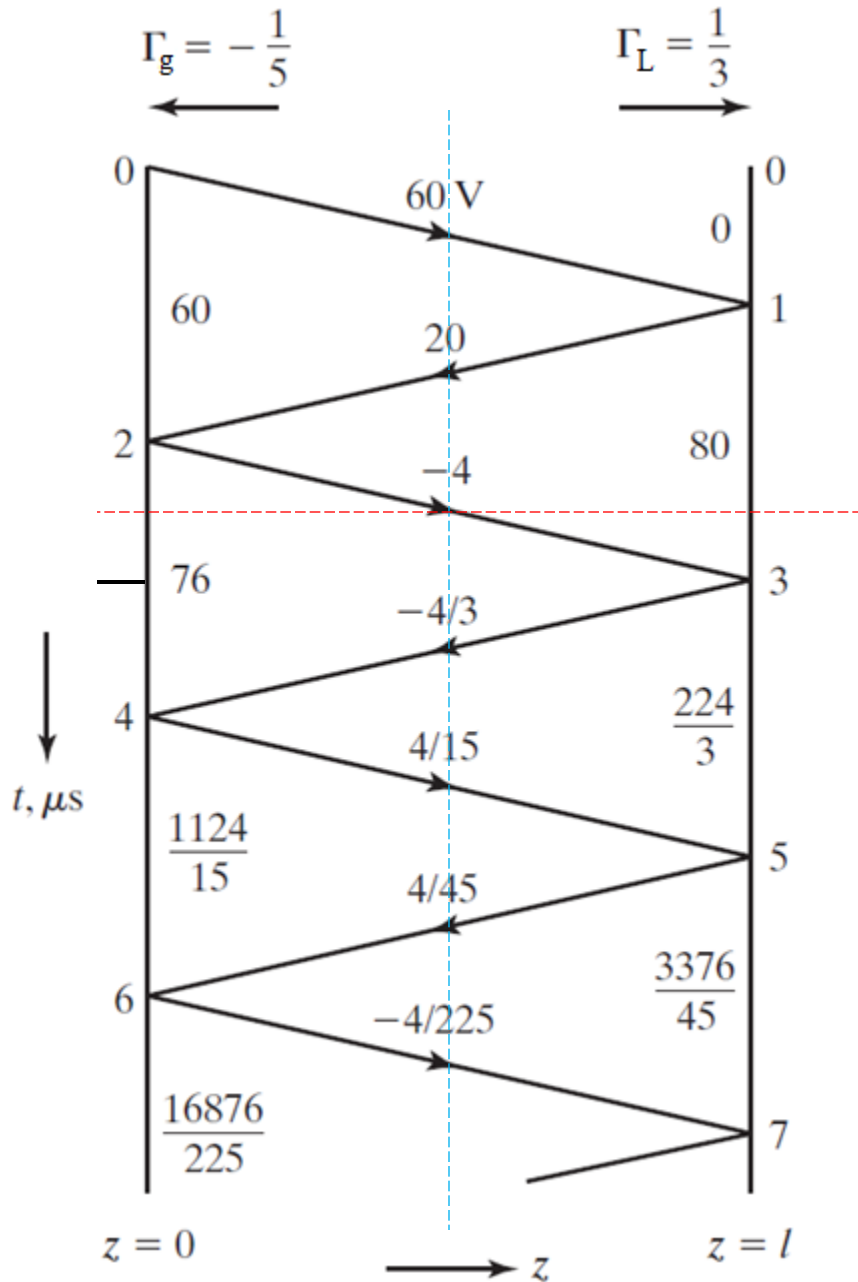
### Example 3

Find the voltage as a function of  $z$  at  $t = 2.5 \mu s$


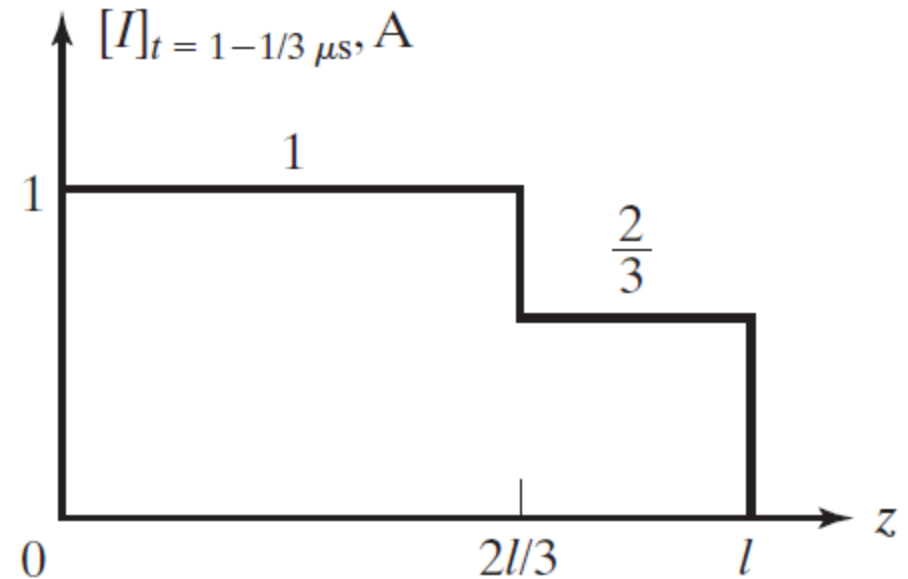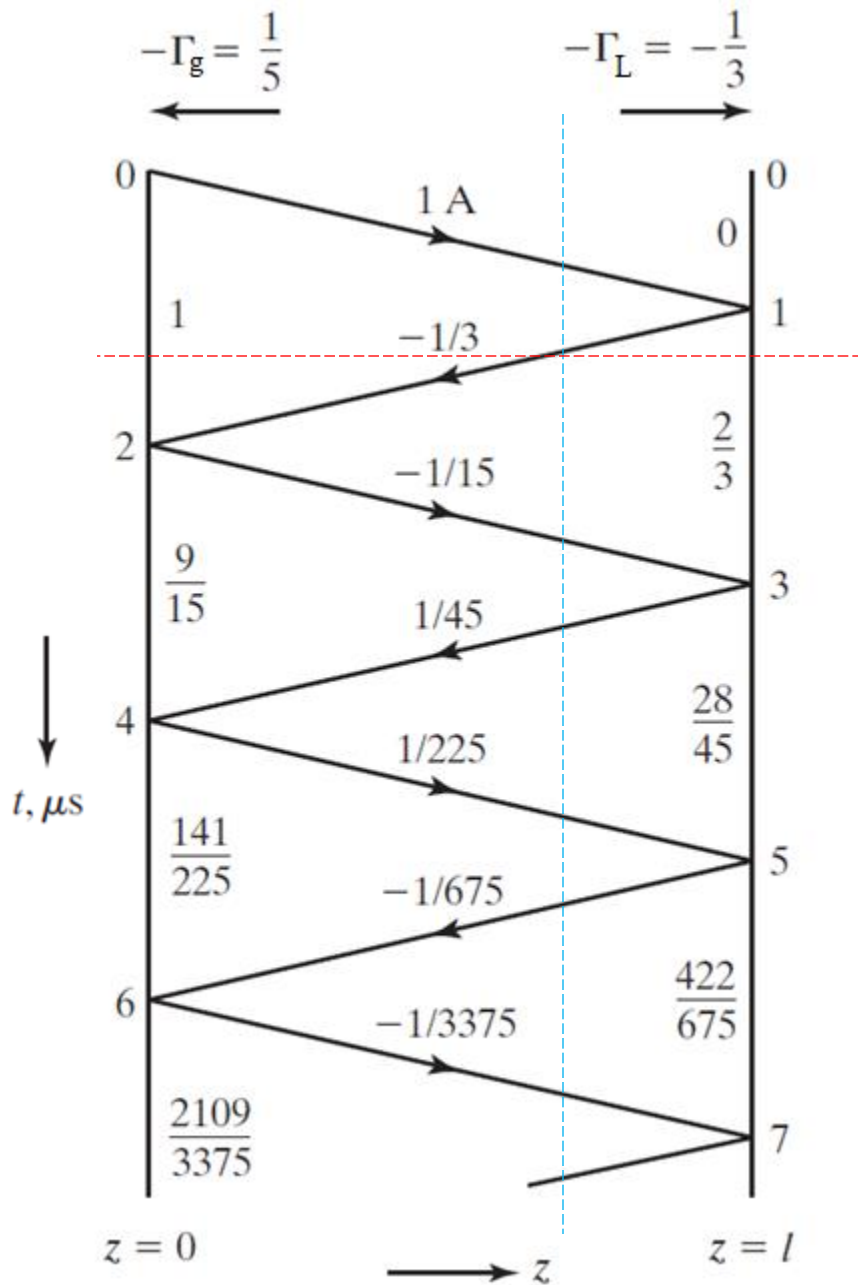
### Example 3

Find the current as a function of  $z$  at  $t = 1.\bar{3} \mu s$



### Example 3

#### Steady State Analysis

$$\sum_{n=0}^{\infty} (-1)^n \left(\frac{1}{15}\right)^n = \frac{1}{1 + 1/15} = 0.9375$$

geometric series

#### Forward Path

$$V_{SS}^+ = 60 - 4 + \frac{4}{15} - \dots = 60 \left( 1 - \frac{1}{15} + \frac{1}{15^2} - \dots \right) = 56.25 \text{ V}$$

$$I_{SS}^+ = 1 - \frac{1}{15} + \frac{1}{225} - \dots = 1 - \frac{1}{15} + \frac{1}{15^2} - \dots = 0.9375 \text{ A}$$

#### Backward Path

$$V_{SS}^- = 20 - \frac{4}{3} + \frac{4}{45} - \dots = 20 \left( 1 - \frac{1}{15} + \frac{1}{15^2} - \dots \right) = 18.75 \text{ V}$$

$$I_{SS}^- = -\frac{1}{3} + \frac{1}{45} - \frac{1}{675} + \dots = -\frac{1}{3} \left( 1 - \frac{1}{15} + \frac{1}{15^2} - \dots \right) = -0.3125 \text{ A}$$

$$V_{SS} = V_{SS}^+ + V_{SS}^- = 75 \text{ V}$$


$$I_{SS} = I_{SS}^+ + I_{SS}^- = 0.625 \text{ A}$$

### Example 3
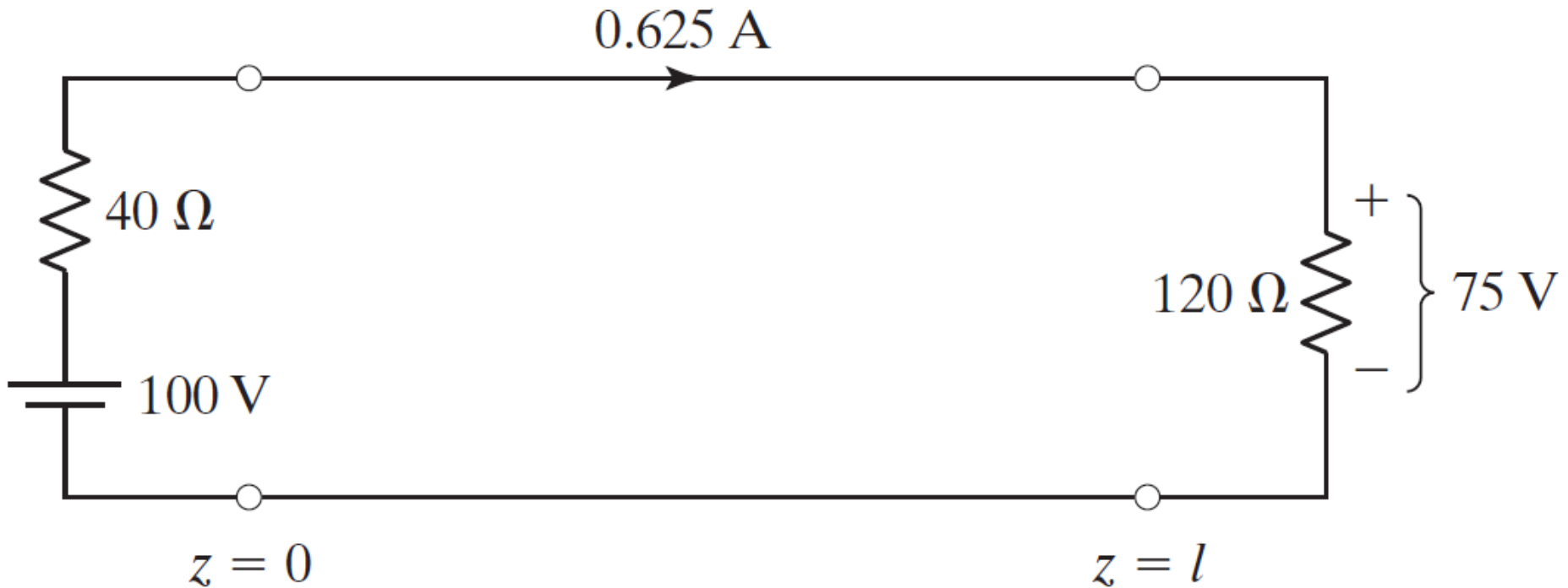
### Steady State Analysis


$$V_{SS} = V_{SS}^+ + V_{SS}^- = 75 \text{ V}$$

$$I_{SS} = I_{SS}^+ + I_{SS}^- = 0.625 \text{ A}$$


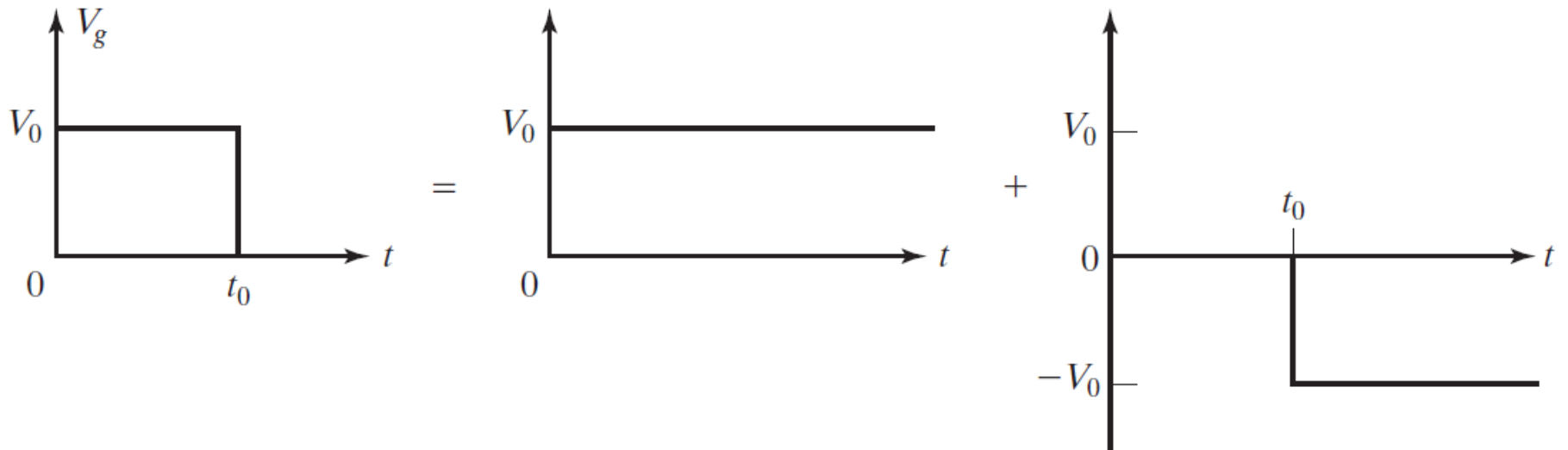
# How can we analyze a pulse signal?

Rectangular pulse as superposition of two step function signals



# Questions

What is the input impedance  $Z_{in}$  of these transmission lines?

