

ECE 329 – Fall 2022

Prof. Ravaioli – Office: 2062 ECEB

Lecture 32

Lecture 32 – Outline

- **Periodicity in transmission lines**
- **Resonances**
- **Standing waves and periodic oscillations**
- **Realization of reactance (inductance or capacitance) with short-circuited or with open-circuited transmission lines**

Reading assignment

**Prof. Kudeki's ECE 329 Lecture Notes on Fields and Waves:
32) Input Impedance and microwave resonators**

Line with a generic load impedance

Since the reflection coefficient is

$$\Gamma_L = \frac{V_0^-}{V_0^+}$$

we can derive

$$V(d) = V_0^+ e^{j\beta d} (1 + \Gamma_L e^{-2j\beta d}) = V_0^+ e^{j\beta d} (1 + \Gamma(d))$$

$$I(d) = \frac{V_0^+ e^{j\beta d}}{Z_0} (1 - \Gamma_L e^{-2j\beta d}) = \frac{V_0^+ e^{j\beta d}}{Z_0} (1 - \Gamma(d))$$

$$\Gamma(d) = \Gamma_L e^{-2j\beta d}$$


generalized reflection coefficient

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

line impedance


Significance of line impedance

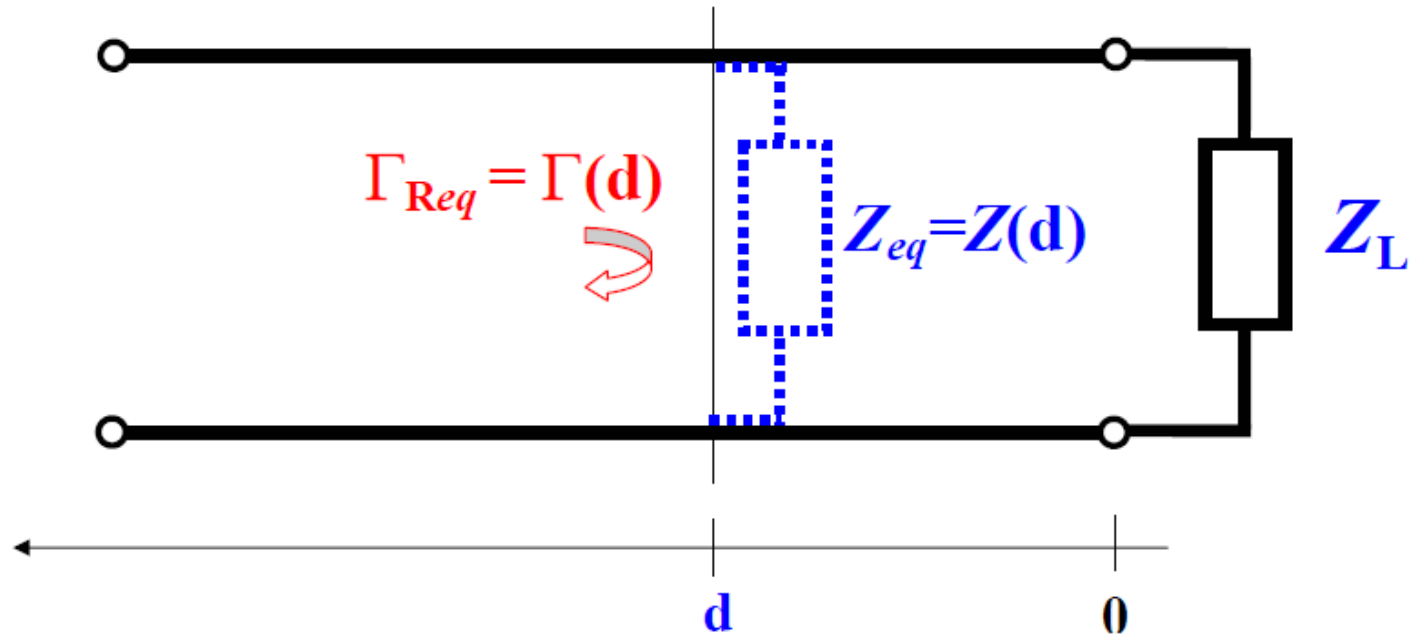Every line location is characterized by a **line impedance $Z(d)$** and a **reflection coefficient $\Gamma(d)$**




Imagine to cut the line at location d . The input impedance of the portion of line terminated by the load is the same as the line impedance at that location “before the cut”. **The behavior of the line on the left of location d is the same if an equivalent impedance with value $Z(d)$ replaces the cut out portion.**

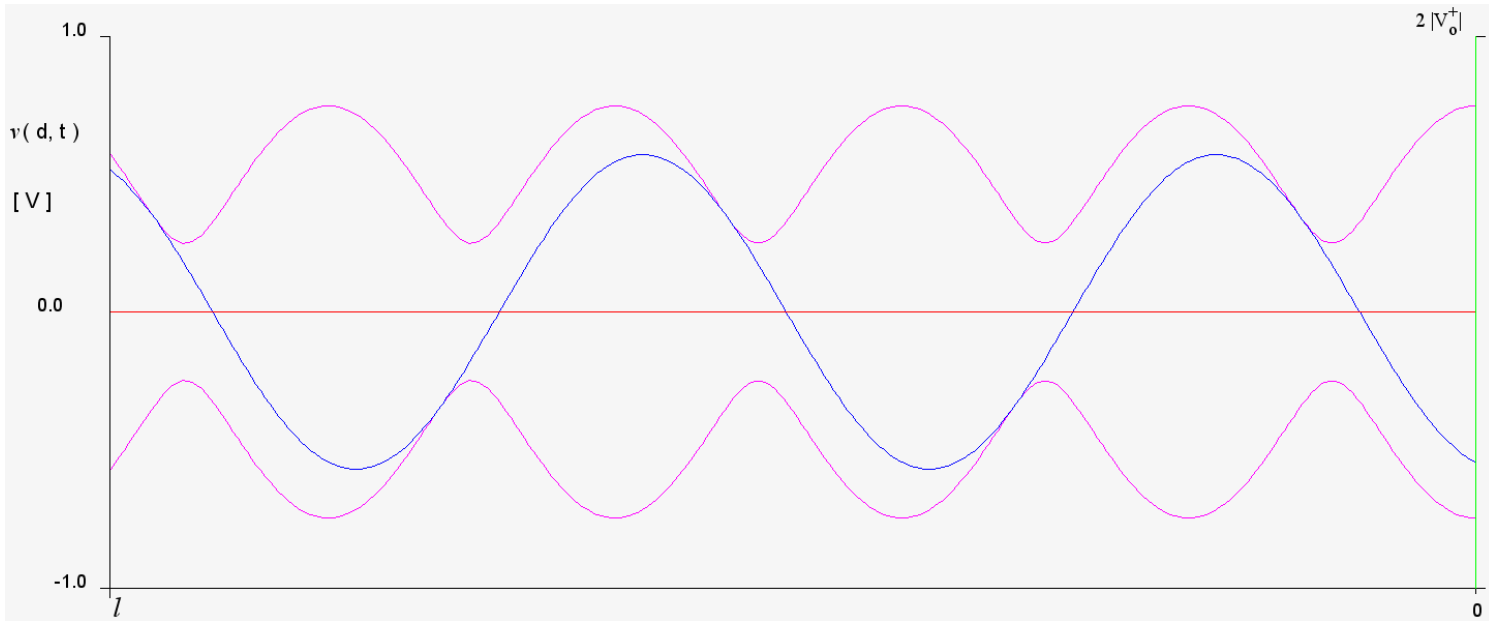
Line with arbitrary load $Z_0 = 50 \Omega$ and $Z_L = 150 \Omega$ $l = 2.38 \lambda$



same behavior at load

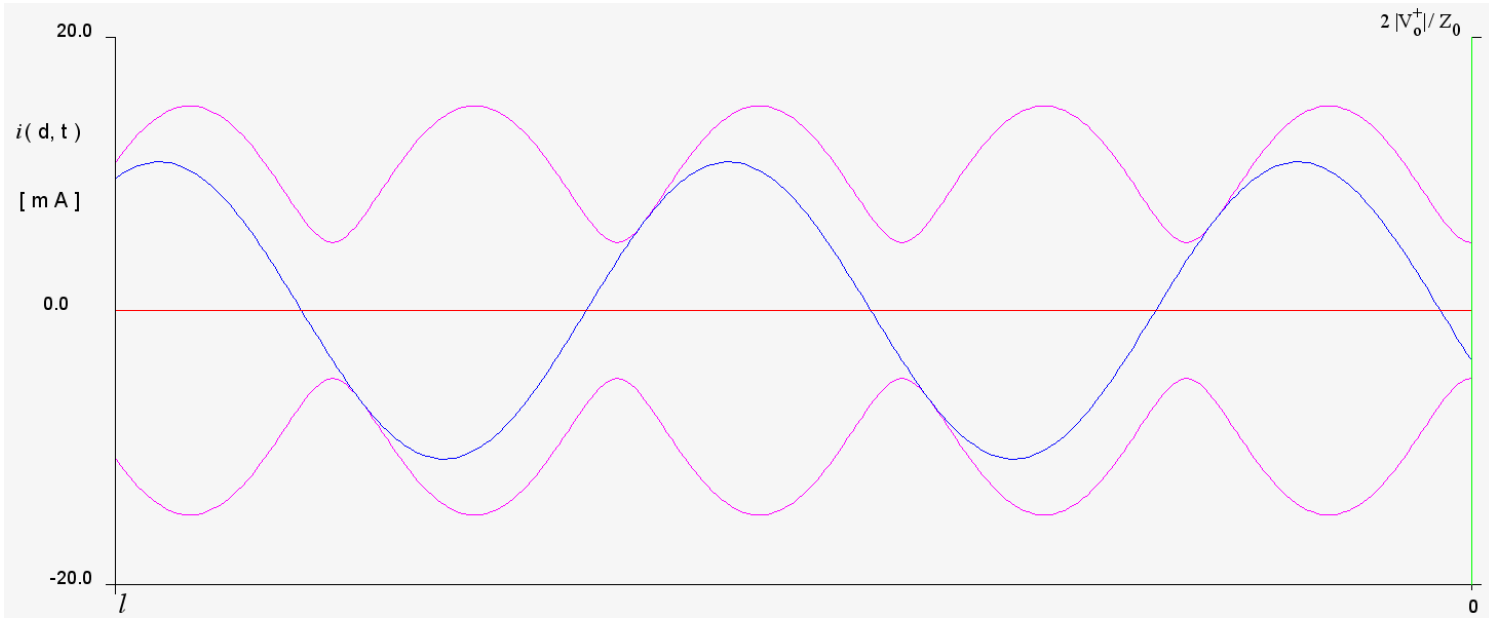

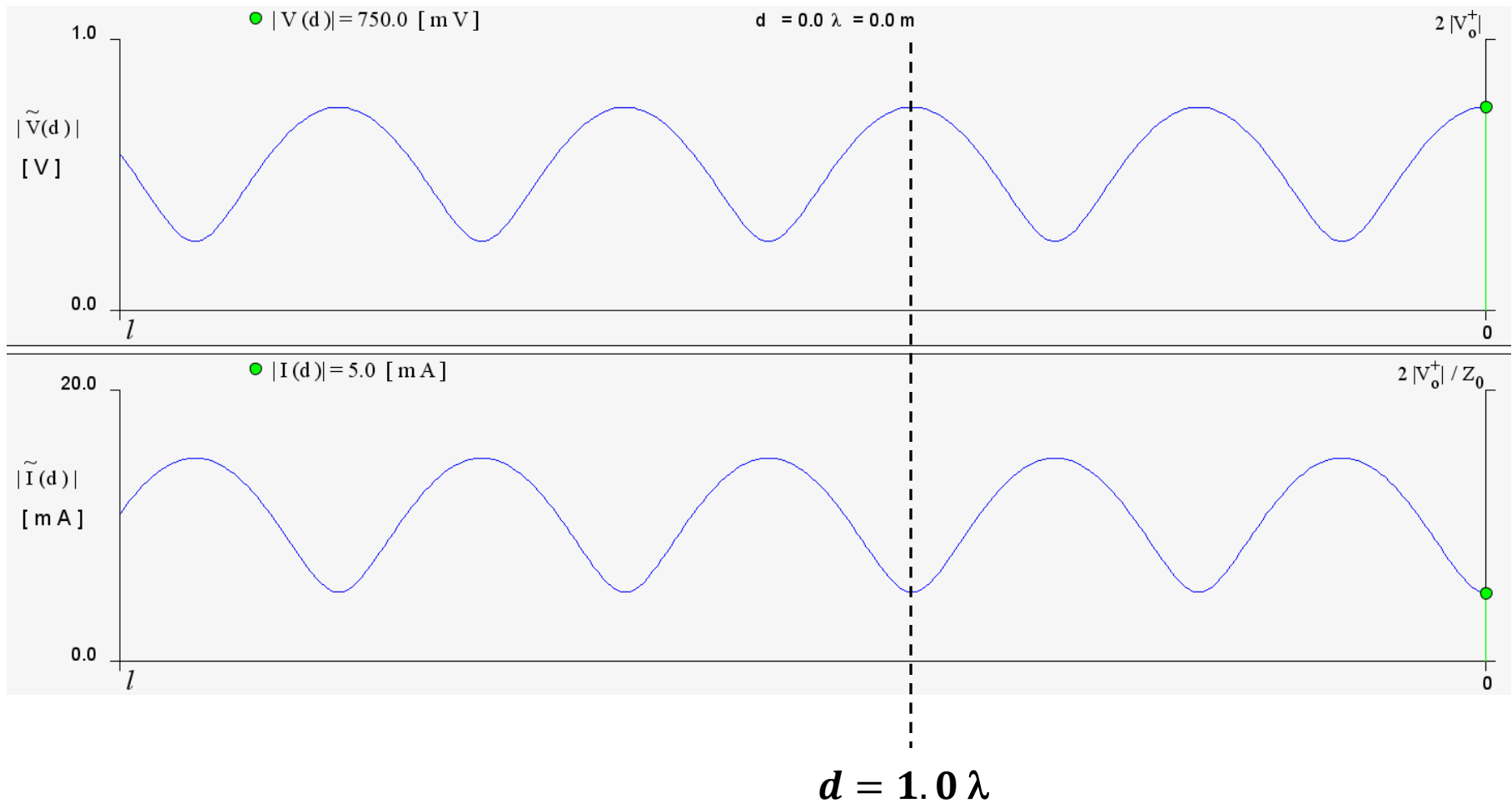
Line with arbitrary load $Z_0 = 50 \Omega$ and $Z_L = 150 \Omega$ $l = 2.38 \lambda$



Standing wave patterns

(Space-dependent magnitudes of the phasors for voltage and current) 6

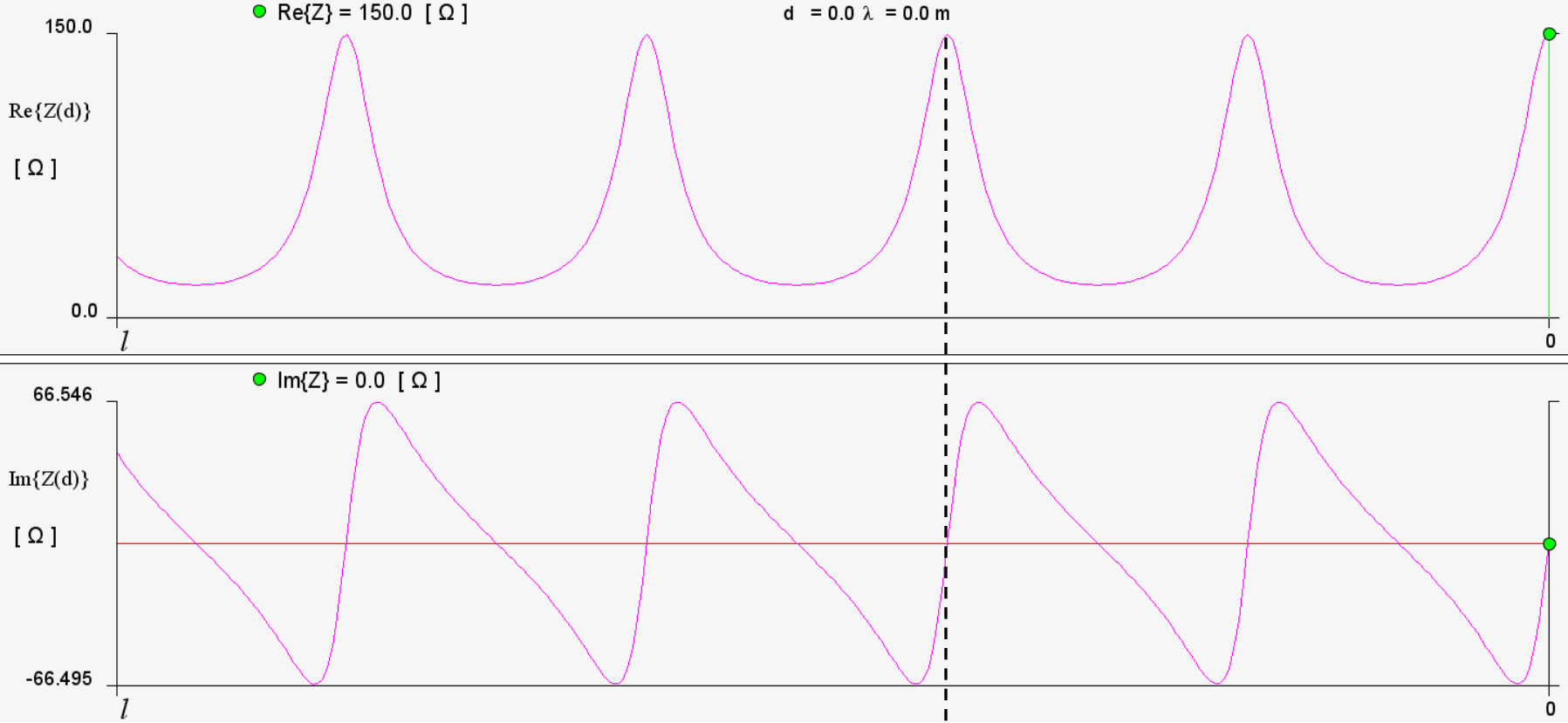
Line with arbitrary load $Z_0 = 50 \Omega$ and $Z_L = 150 \Omega$ $l = 2.38 \lambda$



$d = 1.0 \lambda$

Line impedance


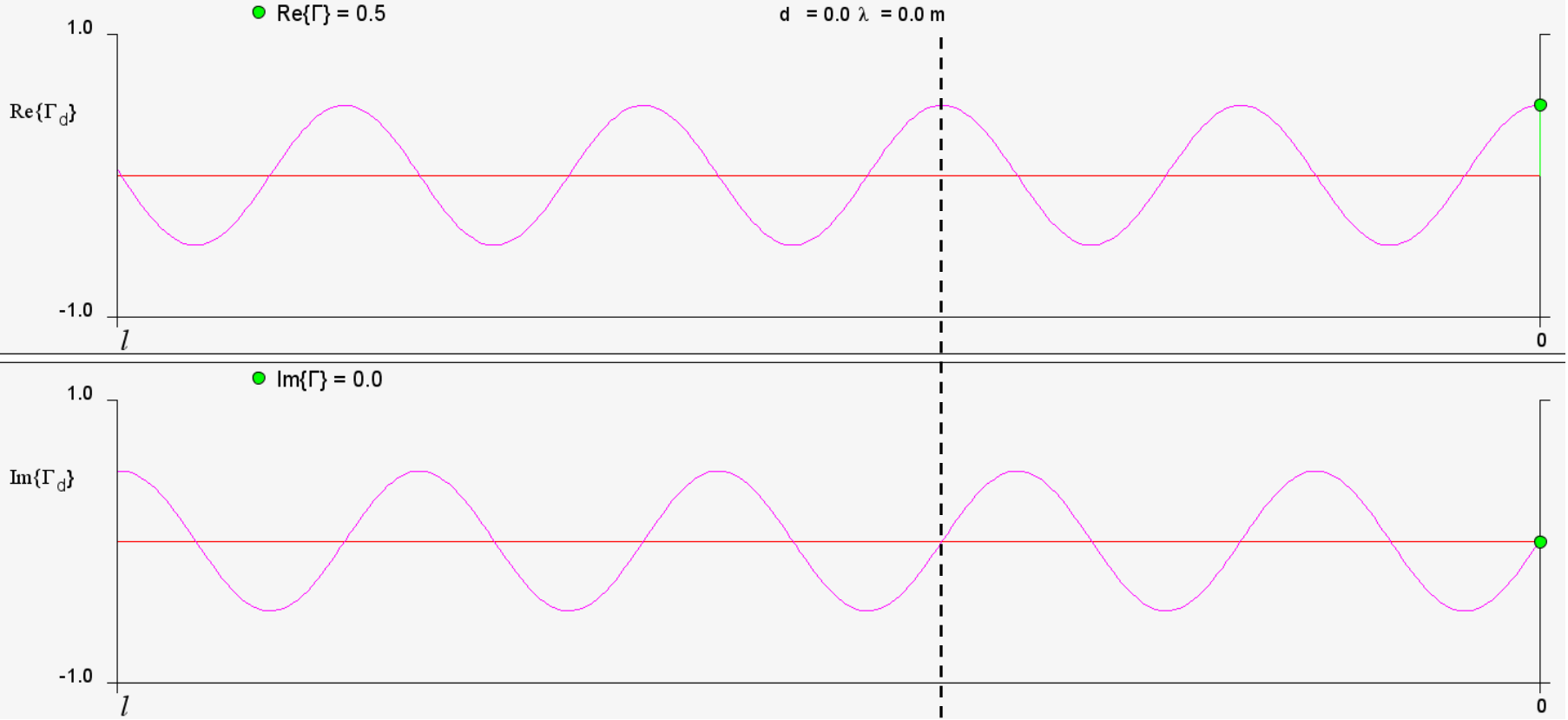
Line with arbitrary load $Z_0 = 50 \Omega$ and $Z_L = 150 \Omega$ $l = 2.38 \lambda$





$d = 1.0 \lambda$

Reflection coefficient

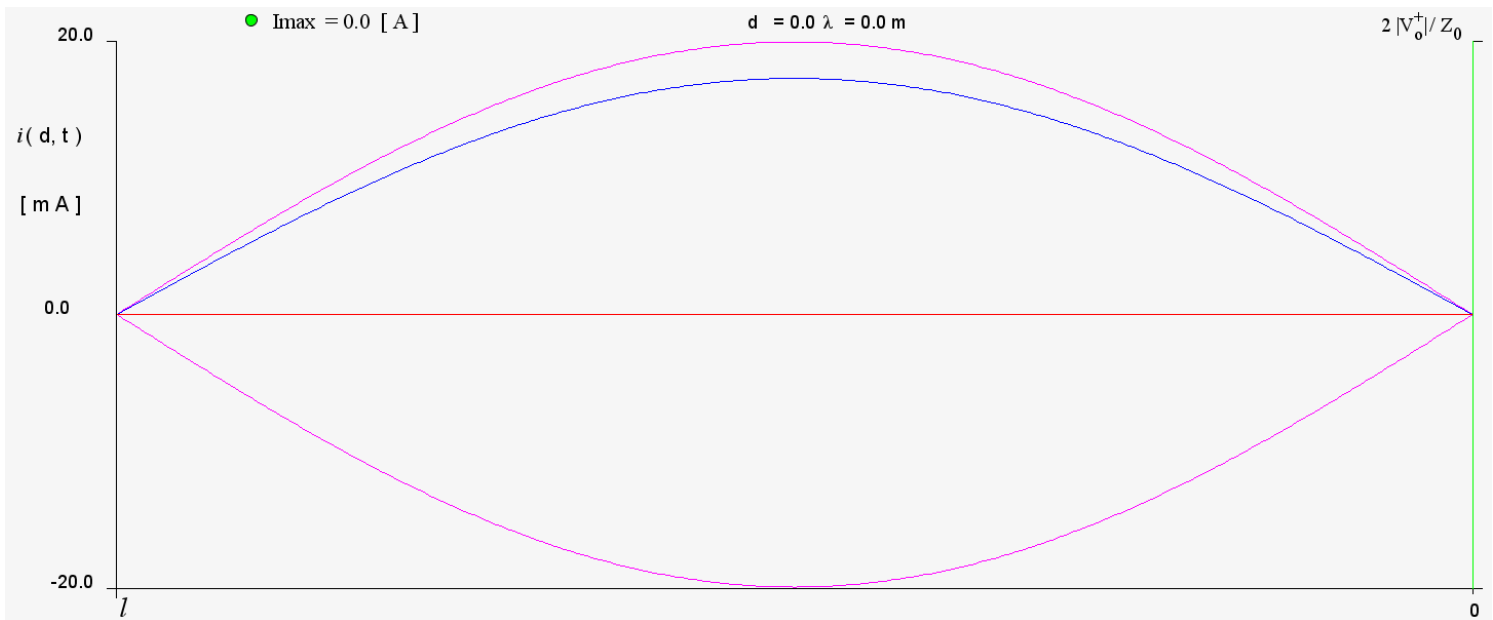
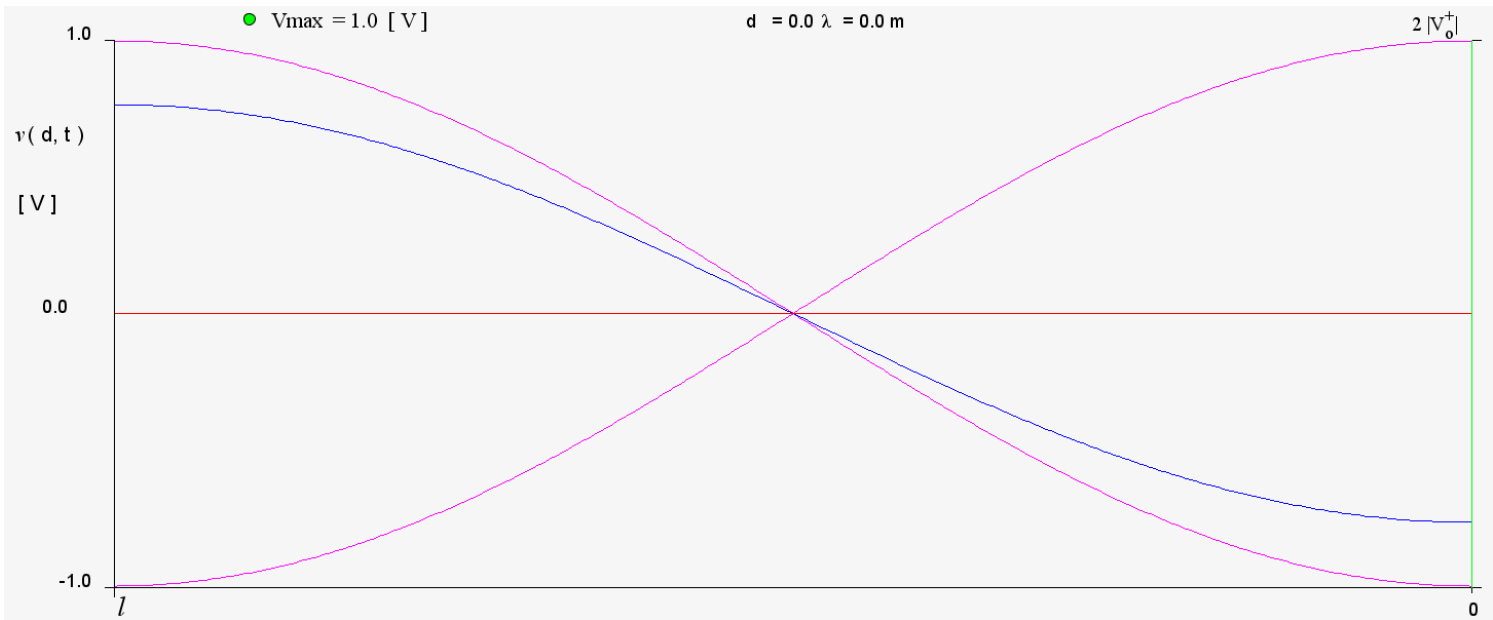
Line with open circuit load $Z_0 = 50 \Omega$ $l = 0.5 \lambda$



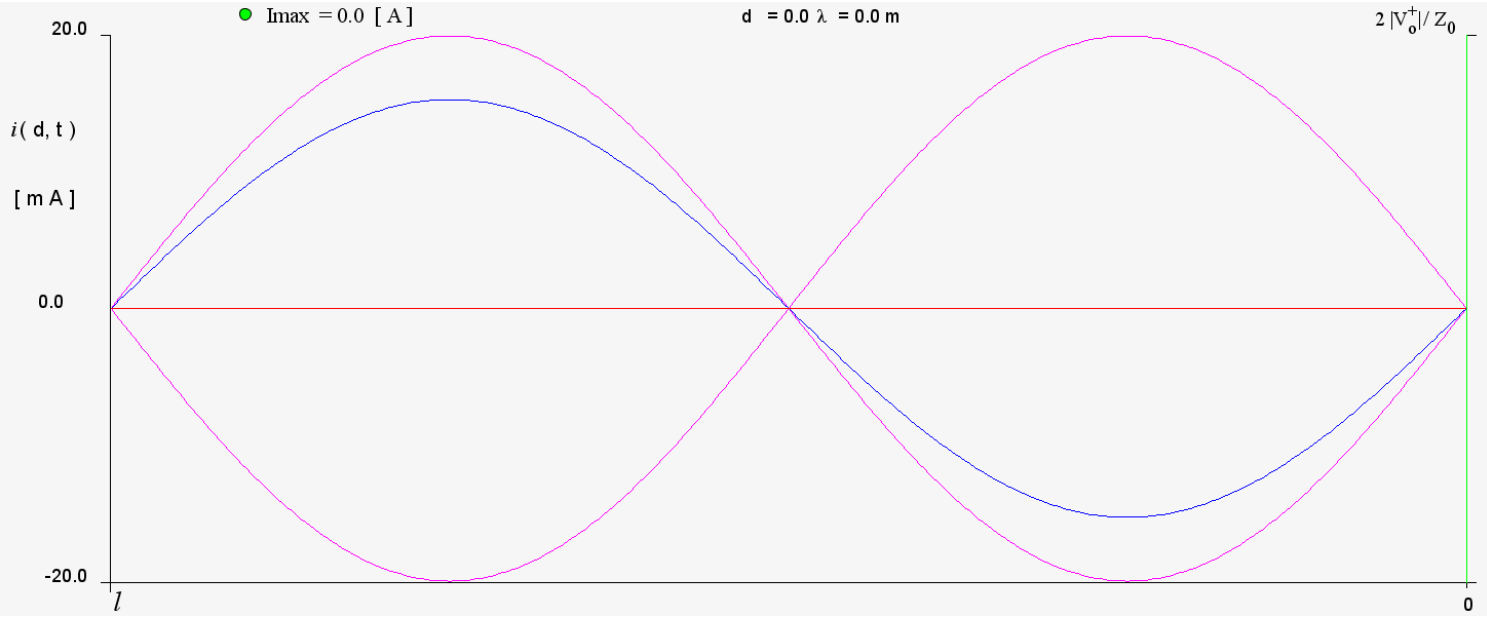
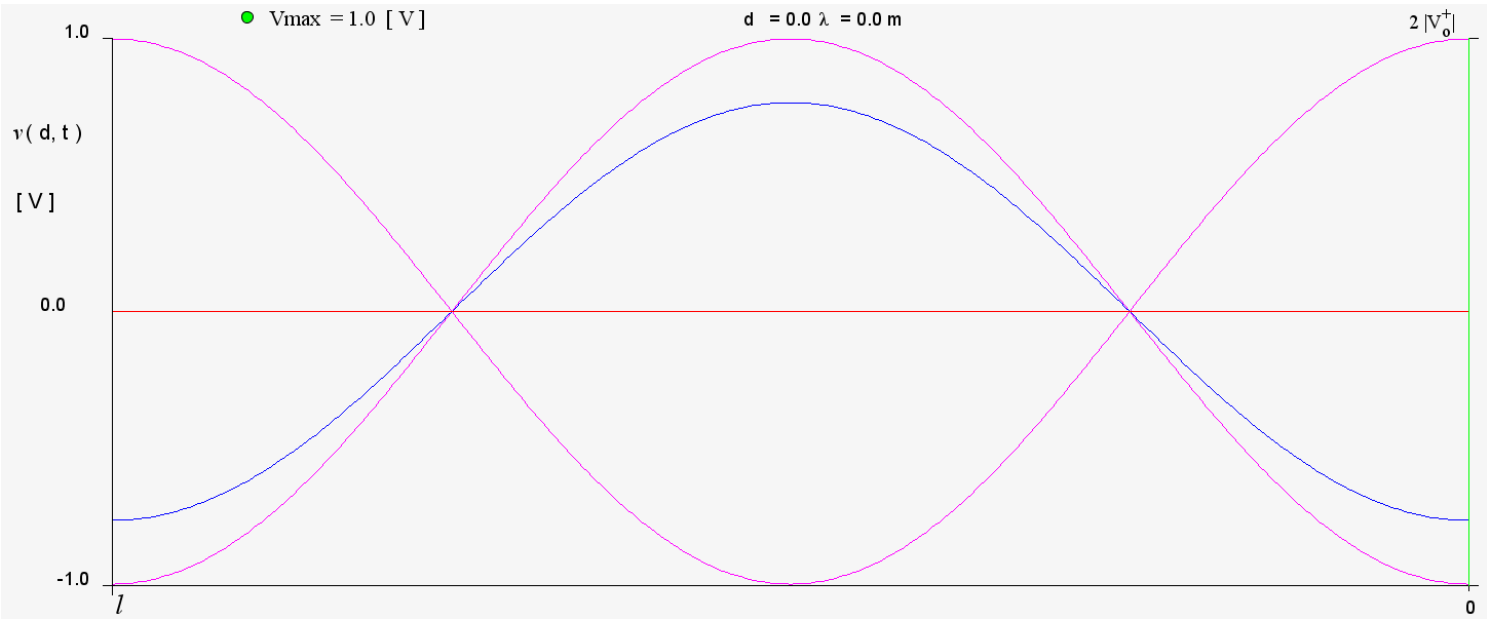
Line with open circuit load $Z_0 = 50 \Omega$ $l = 1.0 \lambda$



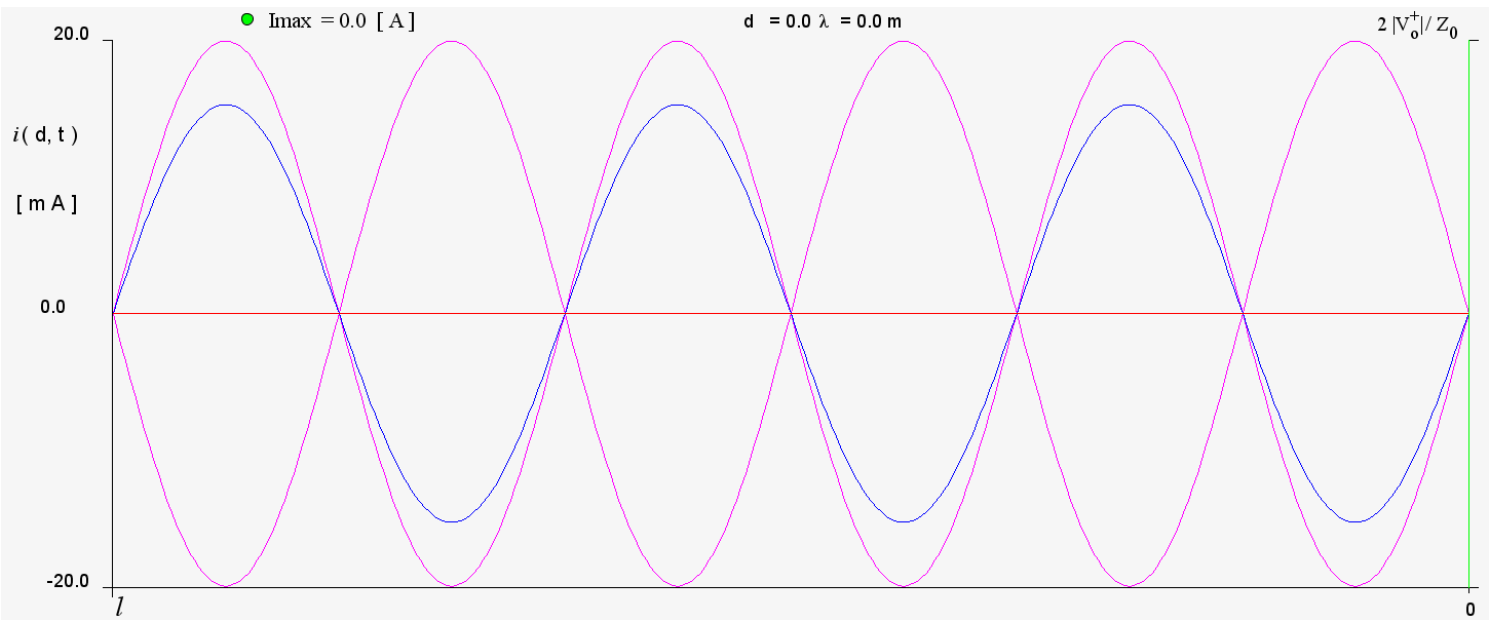
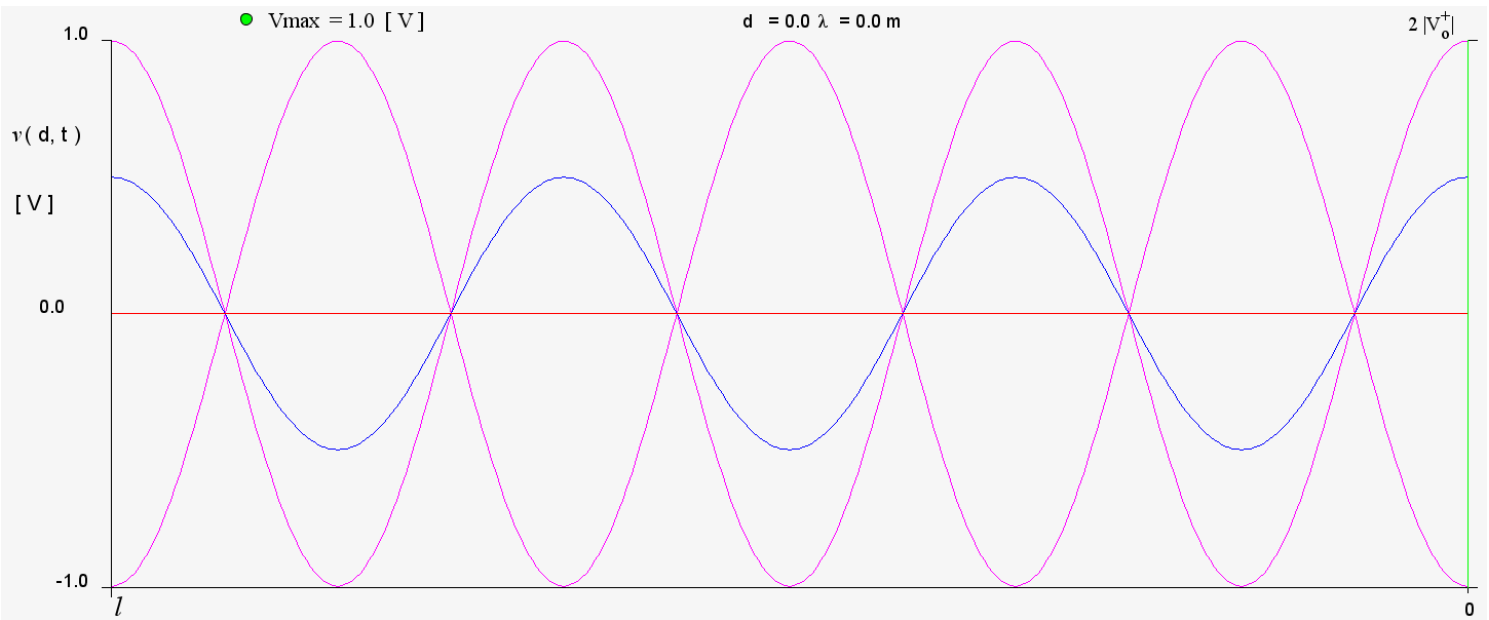
Line with open circuit load $Z_0 = 50 \Omega$ $l = 3.0 \lambda$



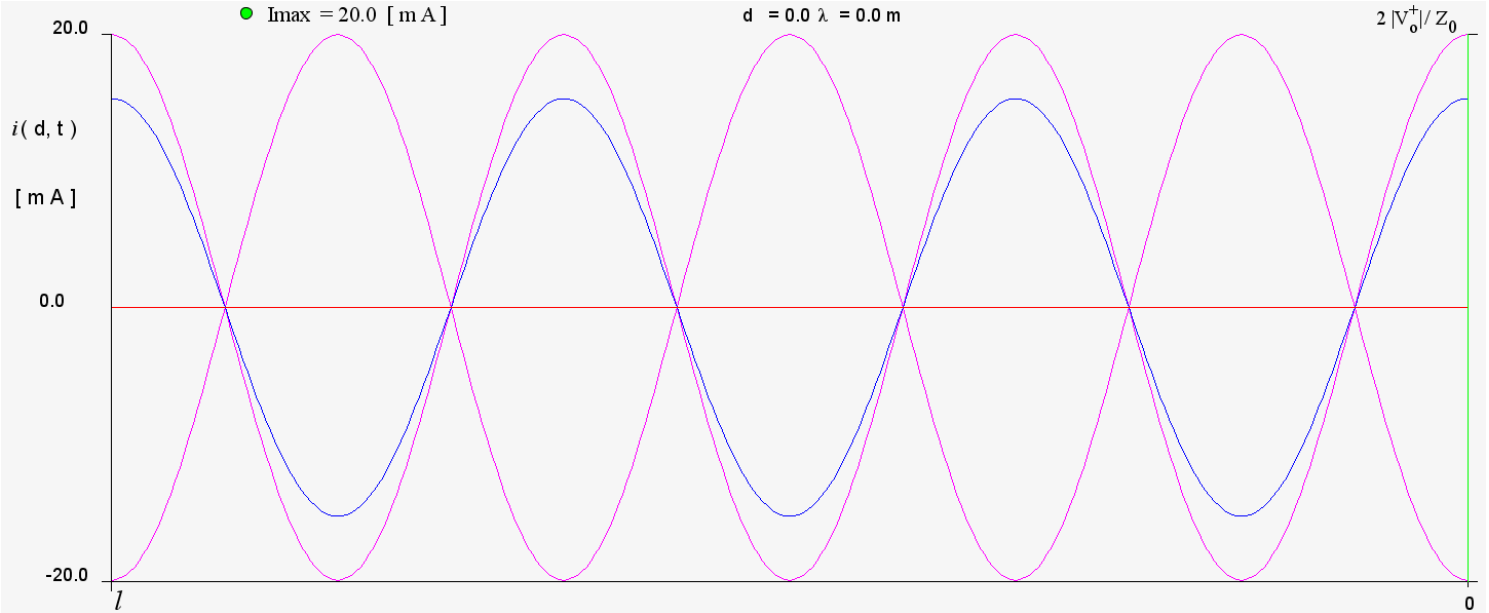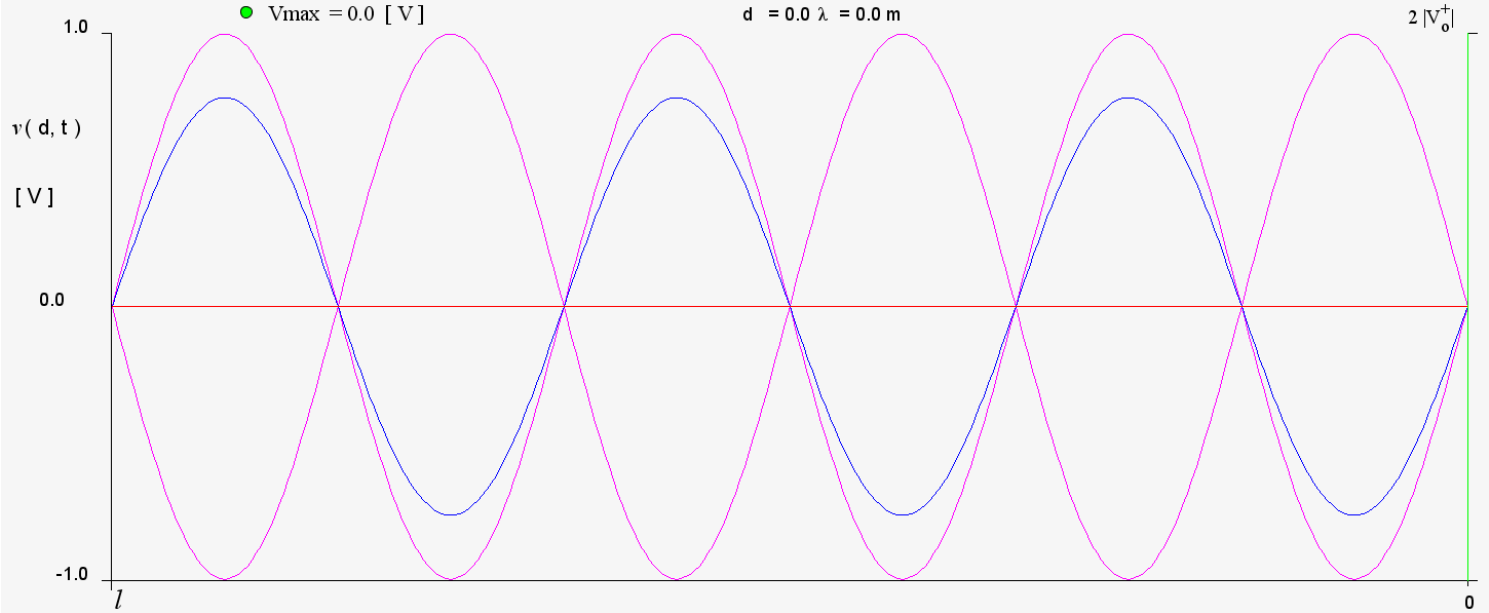Line with short circuit load $Z_0 = 50 \Omega$ $l = 3.0 \lambda$



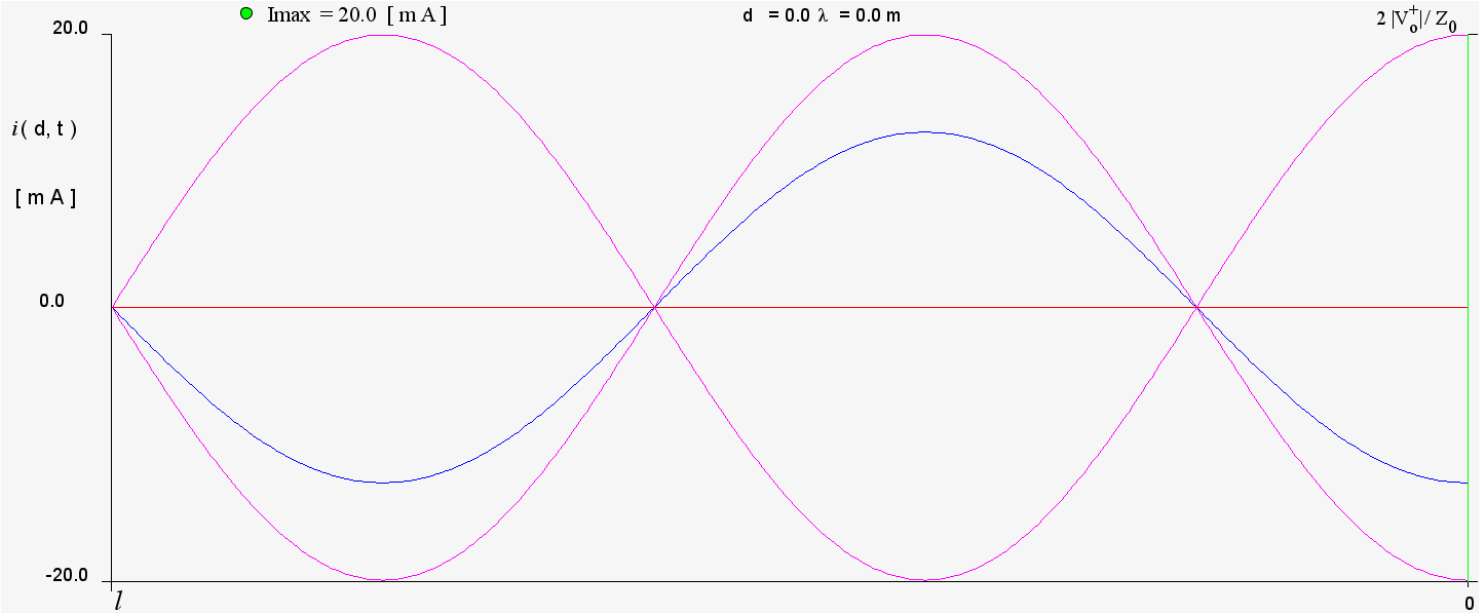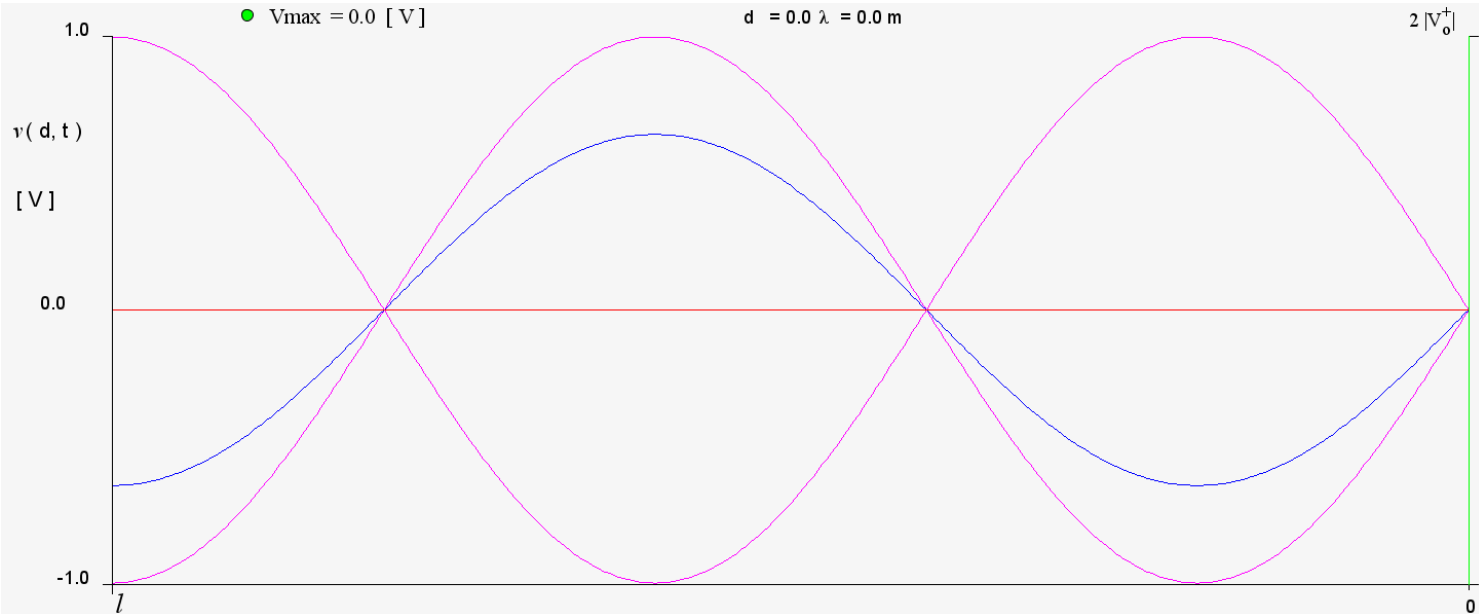short circuit load, open circuit input $Z_0 = 50 \Omega$ $l = 1.25 \lambda$



These explorations show that periodicity of line properties are established by the reflection coefficient which repeats every $\lambda/2$.

For a given length of line we can identify **resonant modes** (complete standing waves) for frequencies which correspond to multiples of $\lambda/2$, when the ends of the line are both open circuits or short circuits.

resonant frequency

$$\omega = \frac{\pi v}{\ell} n$$

$$f = \frac{v}{2\ell} n \text{ Hz}$$

resonant wavelength

$$\lambda = \frac{v}{f} = \frac{2\ell}{n}$$



implying that resonances occur at frequencies for which the physical length corresponds to an integer number of $\lambda/2$.

$$\ell = n \frac{\lambda}{2}$$

Consider a line section open circuited at both ends. The current is expressed by forward and reflected waves as

$$I(z, t) = \frac{f(t - \frac{z}{v})}{Z_o} - \frac{g(t + \frac{z}{v})}{Z_o}$$

with zero boundary conditions at the ends

$$I(0, t) = \frac{f(t)}{Z_o} - \frac{g(t)}{Z_o} = 0$$

waveforms are the same



$$g(t) = f(t)$$

$$I(l, t) = \frac{f(t - \frac{l}{v})}{Z_o} - \frac{g(t + \frac{l}{v})}{Z_o} = 0$$



$$f(t - \frac{l}{v}) = f(t + \frac{l}{v})$$

$$f(t) = f(t + \frac{2l}{v})$$

period

$$T = \frac{2l}{v}$$

periodicity

fundamental
frequency

$$\omega_o = \frac{2\pi}{T} = \frac{\pi v}{l}$$

From Fourier analysis

$$f(t) = F_o + \sum_{n=1}^{\infty} F_n \cos(n\omega_o t + \theta_n)$$

with zero boundary conditions at the ends

$$\begin{aligned} I(z, t) &= \frac{f(t - \frac{z}{v}) - f(t + \frac{z}{v})}{Z_o} \\ &= \sum_{n=1}^{\infty} \frac{F_n}{Z_o} [\cos(n\omega_o t + \theta_n - n\beta_o z) - \cos(n\omega_o t + \theta_n + n\beta_o z)] \end{aligned}$$

fundamental
wavenumber

$$\beta_o \equiv \omega_o / v = \pi / \ell$$

$$\beta_o = \frac{2\pi}{\lambda_o} \rightarrow \ell = \frac{\lambda_o}{2}$$

In phasor form

$$\begin{aligned}\tilde{I}(z) &= \sum_{n=1}^{\infty} \frac{F_n}{Z_o} e^{j\theta_n} [e^{-jn\beta_o z} - e^{jn\beta_o z}] \\ &= \sum_{n=1}^{\infty} \frac{F_n}{Z_o} e^{j\theta_n} (-2j) \sin(n\beta_o z)\end{aligned}$$

Back to the time domain

$$I(z, t) = \sum_{n=1}^{\infty} \frac{2F_n}{Z_o} \sin(n\omega_o t + \theta_n) \sin(n\beta_o z)$$

$2 \sin(A) \sin(B) = \cos(A - B) - \cos(A + B)$

compare with original form

Similarly for the voltage

$$V(z, t) = \sum_{n=1}^{\infty} 2F_n \cos(n\omega_o t + \theta_n) \cos(n\beta_o z)$$

from the phasor form

$$\tilde{V}(z) = \sum_n F_n e^{j\theta_n} [e^{-jn\beta_o z} + e^{jn\beta_o z}]$$

If the transmission line is terminated by a short circuit and has an open circuit on the other end then resonant frequencies are obtained when the length ℓ corresponds to an odd multiple of $\lambda/4$

$$\frac{\lambda}{4} = \frac{2\pi/\beta}{4} = \frac{\pi}{2\beta}$$

resonant condition

$$\ell = \frac{\lambda}{4} (2n + 1), \quad n \geq 0$$

$$\omega = \frac{\pi v}{\ell} \left(\frac{1}{2} + n \right)$$

resonant frequency


$$f = \frac{v}{2\ell} \left(\frac{1}{2} + n \right)$$

for $n \geq 0$

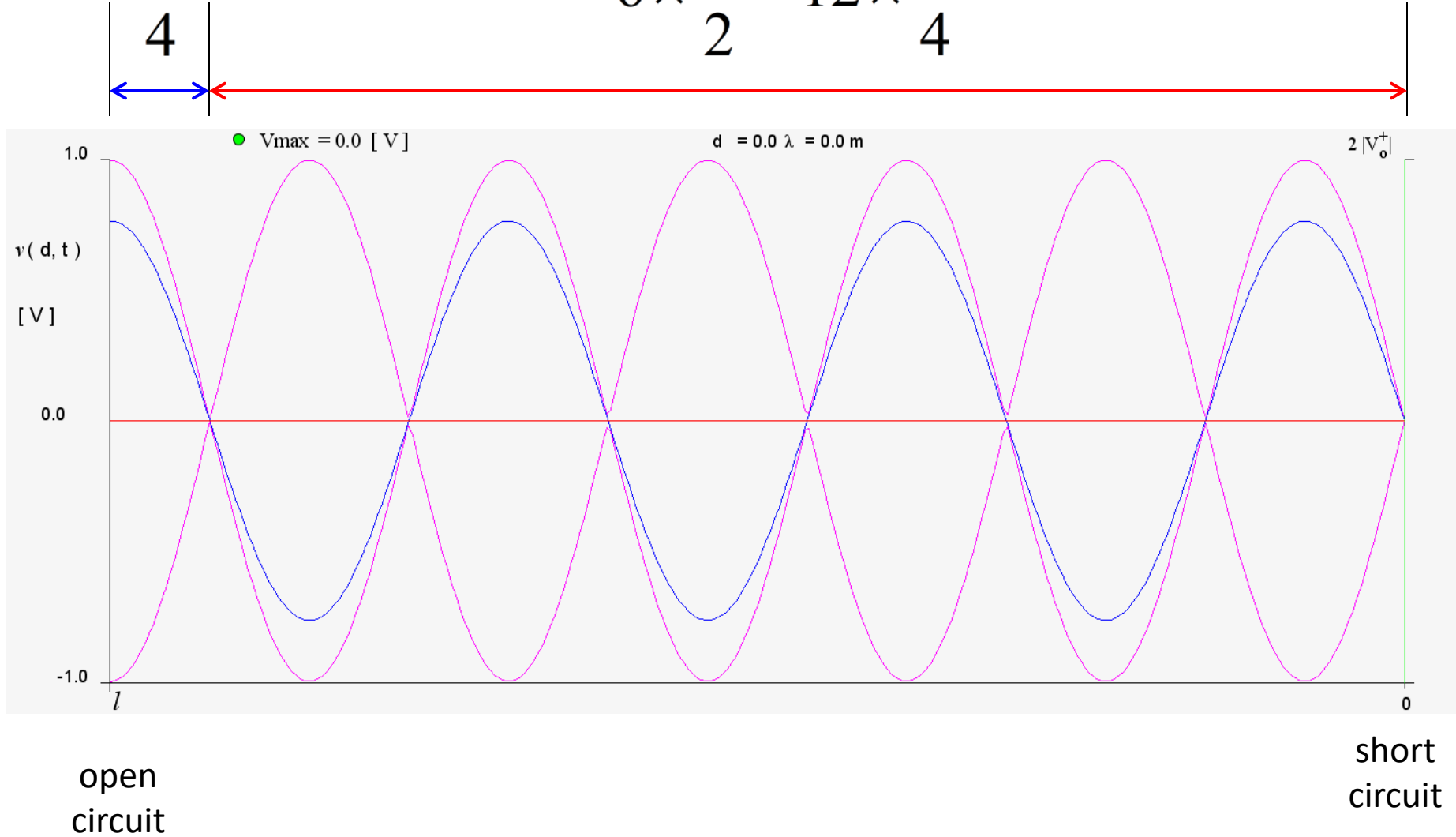
Example

$$\frac{\lambda}{4}$$

$$6 \times \frac{\lambda}{2} = 12 \times \frac{\lambda}{4}$$



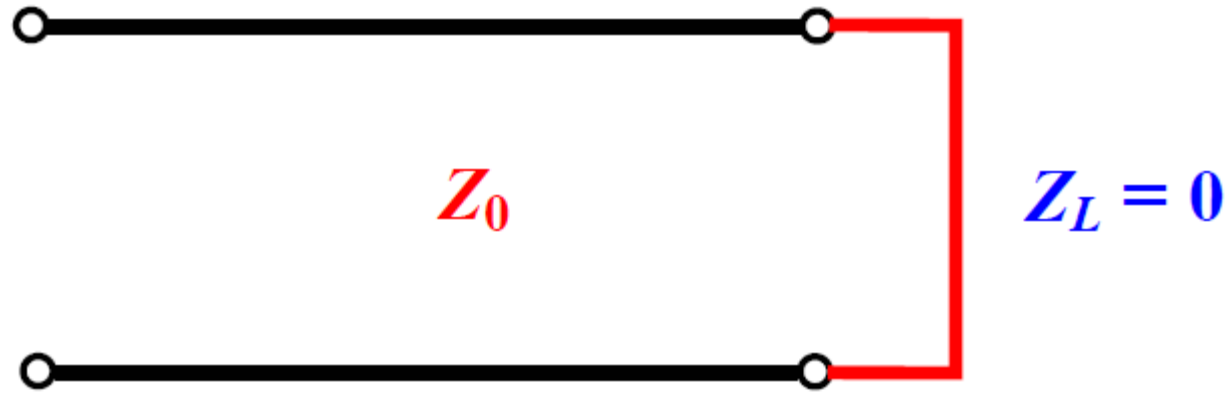Realize any imaginary impedance with a short-circuited line



$$V(d = 0) = V_0^+ e^{j\beta_0} [1 + \Gamma_L e^{j2\beta_0}] = V_0^+ [1 + \Gamma_L] = 0$$

$$\Rightarrow \Gamma_L = -1$$

$$\Gamma_L = \frac{V_0^-}{V_0^+} \Rightarrow V_0^- = -V_0^+$$

short-circuited line

line voltage

$$\begin{aligned} V(d) &= V_0^+ e^{j\beta d} + V_0^- e^{-j\beta d} = V_0^+ e^{j\beta d} - V_0^+ e^{-j\beta d} \\ &= V_0^+ \left[e^{j\beta d} - e^{-j\beta d} \right] = 2jV_0^+ \sin(\beta d) \end{aligned}$$

line current

$$\begin{aligned} I(d) &= \frac{1}{Z_0} \left[V_0^+ e^{j\beta d} - V_0^- e^{-j\beta d} \right] = \frac{1}{Z_0} \left[V_0^+ e^{j\beta d} + V_0^+ e^{-j\beta d} \right] \\ &= \frac{V_0^+}{Z_0} \left[e^{j\beta d} + e^{-j\beta d} \right] = \frac{2V_0^+}{Z_0} \cos(\beta d) \end{aligned}$$

line impedance

$$Z(d) = \frac{V(d)}{I(d)} = \frac{2jV_0^+ \sin(\beta d)}{2V_0^+ \cos(\beta d)/Z_0} = jZ_0 \tan(\beta d)$$

Realize any imaginary impedance with an open-circuited line



Z_0

$Z_L \rightarrow \infty$



$$I(d=0) = \frac{V_0^+}{Z_0} e^{j\beta_0 d} [1 - \Gamma_L e^{j2\beta_0 d}] = \frac{V_0^+}{Z_0} [1 - \Gamma_L] = 0$$

$$\Rightarrow \Gamma_L = 1$$

$$\Gamma_L = \frac{V_0^-}{V_0^+} \Rightarrow V_0^- = V_0^+$$

open-circuited line

line voltage

$$\begin{aligned} V(d) &= V_0^+ e^{j\beta d} + V_0^- e^{-j\beta d} = V_0^+ e^{j\beta d} + V_0^+ e^{-j\beta d} \\ &= V_0^+ \left[e^{j\beta d} + e^{-j\beta d} \right] = 2V_0^+ \cos(\beta d) \end{aligned}$$

line current

$$\begin{aligned} I(d) &= \frac{1}{Z_0} \left[V_0^+ e^{j\beta d} - V_0^- e^{-j\beta d} \right] = \frac{1}{Z_0} \left[V_0^+ e^{j\beta d} - V_0^+ e^{-j\beta d} \right] \\ &= \frac{V_0^+}{Z_0} \left[e^{j\beta d} - e^{-j\beta d} \right] = \frac{2jV_0^+}{Z_0} \sin(\beta d) \end{aligned}$$

line impedance

$$Z(d) = \frac{V(d)}{I(d)} = \frac{2V_0^+ \cos(\beta d)}{2jV_0^+ \sin(\beta d)/Z_0} = -j \frac{Z_0}{\tan(\beta d)}$$

Reactive impedances can be realized with **transmission lines** terminated by a short or by an open circuit. The input impedance of a loss-less transmission line of length **L** terminated by a **short circuit** is purely imaginary

$$Z_{in} = j Z_0 \tan(\beta L) = j Z_0 \tan\left(\frac{2\pi}{\lambda} L\right) = j Z_0 \tan\left(\frac{2\pi f}{v_p} L\right)$$

For a specified frequency f , **any reactance value** (positive or negative!) can be obtained by changing the length of the line from 0 to $\lambda/2$. An inductance is realized for $L < \lambda/4$ (positive tangent) while a capacitance is realized for $\lambda/4 < L < \lambda/2$ (negative tangent).

When $L = 0$ and $L = \lambda/2$ the tangent is zero, and the input impedance corresponds to a **short circuit**. However, when $L = \lambda/4$ the tangent is infinite and the input impedance corresponds to an **open circuit**.

Since the tangent function is **periodic**, the same impedance behavior of the impedance will repeat identically for each additional line increment of length $\lambda/2$. A similar **periodic** behavior is also obtained when the length of the line is fixed and the frequency of operation is changed.

At zero frequency (infinite wavelength), the short circuited line behaves as a short circuit for any line length. When the frequency is increased, the wavelength shortens and one obtains an inductance for $L < \lambda/4$ and a capacitance for $\lambda/4 < L < \lambda/2$, with an open circuit at $L = \lambda/4$ and a short circuit again at $L = \lambda/2$.


Note that the frequency behavior of lumped elements is very different. Consider an ideal inductor with inductance L assumed to be constant with frequency, for simplicity. At zero frequency the inductor also behaves as a short circuit, but the reactance varies **monotonically** and **linearly** with frequency as

$$X = \omega L \text{ (always an inductance)}$$


Short circuited transmission line – Fixed frequency

L	$L = 0$	$Z_{in} = 0$	short circuit
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance
	$L = \frac{\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} < 0$	capacitance
	$L = \frac{\lambda}{2}$	$Z_{in} = 0$	short circuit
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance
	$L = \frac{3\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} < 0$	capacitance

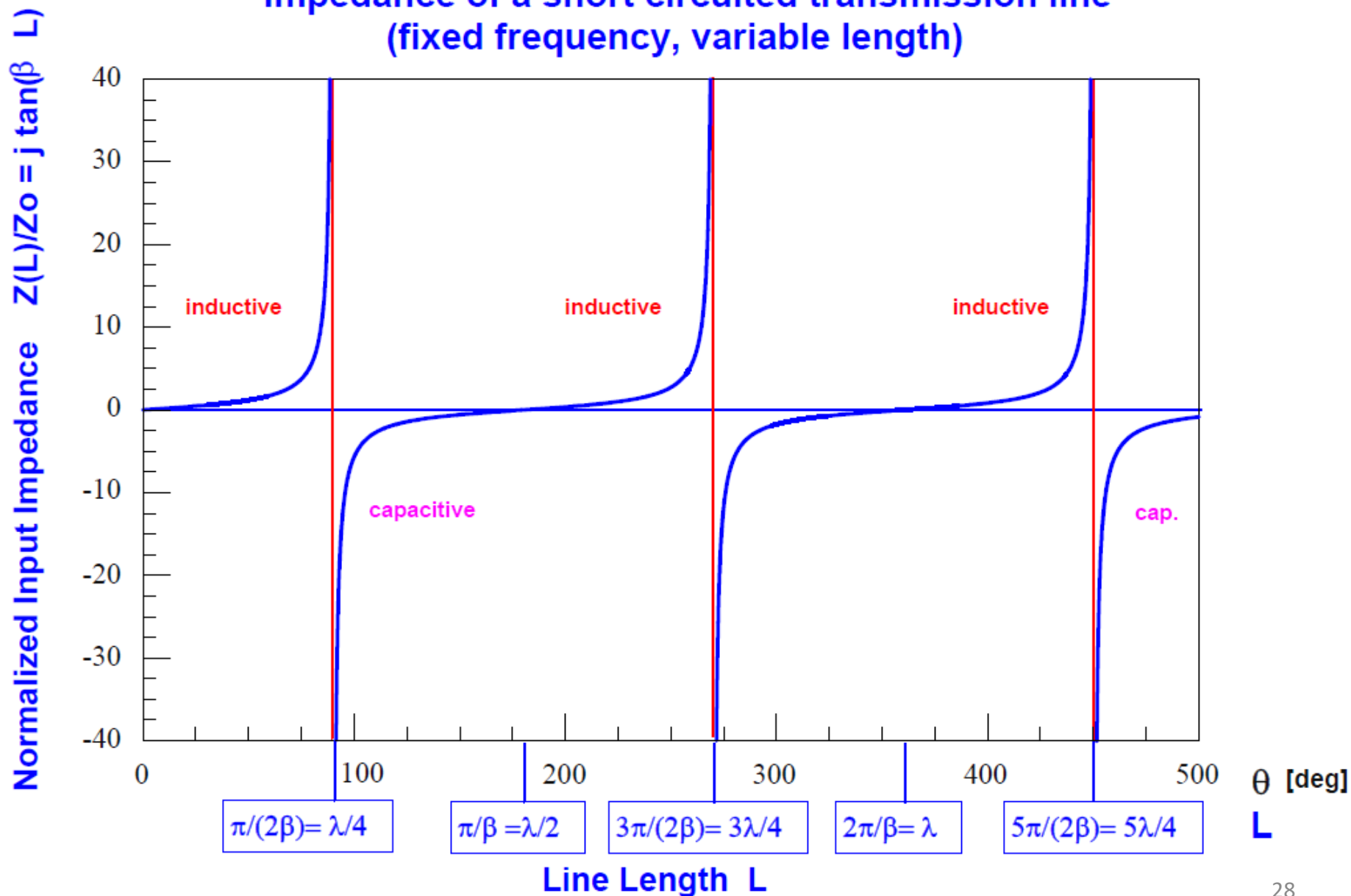Impedance of a short circuited transmission line (fixed frequency, variable length)



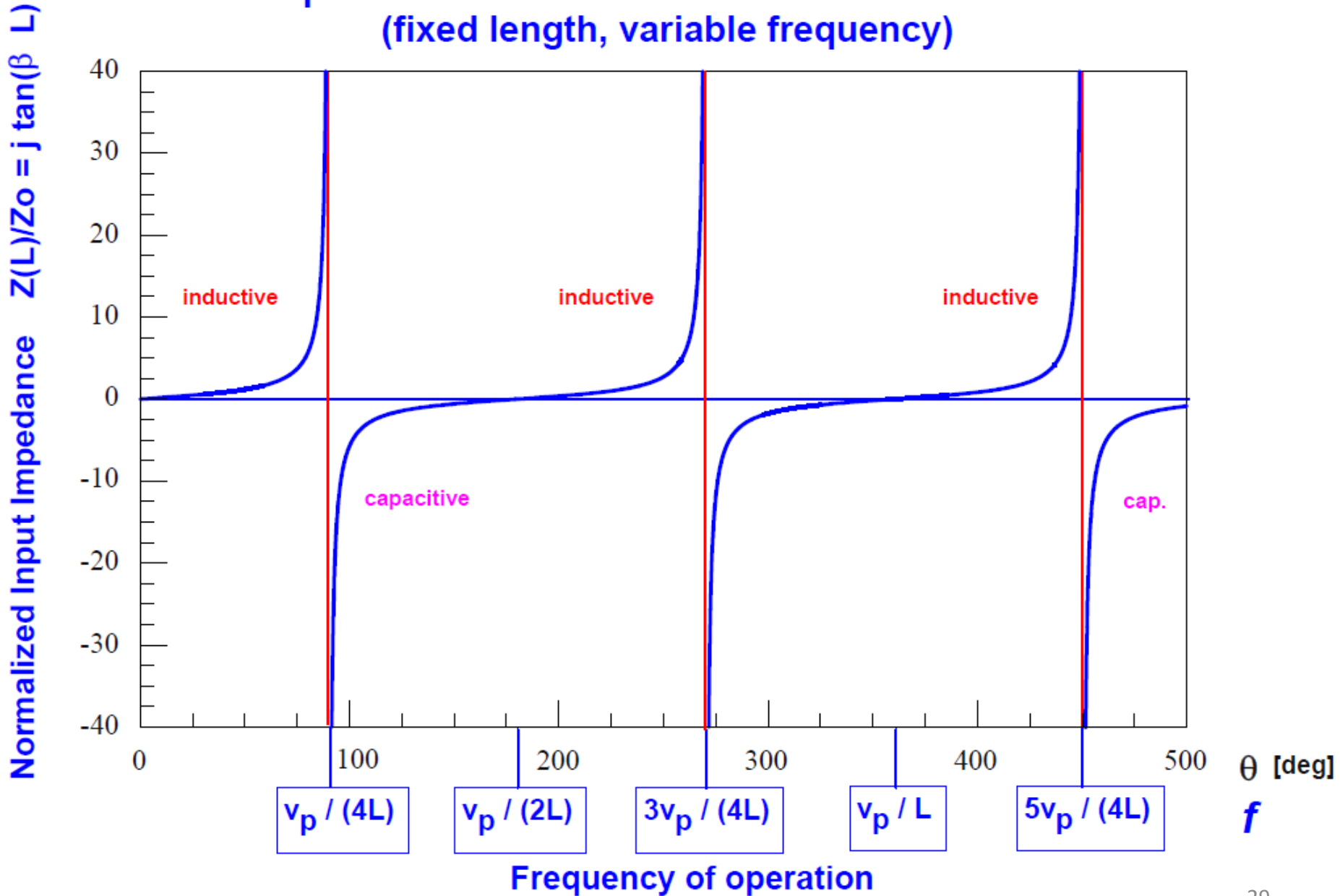Impedance of a short circuited transmission line (fixed length, variable frequency)



L = Line length

For a transmission line of length L terminated by an open circuit, the input impedance is again purely imaginary

$$Z_{in} = -j \frac{Z_0}{\tan(\beta L)} = -j \frac{Z_0}{\tan\left(\frac{2\pi}{\lambda} L\right)} = -j \frac{Z_0}{\tan\left(\frac{2\pi f}{v_p} L\right)}$$

We can also use the open circuited line to realize any reactance, but starting from a **capacitive** value when the line length is very short.

Note once again that the frequency behavior of a corresponding lumped element is different. Consider an ideal capacitor with capacitance C assumed to be constant with frequency. At zero frequency the capacitor behaves as an open circuit, but the reactance varies **monotonically** and **linearly** with frequency as

$$X = \frac{1}{\omega C} \text{ (always a capacitance)}$$


Open circuit transmission line – Fixed frequency

L ↓	$L = 0$	$Z_{in} \rightarrow \infty$	open circuit	}
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{\lambda}{2}$	$Z_{in} \rightarrow \infty$	open circuit	}
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{3\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} > 0$	inductance	


...

Impedance of an open circuited transmission line (fixed frequency, variable length)

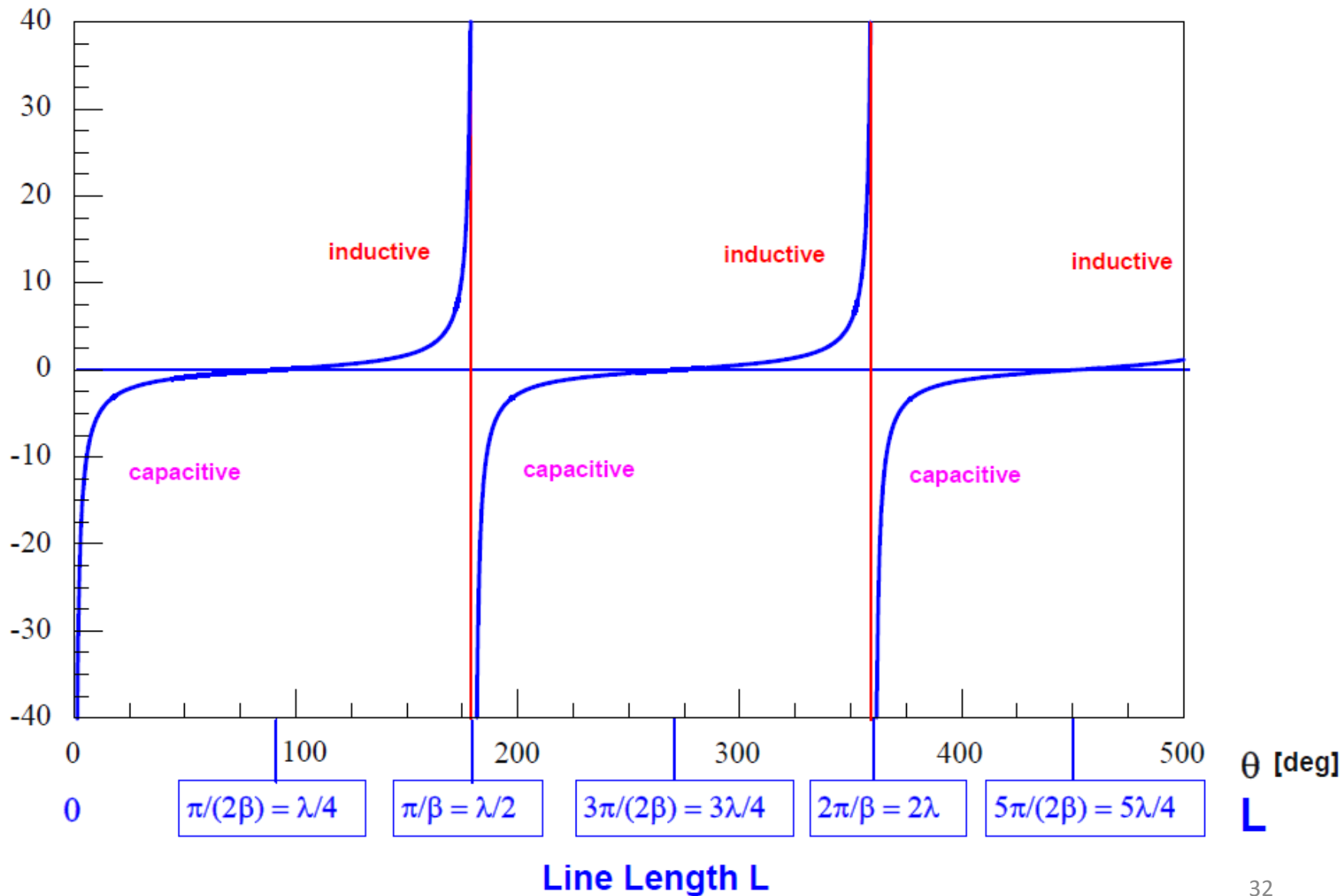Normalized Input Impedance $Z(L)/Z_0 = -j \cotan(\beta L)$



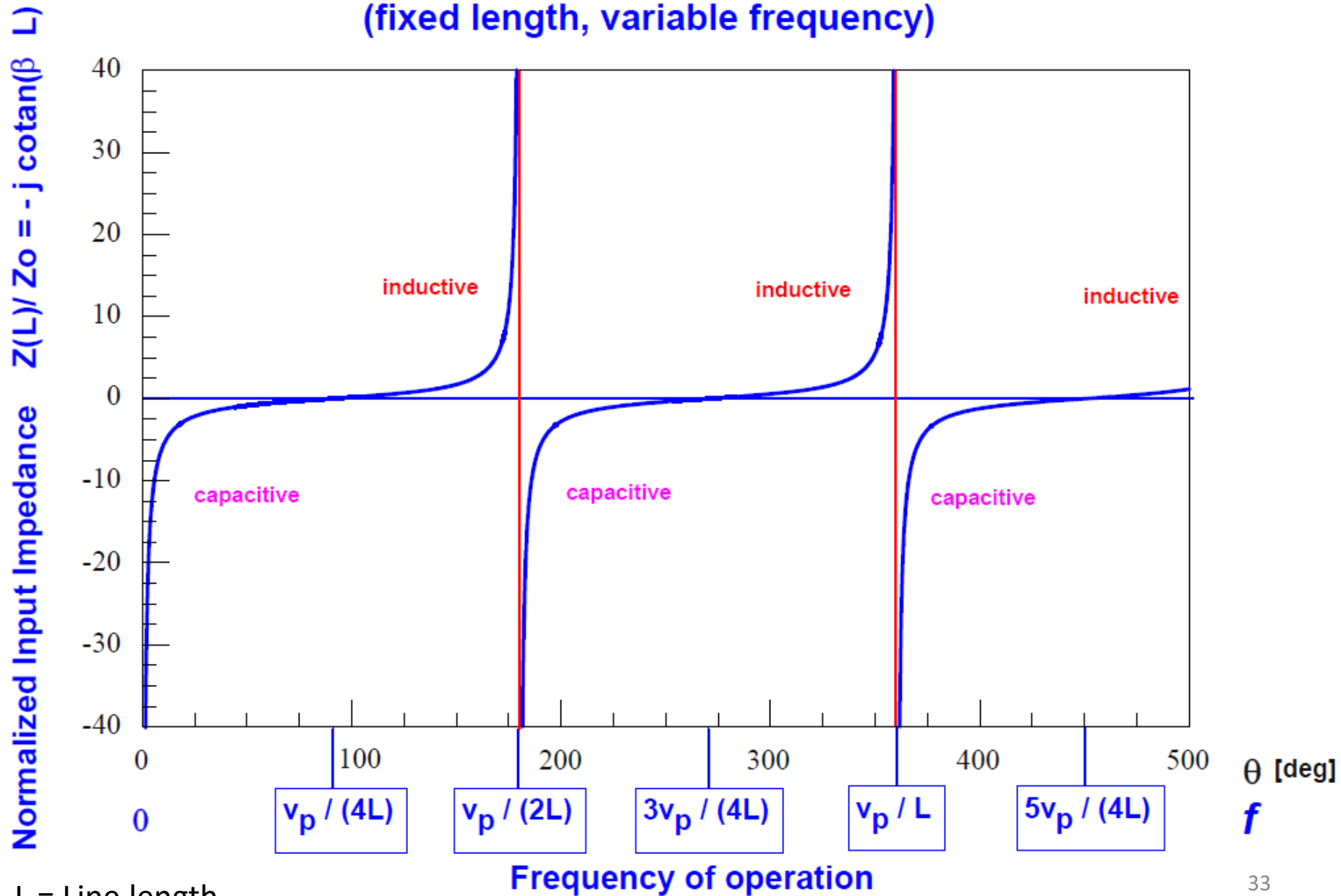Impedance of an open circuited transmission line (fixed length, variable frequency)



L = Line length

You can also use

$$Y_o \equiv \frac{1}{Z_o} \quad \text{Characteristic admittance.}$$

Short circuited line

Input Impedance

$$Z(l) = jZ_o \tan(\beta l)$$


Input Admittance

$$Y(l) = \frac{1}{Z(l)} = \frac{1}{jZ_o \tan(\beta l)} = -jY_o \cot(\beta l)$$

Resonant circuits

$$\omega = \frac{1}{\sqrt{LC}} \equiv \omega_0$$


Series

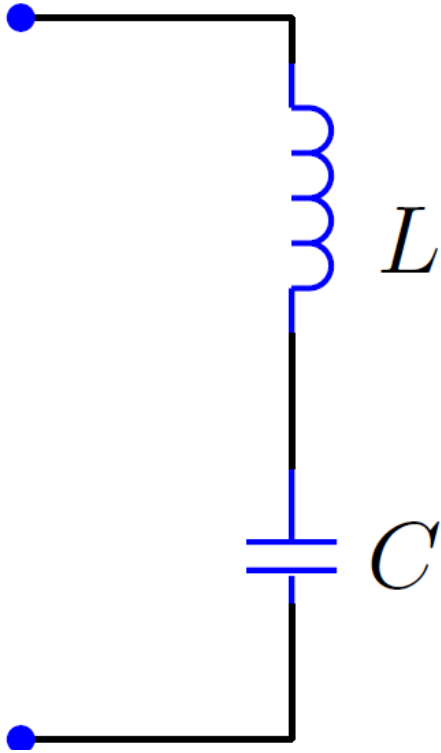

$$Z_s = j\left(\omega L - \frac{1}{\omega C}\right)$$

short circuit at resonance


Parallel

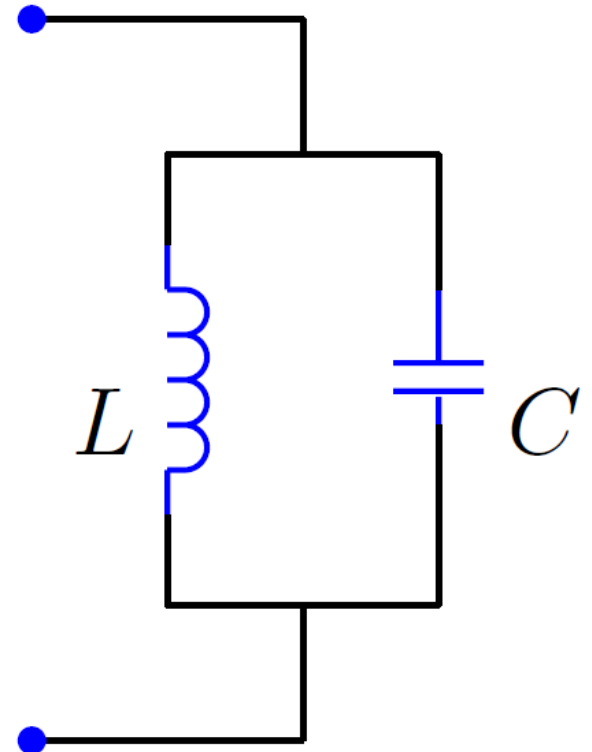

$$Y_p = j\left(\omega C - \frac{1}{\omega L}\right)$$

open circuit at resonance

Resonant circuits

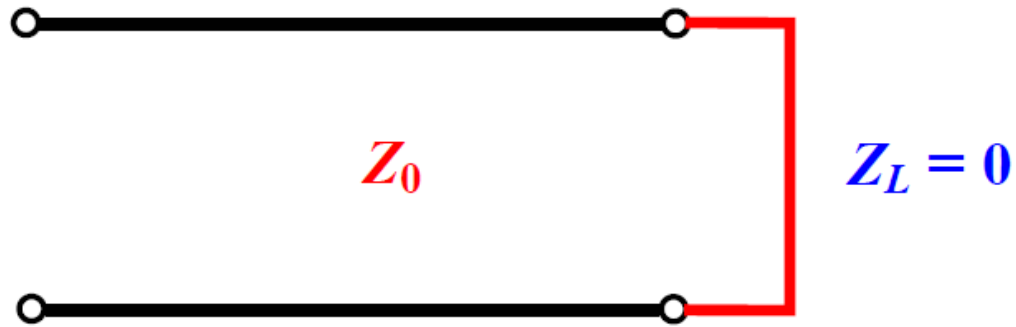

A short-circuited line *stub* is equivalent to an open circuit when the length is an odd multiple of $\lambda/4$ with resonant frequencies


$$f = \frac{v}{2\ell} \left(\frac{1}{2} + n \right) \text{ for } n = 0, 1, 2, 3, \dots$$

A short-circuited *stub* is equivalent to a short circuit when the length is an even multiple of $\lambda/4$ (integer number of $\lambda/2$) with resonant frequencies


$$f = \frac{v}{2\ell} n \text{ for } n = 1, 2, 3, \dots$$

You can build circuits with short TL stubs as reactive elements


Series network:

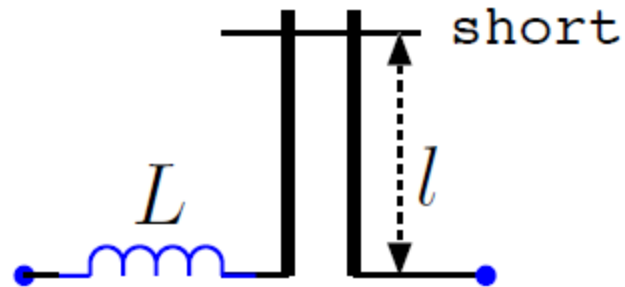

Parallel network:

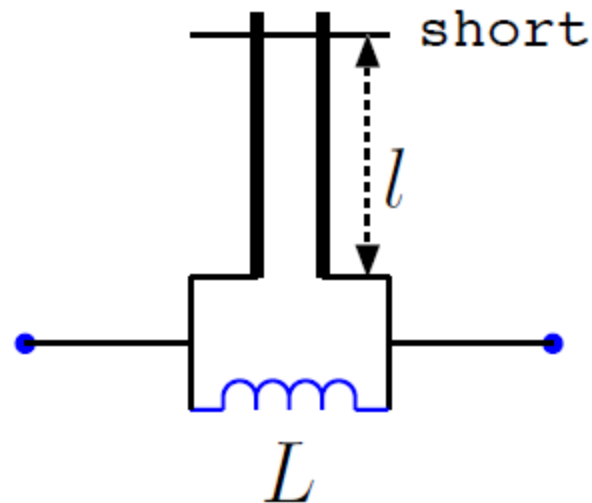

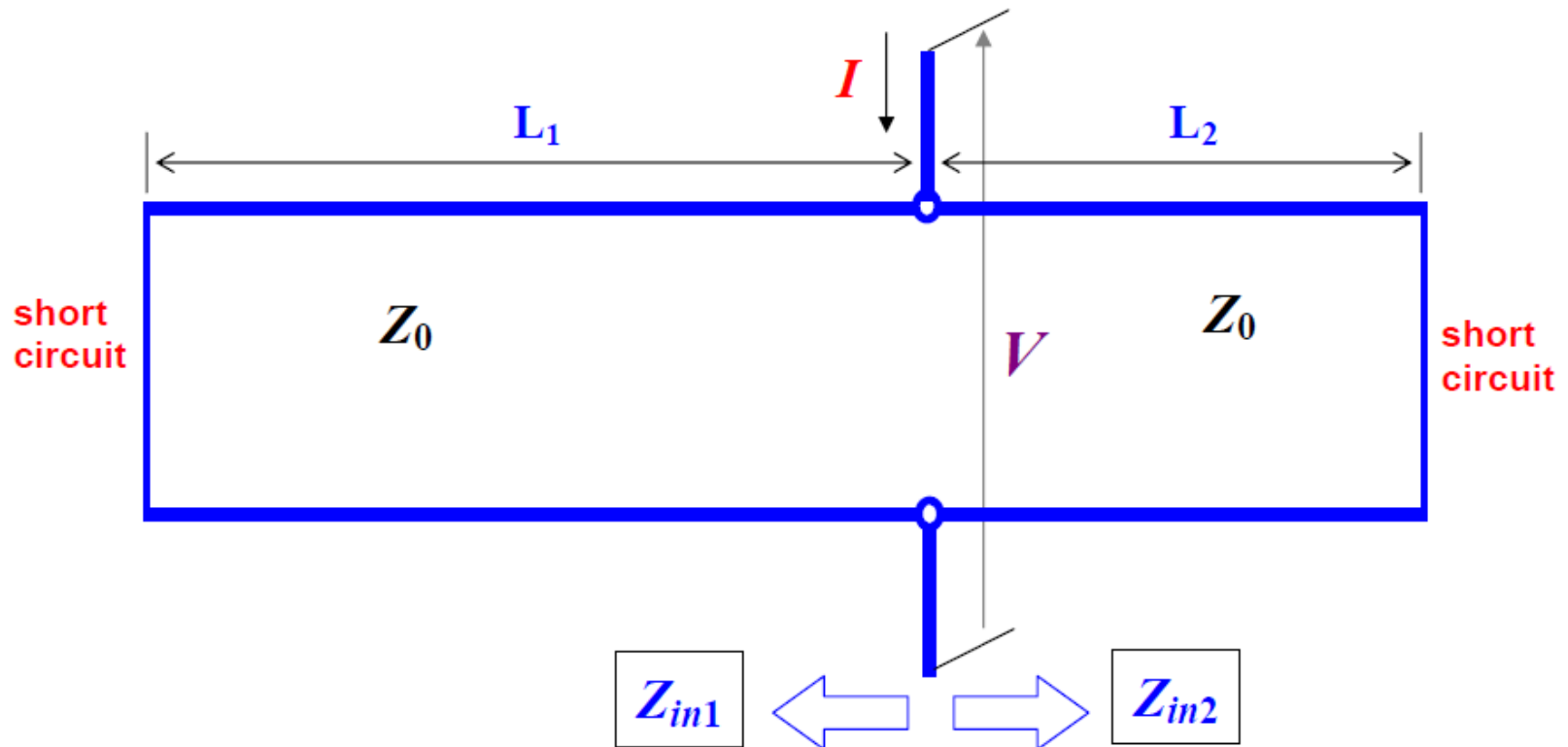It is possible to realize **resonant circuits** by using **transmission lines** as reactive elements. For instance, consider the circuit below realized with lines having the same characteristic impedance:



$$Z_{in1} = jZ_0 \tan(\beta L_1)$$

$$Z_{in2} = jZ_0 \tan(\beta L_2)$$

The circuit is **resonant** if L_1 and L_2 are chosen such that an inductance and a capacitance are realized.

A **resonance condition** is established when the total input impedance of the parallel circuit is **infinite** or, equivalently, when the input admittance of the parallel circuit is **zero**

$$\frac{1}{jZ_0 \tan(\beta_r L_1)} + \frac{1}{jZ_0 \tan(\beta_r L_2)} = 0$$

or

$$\tan\left(\frac{\omega_r L_1}{v_p}\right) = -\tan\left(\frac{\omega_r L_2}{v_p}\right) \quad \text{with} \quad \beta_r = \frac{2\pi}{\lambda_r} = \frac{\omega_r}{v_p}$$

Since the tangent is a periodic function, there is a multiplicity of possible **resonant angular frequencies** ω_r that satisfy the condition above. The values can be found by using a **numerical** procedure to solve the transcendental equation above.