

ECE 329 – Fall 2021

Prof. Ravaioli – Office: 2062 ECEB

Lecture 34-35

Lecture 34-35 – Outline

- **General properties of transmission lines**
- **Relationship between reflection coefficient and impedance**
- **Graphical representation of impedance in the domain of the reflection coefficient: Smith chart**
- **Fundamental operations on the Smith chart**
- **Examples of Smith chart applications**

Reading assignment

Prof. Kudeki's ECE 329 Lecture Notes on Fields and Waves:

34) Line impedance, generalized reflection coefficient, Smith Chart

35) Smith Chart examples

SUMMARY – $\lambda/2$ transmission line

$$V_{in} = -V_L$$

$$I_{in} = -I_L$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{-V_L}{-I_L} = Z_L$$

SUMMARY – $\lambda/4$ transmission line

$$V_{in} = j I_L Z_0 \quad \longrightarrow \quad I_L = -j \frac{V_{in}}{Z_0}$$

$$I_{in} = j \frac{V_L}{Z_0}$$

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{j I_L Z_0}{j V_L / Z_0} = \frac{Z_0^2}{V_L / I_L} = \frac{Z_0^2}{Z_L}$$

impedance transformation of a $\lambda/4$ transformer

Example

$$Z_L = 100 \Omega$$

$$l = 0.75\lambda$$

$$Z_o = 50 \Omega$$

$$V_g = j10 \text{ V}$$

$$Z_g = 25 \Omega$$

Determine V_L and I_L

$$Z_{in} = \frac{Z_o^2}{Z(0.5\lambda)} = \frac{50^2}{100} = 25 \Omega$$

same as load

Voltage divider

$$V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} = j10 \frac{25}{25 + 25} = j5 \text{ V}$$

Example

$$Z_L = 100 \Omega \quad l = 0.75\lambda$$

$$Z_o = 50 \Omega \quad V_g = j10 \text{ V} \quad Z_g = 25 \Omega$$

half-wave transformer rule

$$V(0.25\lambda) = -V_{in} = -j5 \text{ V}$$

which input voltage for final quarter-wave section, and


$$I_L = -j \frac{V(0.25\lambda)}{Z_o} = -j \frac{-j5}{50} = -0.1 \text{ A}$$

$$I_L = -j \frac{V_{in}}{Z_o}$$

from Lecture 33

load voltage
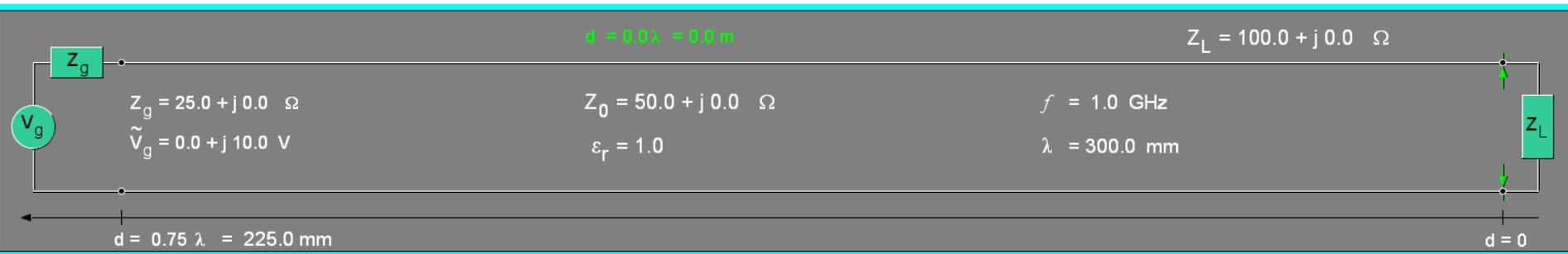
$$V_L = Z_L I_L = (100 \Omega)(-0.1 \text{ A}) = -10 \text{ V}$$



Set Line

Length units: [λ] [m]

Lossless Approximation

Characteristic Impedance $Z_0 =$ [Ω]
 Frequency $f =$ [Hz]
 Relative Permittivity $\epsilon_r =$
 Line Length $l =$ [λ]

Instructions

$Z_L =$ + j [Ω]
 Impedance Admittance

Set Generator

$\tilde{V}_g =$ + j [V]
 $Z_g =$ + j [Ω]

Output

Transmission Line Data 1

Cursor $d = 0.0 \lambda = 0.0 \text{ m}$

Impedance $Z(d) = 100.0 + j 0.0$
 [Ω] $= 100.0 \angle 0.0 \text{ rad}$

Admittance $Y(d) = 0.01 + j 0.0$
 [S] $= 0.01 \angle 0.0 \text{ rad}$



Reflection Coefficient $\Gamma_d = 0.33333333 + j 0.0$
 $= 0.33333333 \angle 0.0 \text{ rad}$
 $= 0.33333333 \angle 0.0^\circ$

Voltage $\tilde{V}(d) = -10.0 + j 0.0$
 [V] $= 10.0 \angle -3.1416 \text{ rad}$



Current $\tilde{I}(d) = -0.1 + j 0.0$
 [A] $= 0.1 \angle -3.1416 \text{ rad}$

Power Flow $P_{av} = 500.0$
 [mW]



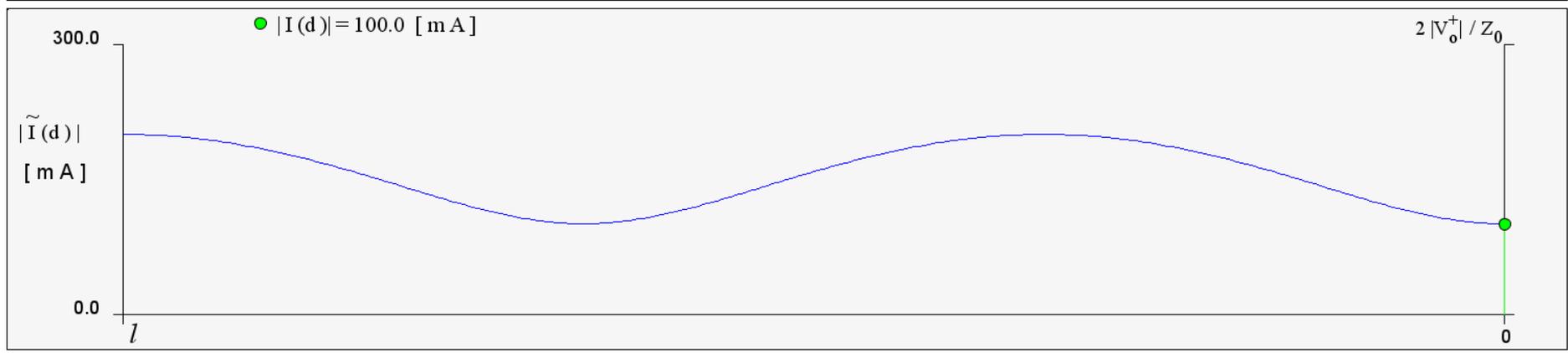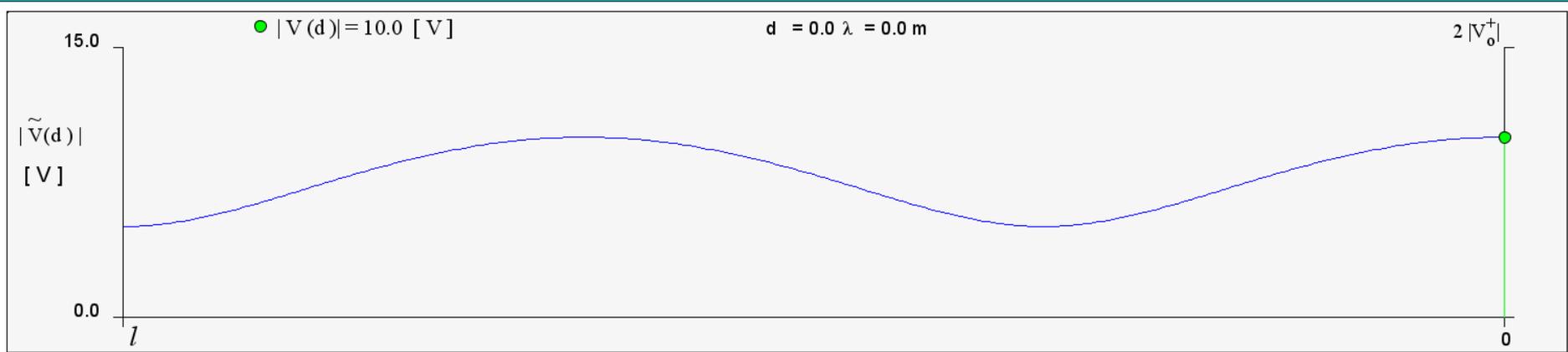


Standing Wave Pattern - |V| & |I|

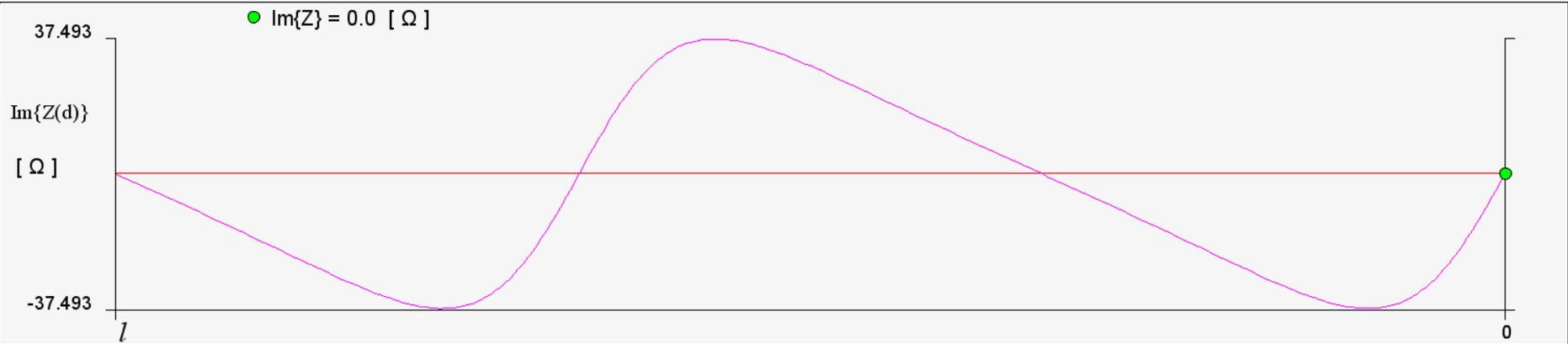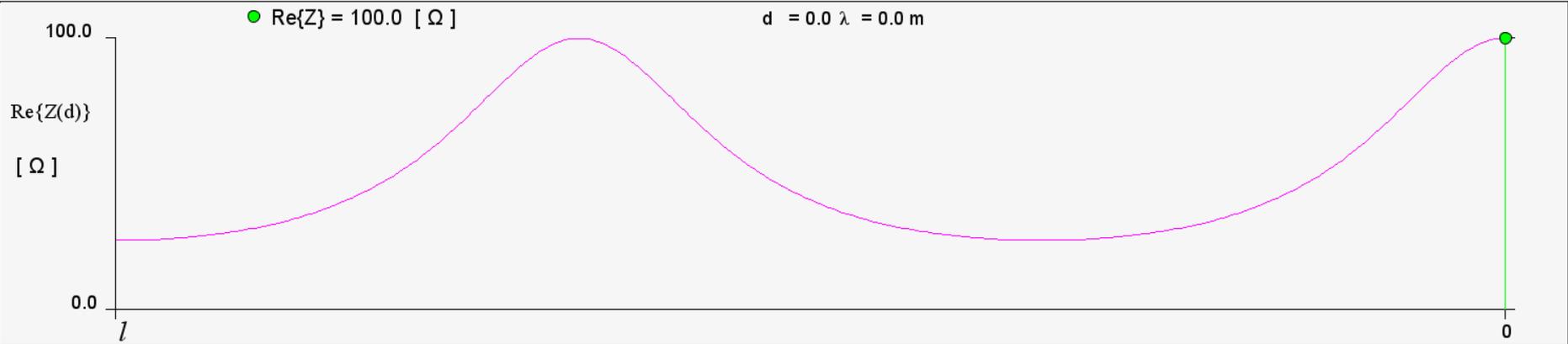

Impedance

$$d = 0.75 \lambda$$


$$d = 0.25 \lambda$$

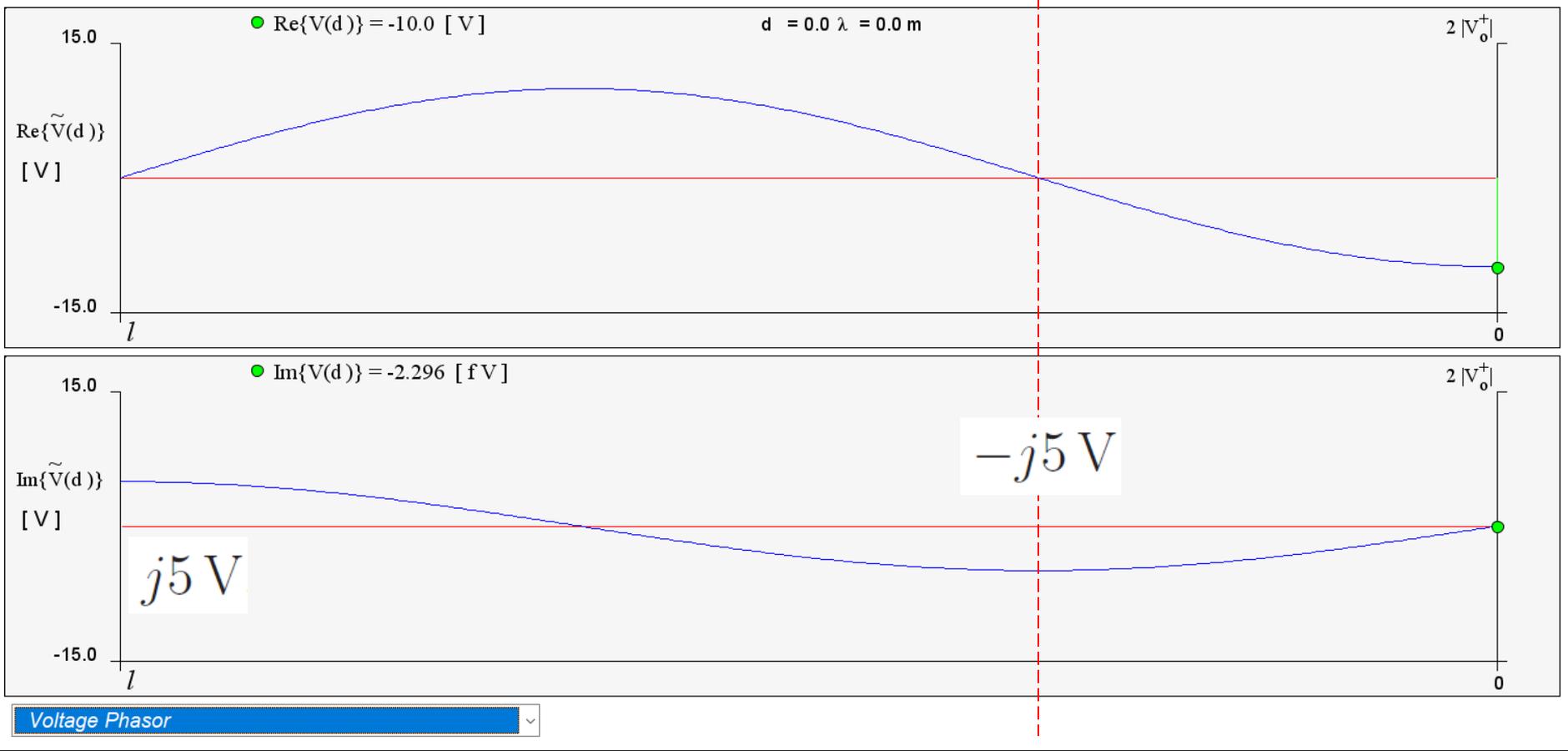

$$d = 0.75 \lambda$$

$$d = 0.5 \lambda$$

$$d = 0.25 \lambda$$

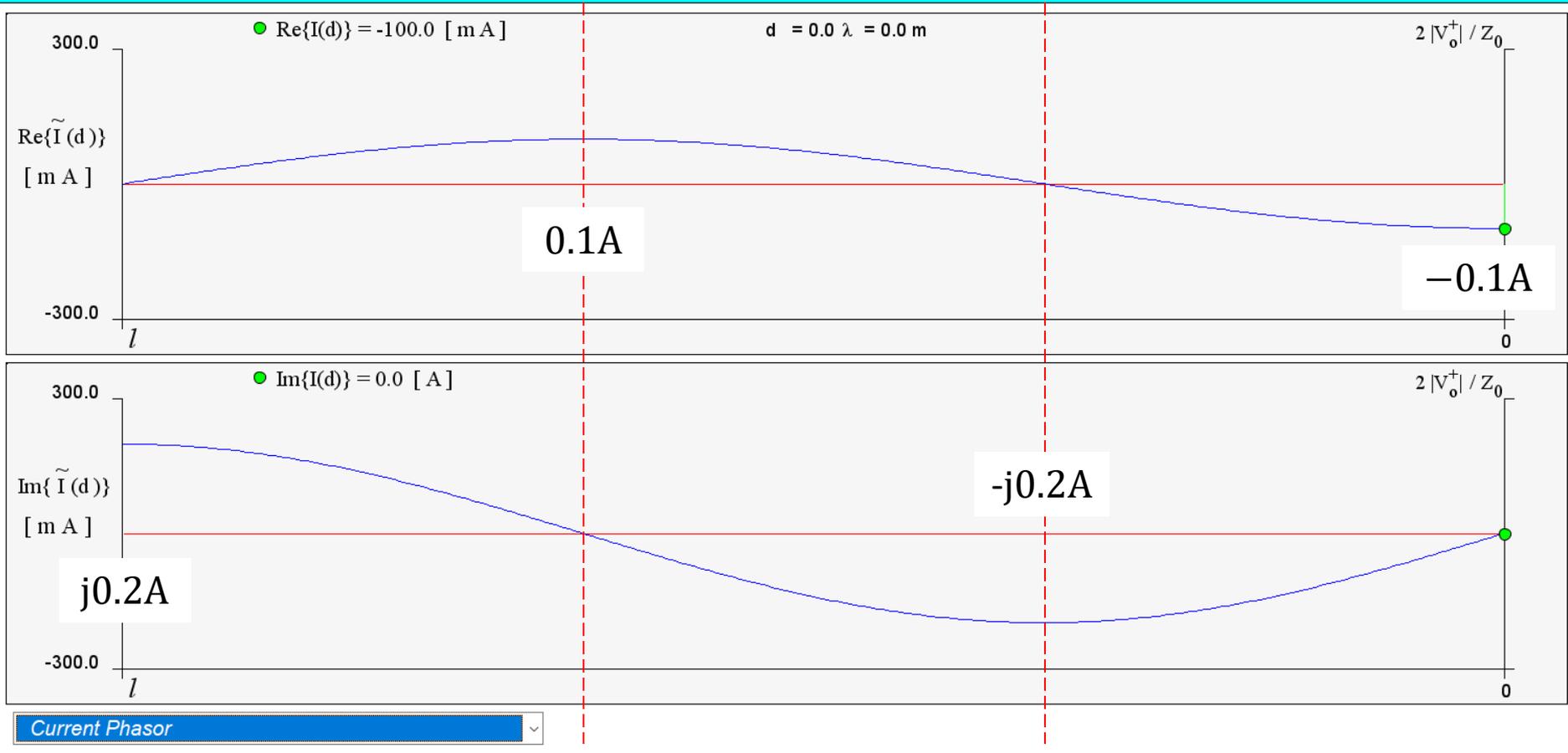

Introduction to the Smith Chart

Once again, we have obtained the following expressions for a TL:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

load reflection coefficient

$$\Gamma(d) = \Gamma_L e^{-2j\beta d}$$

generalized reflection coefficient

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$


line impedance

Can we plot these quantities?


Reflection coefficient is complex (2 coordinates) and impedance is also complex (2 additional coordinates) = this is a 4-dimensional problem.

Introduction to the Smith Chart

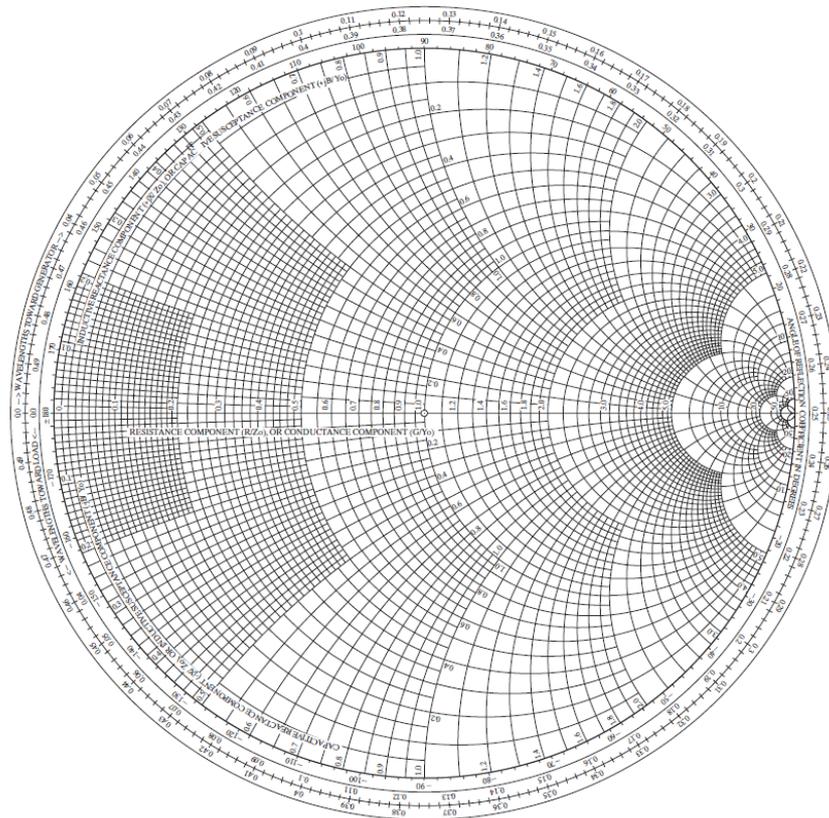The Smith chart is one of the most useful graphical tools for high frequency circuit applications. The chart provides a clever way to visualize complex functions and it continues to endure popularity, decades after its original conception.



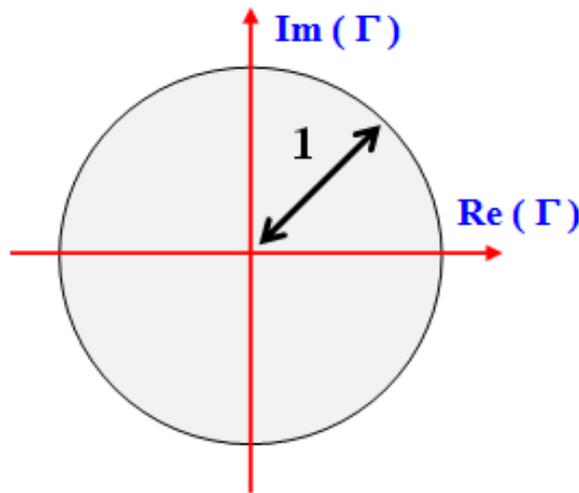
From a mathematical point of view, the Smith chart is a 4-D representation of all possible complex impedances with respect to coordinates defined by the complex reflection coefficient.




The domain of definition of the reflection coefficient for a loss-less line is a circle of unitary radius in the complex plane. This is also the domain of the Smith chart.

For a general lossy line we may have $|\Gamma| > 1$, due to the complex characteristic impedance, thus requiring an extended Smith chart.

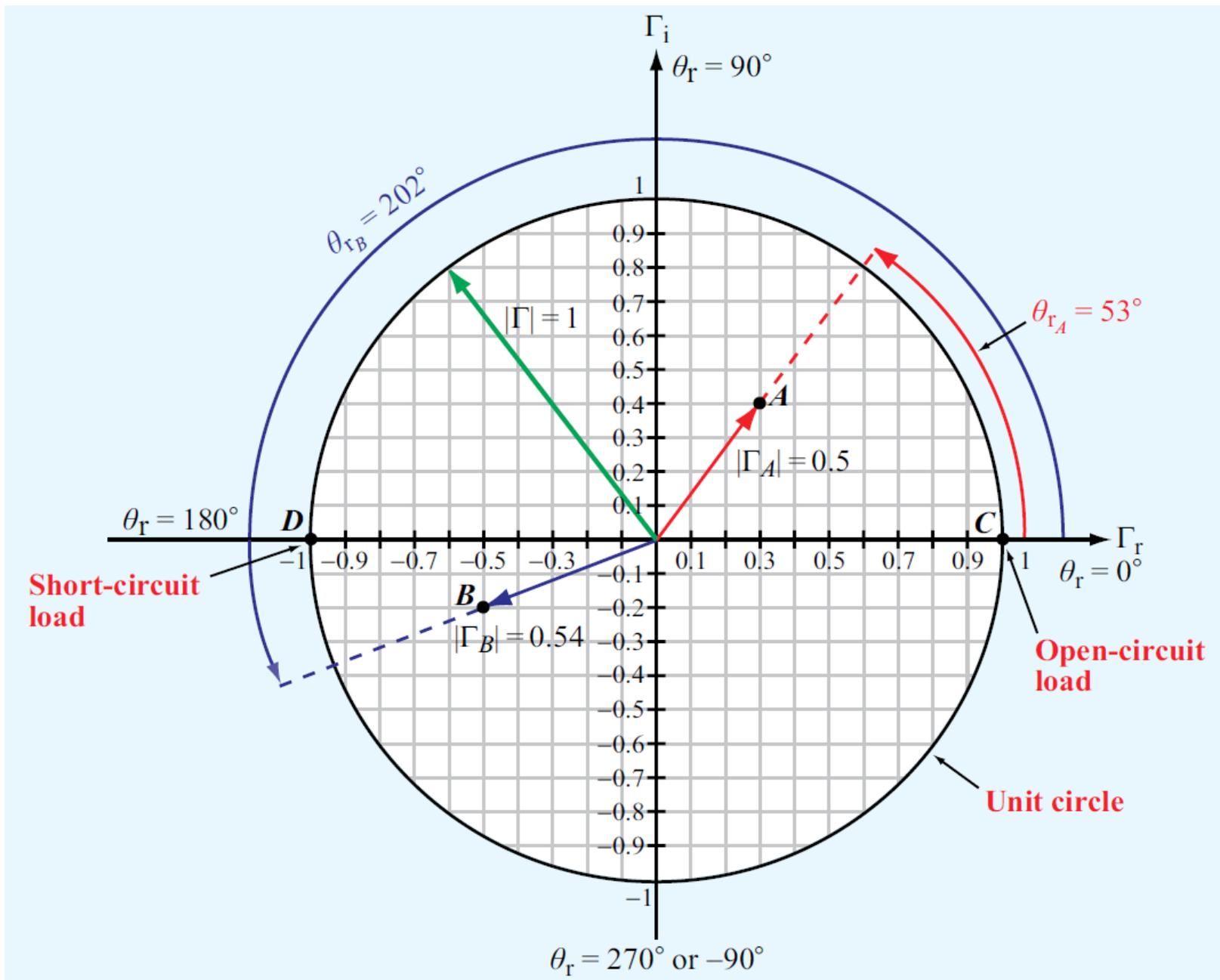Domain of the Reflection Coefficient in a loss-less line



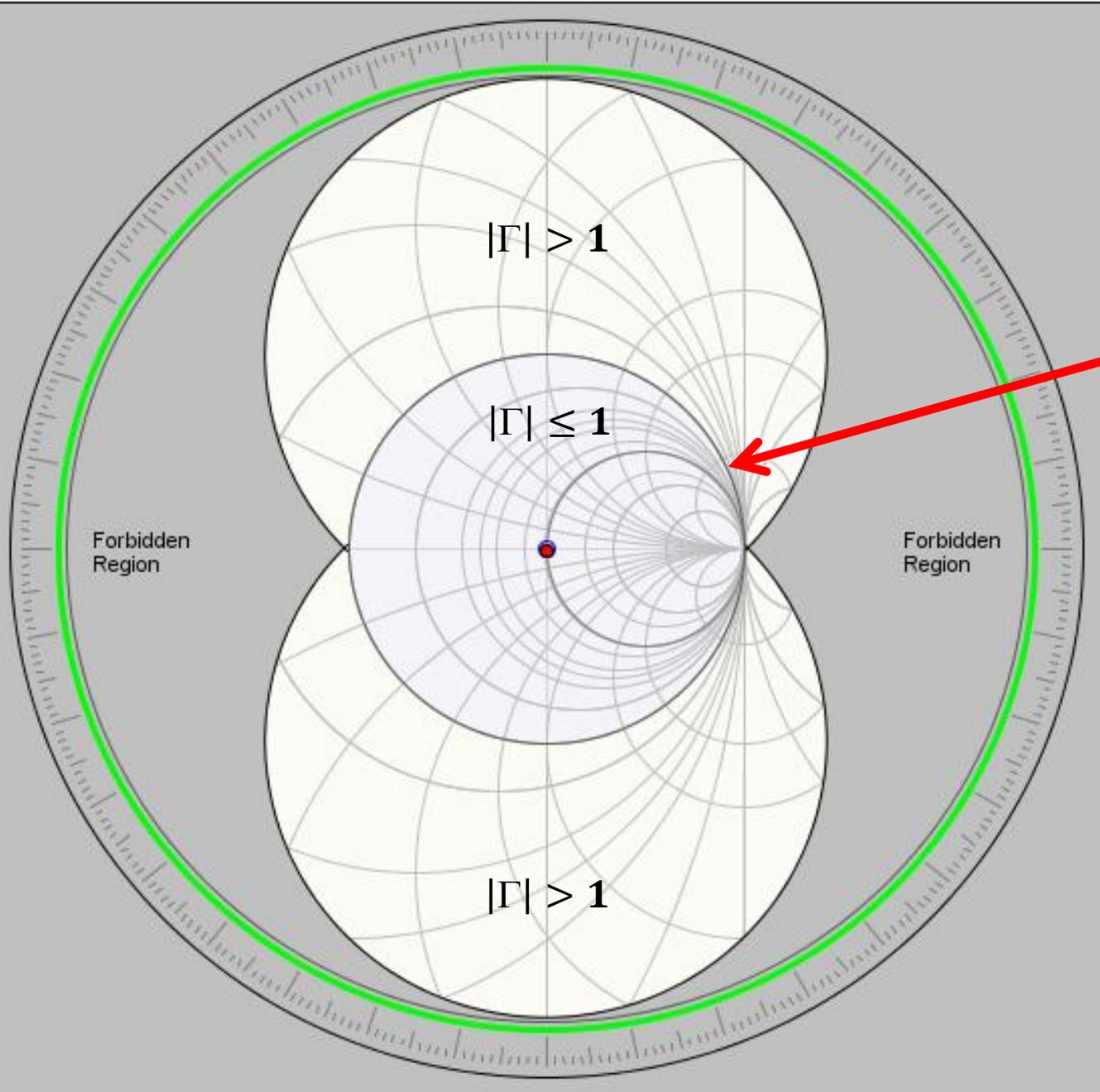EXTRA – This is what the extended Smith chart for lossy lines would look like



**Lossless line
Smith Chart**

**Use of this extended
chart is actually rare**

The goal of the Smith chart is to identify **all possible impedances** on the domain of existence of the reflection coefficient. To do so, we start from the general definition of **line impedance**

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

This provides the complex function $Z(d) = f\{\text{Re}(\Gamma), \text{Im}(\Gamma)\}$ we wish to plot but the result would apply only to a specific value of Z_0 .

To obtain **universal curves** we introduce the **normalized impedance**

$$z_n(d) = \frac{Z(d)}{Z_0} = \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

The **normalized impedance** is represented on the **Smith chart** by using families of curves that identify the **normalized resistance** r (real part) and the **normalized reactance** x (imaginary part)

$$z_n(d) = \text{Re}(z_n) + j \text{Im}(z_n) = r + jx$$

Let's represent the **reflection coefficient** in terms of its coordinates

$$\Gamma(d) = \text{Re}(\Gamma) + j \text{Im}(\Gamma)$$

Now we can write

$$r + jx = \frac{1 + \text{Re}(\Gamma) + j \text{Im}(\Gamma)}{1 - \text{Re}(\Gamma) - j \text{Im}(\Gamma)} = \frac{1 - \text{Re}^2(\Gamma) - \text{Im}^2(\Gamma) + j2 \text{Im}(\Gamma)}{(1 - \text{Re}(\Gamma))^2 + \text{Im}^2(\Gamma)}$$

The real part gives

$$r = \frac{1 - \operatorname{Re}^2(\Gamma) - \operatorname{Im}^2(\Gamma)}{(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma)}$$

Add a quantity equal to zero

$$r(\operatorname{Re}(\Gamma) - 1)^2 + (\operatorname{Re}^2(\Gamma) - 1) + r\operatorname{Im}^2(\Gamma) + \operatorname{Im}^2(\Gamma) + \underbrace{\frac{1}{1+r} - \frac{1}{1+r}}_{=0} = 0$$

$$(1+r) \left[\operatorname{Re}^2(\Gamma) - 2\operatorname{Re}(\Gamma) \frac{r}{1+r} + \frac{r^2}{(1+r)^2} \right] + (1+r)\operatorname{Im}^2(\Gamma) = \frac{1}{1+r}$$


$$\Rightarrow \left[\operatorname{Re}(\Gamma) - \frac{r}{1+r} \right]^2 + \operatorname{Im}^2(\Gamma) = \left(\frac{1}{1+r} \right)^2$$

Equation of a circle

The result for the *real part* shows that all the possible impedances with a given normalized resistance r are found on a *circle* with

$$\text{Center} = \left\{ \frac{r}{1+r}, 0 \right\} \quad \text{Radius} = \frac{1}{1+r}$$

defining a family of circles in the domain $|\Gamma| \leq 1$.

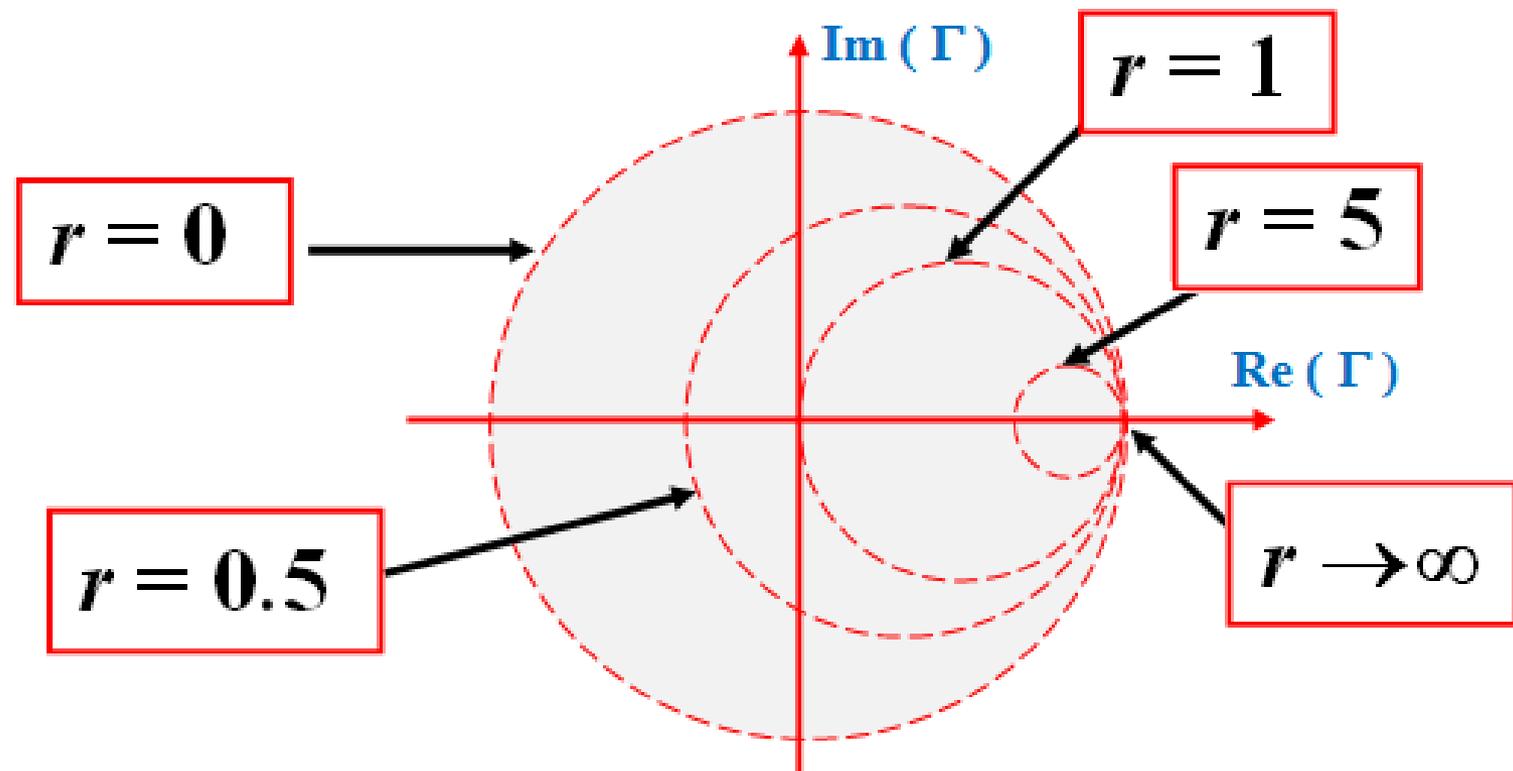

The imaginary part gives

$$x = \frac{2\operatorname{Im}(\Gamma)}{(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma)}$$

Multiply by x and add a quantity equal to zero

$$x^2 \left[(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma) \right] - 2x \operatorname{Im}(\Gamma) + \underbrace{1 - 1}_{= 0} = 0$$

$$(1 - \operatorname{Re}(\Gamma))^2 + \left[\operatorname{Im}^2(\Gamma) - \frac{2}{x} \operatorname{Im}(\Gamma) + \frac{1}{x^2} \right] = \frac{1}{x^2}$$


$$\Rightarrow (\operatorname{Re}(\Gamma) - 1)^2 + \left[\operatorname{Im}(\Gamma) - \frac{1}{x} \right]^2 = \frac{1}{x^2}$$

Equation of a circle


The result for the *imaginary part* shows that all the possible impedances with a given normalized reactance x are on a *circle* with

$$\text{Center} = \left\{ 1, \frac{1}{x} \right\} \qquad \text{Radius} = \frac{1}{x}$$

defining a family of arcs in the domain $|\Gamma| \leq 1$.

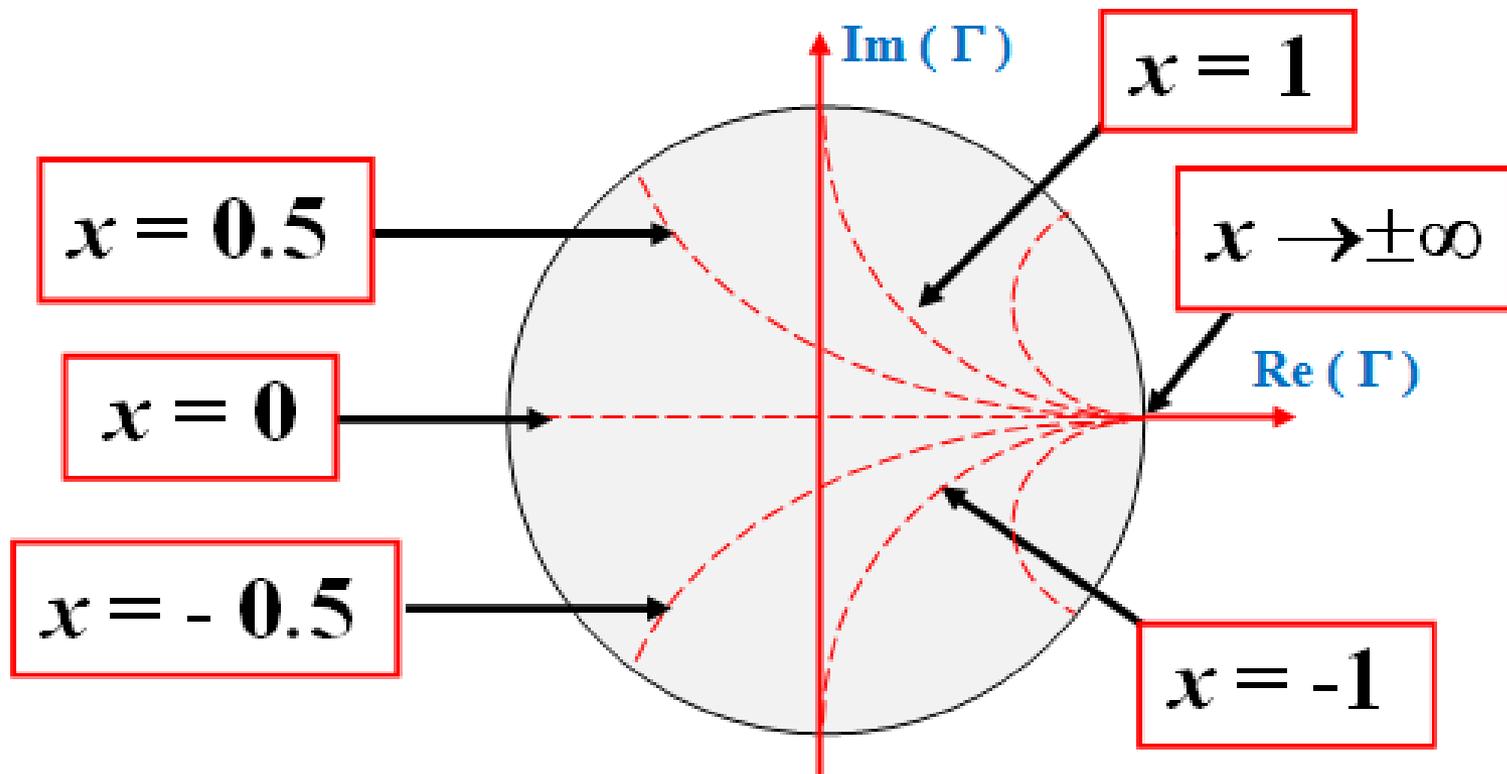

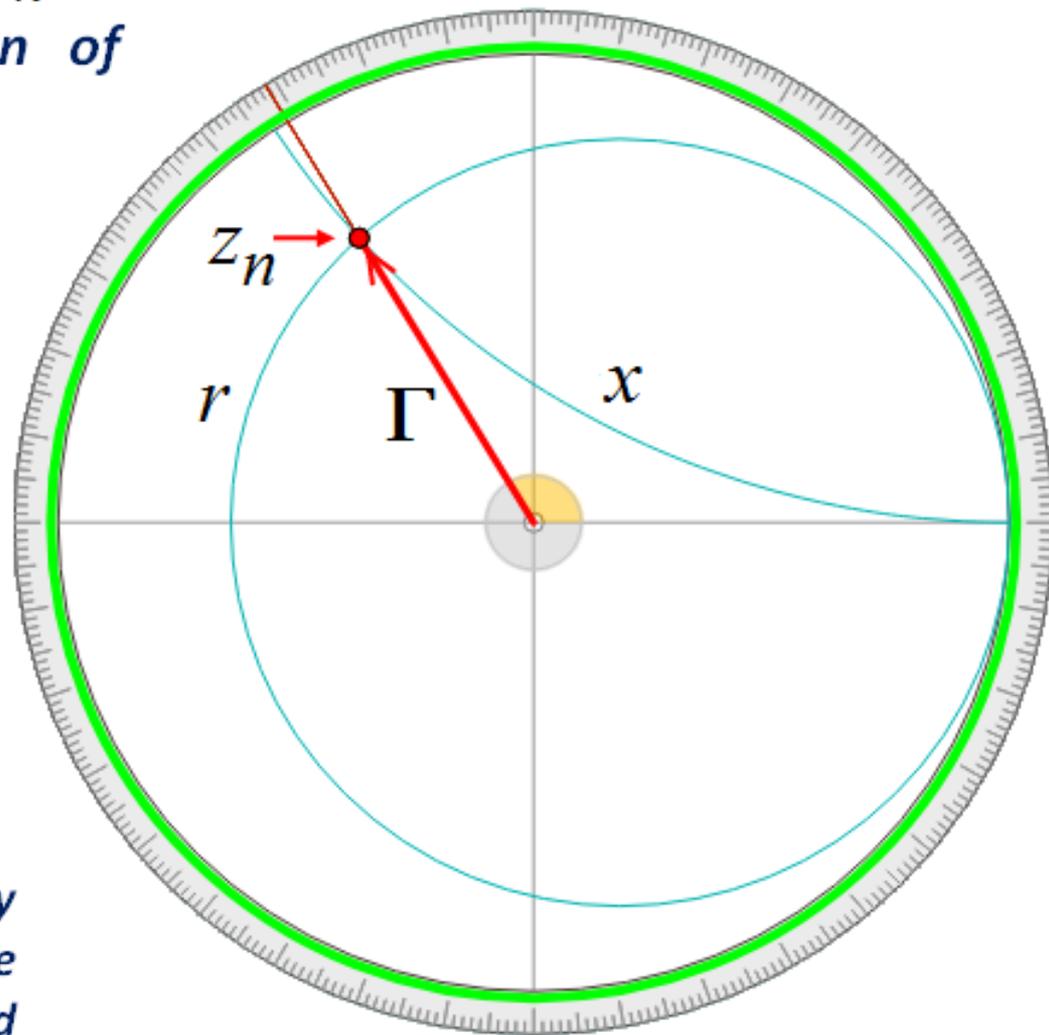There is one-to-one correspondence between **reflection coefficient** and **impedance**. Any value of z_n is identified by the intersection of two curves.




The Smith Chart is assembled by drawing a number of representative curves for normalized resistance and normalized reactance.

Smith Chart for Impedances

Positive (inductive) reactance

Negative (capacitive) reactance

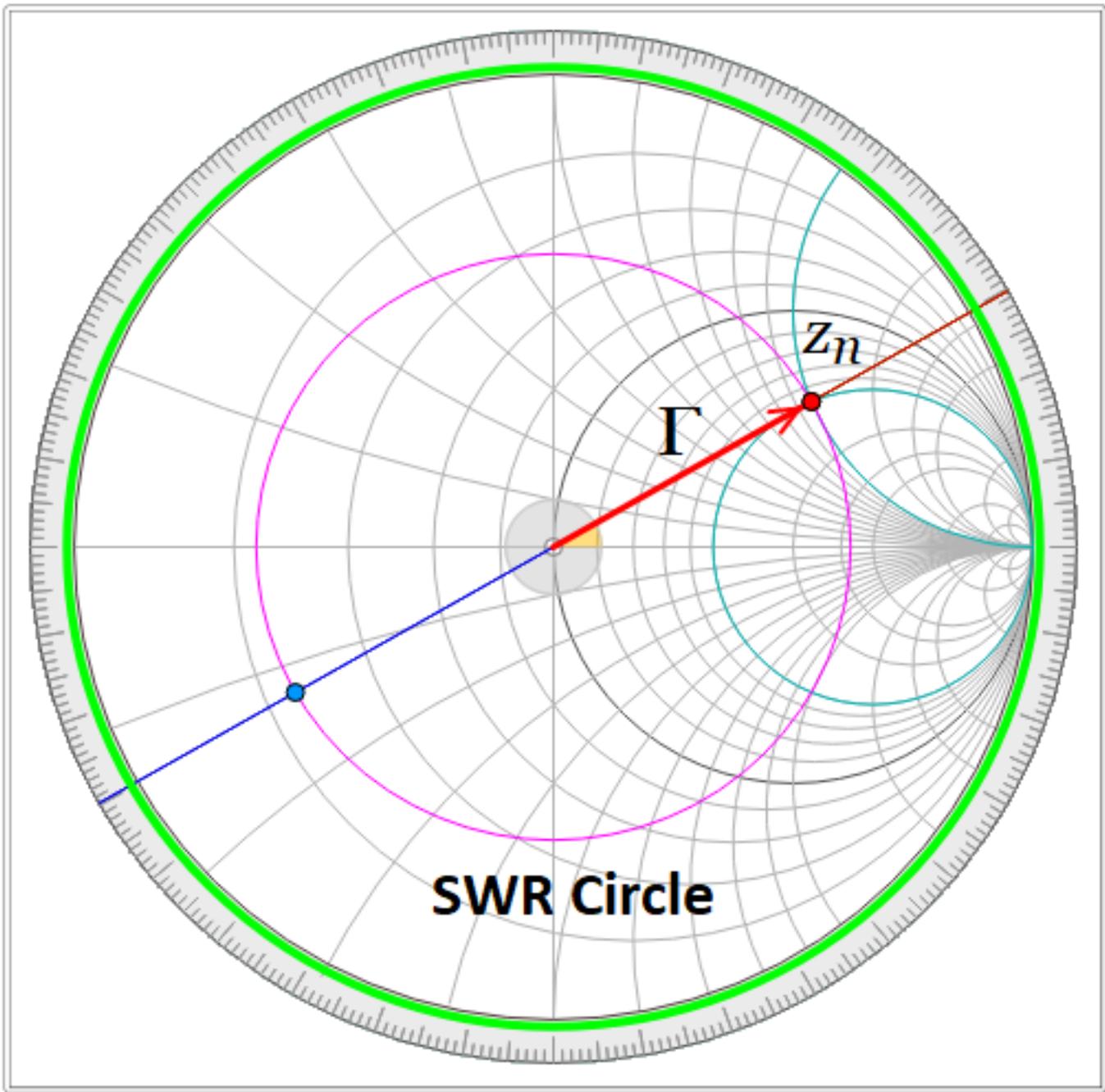



The five basic techniques of the Smith Chart

- 1) Given a reflection coefficient, obtain the corresponding impedance
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) Given an impedance find the corresponding admittance


The five basic techniques of the Smith Chart

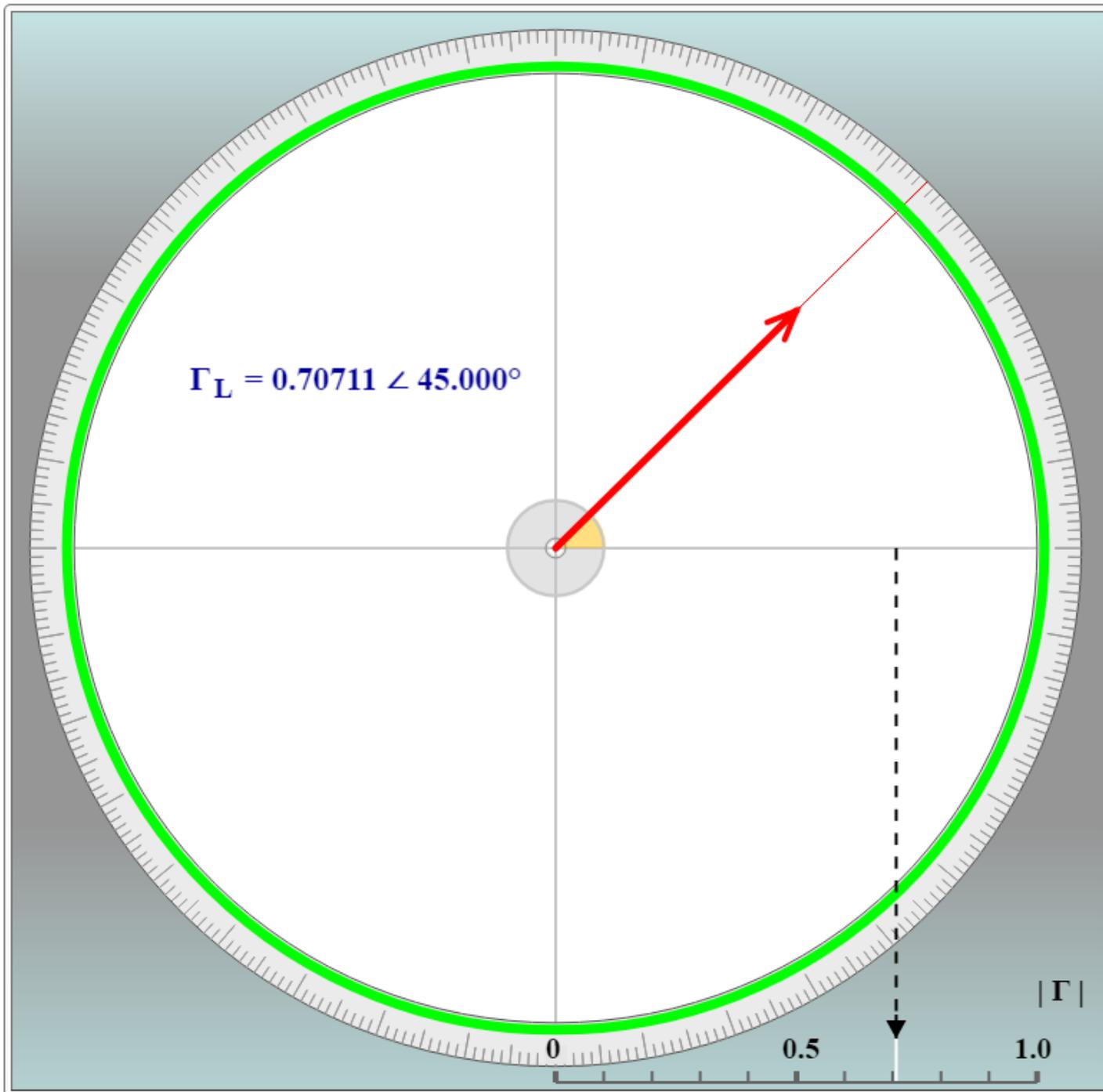- 1) Given a reflection coefficient, obtain the corresponding impedance**
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) Given an impedance find the corresponding admittance



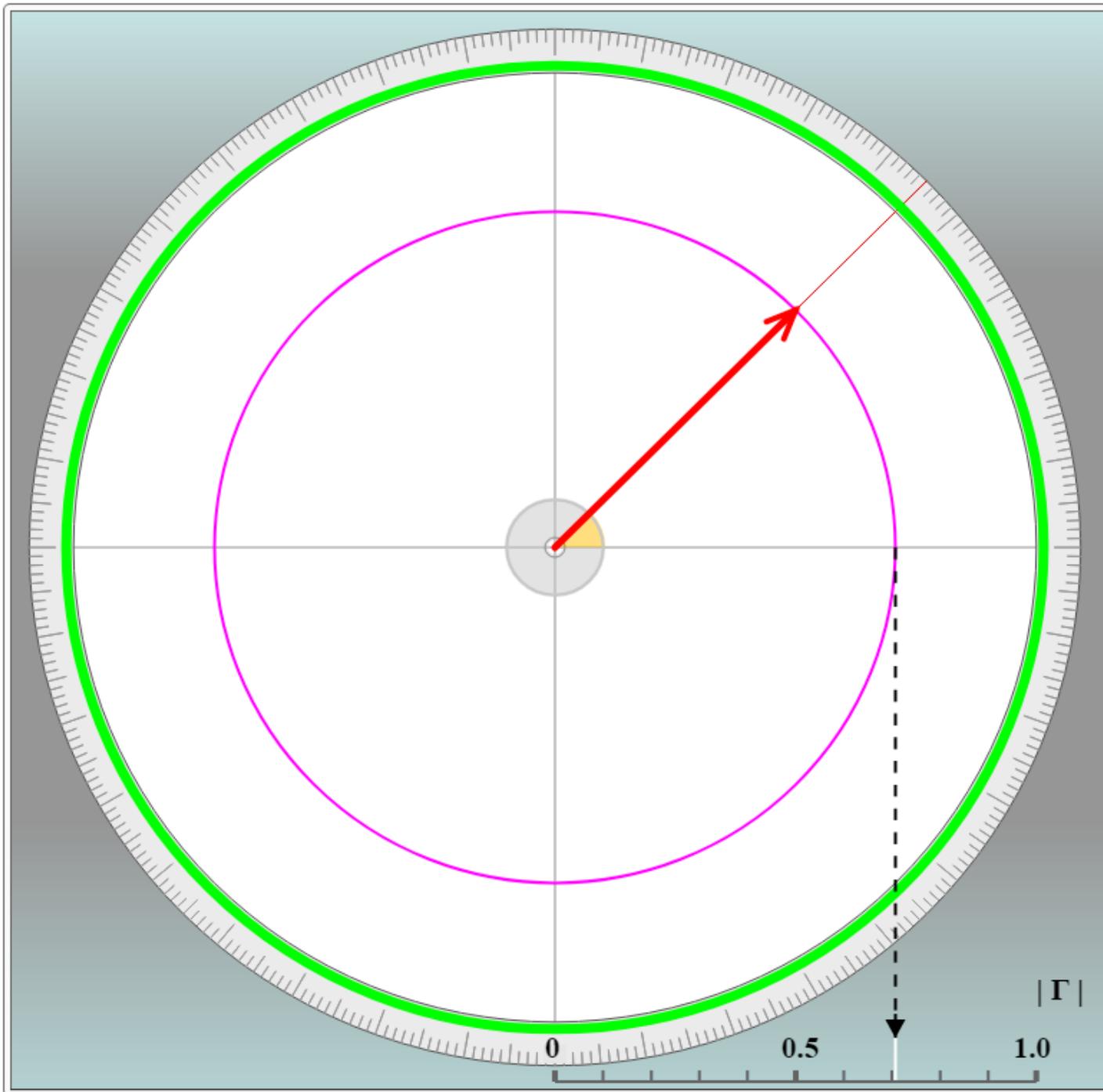


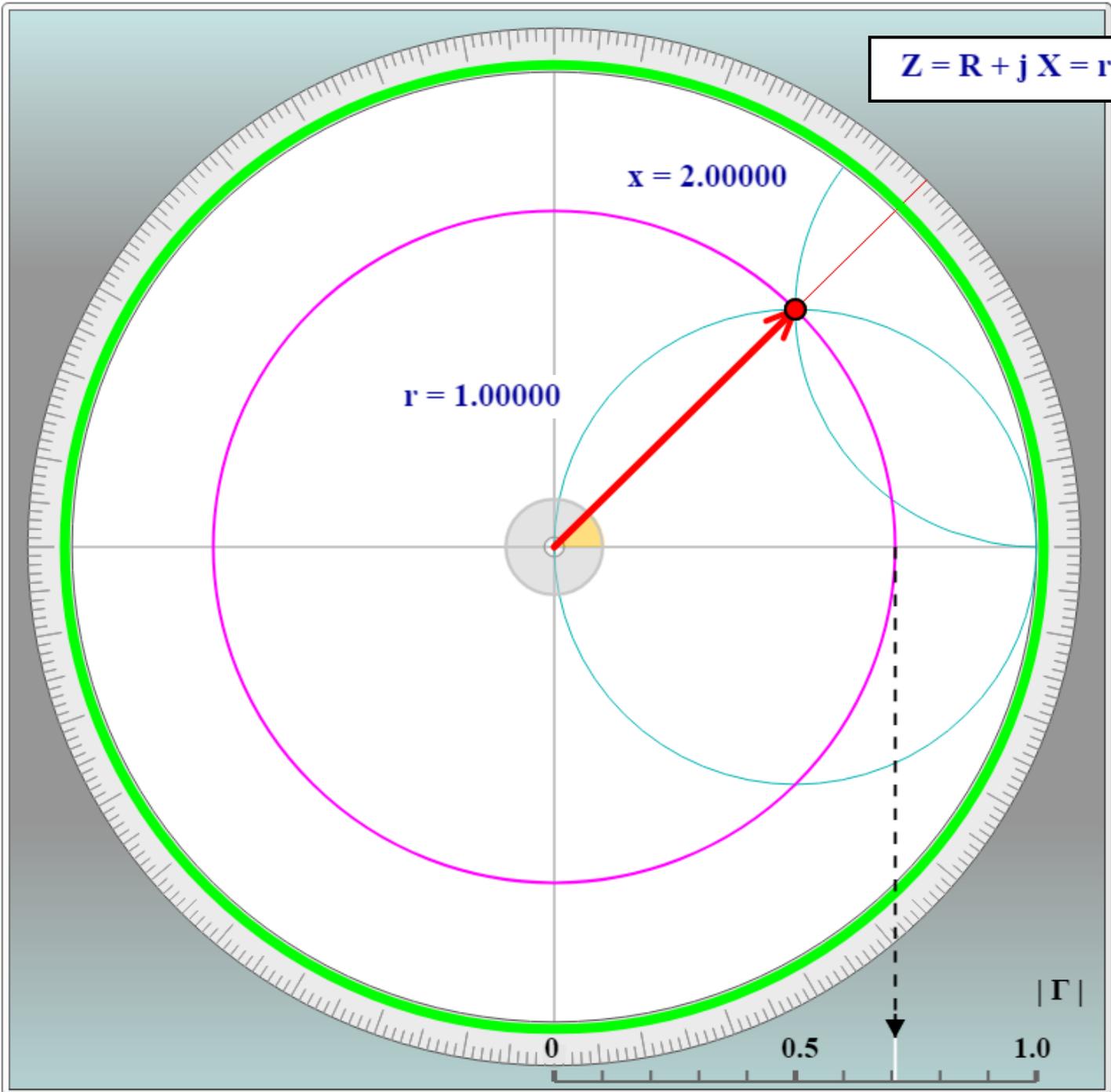
$$Z = R + jX = r \cdot Z_0 + jx \cdot Z_0$$



The five basic techniques of the Smith Chart

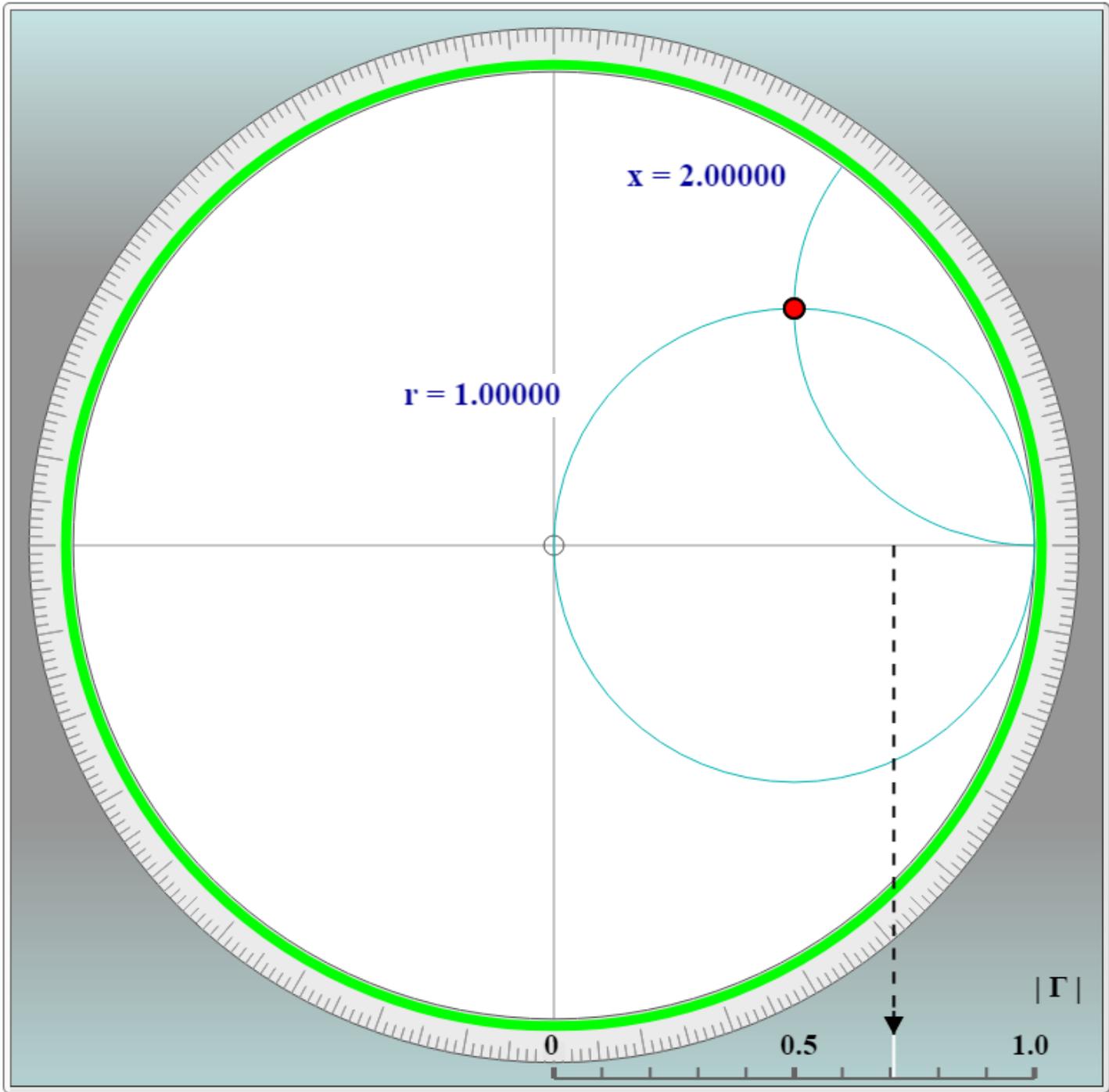- 1) Given an impedance, obtain the corresponding reflection coefficient**
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) Given an impedance find the corresponding admittance



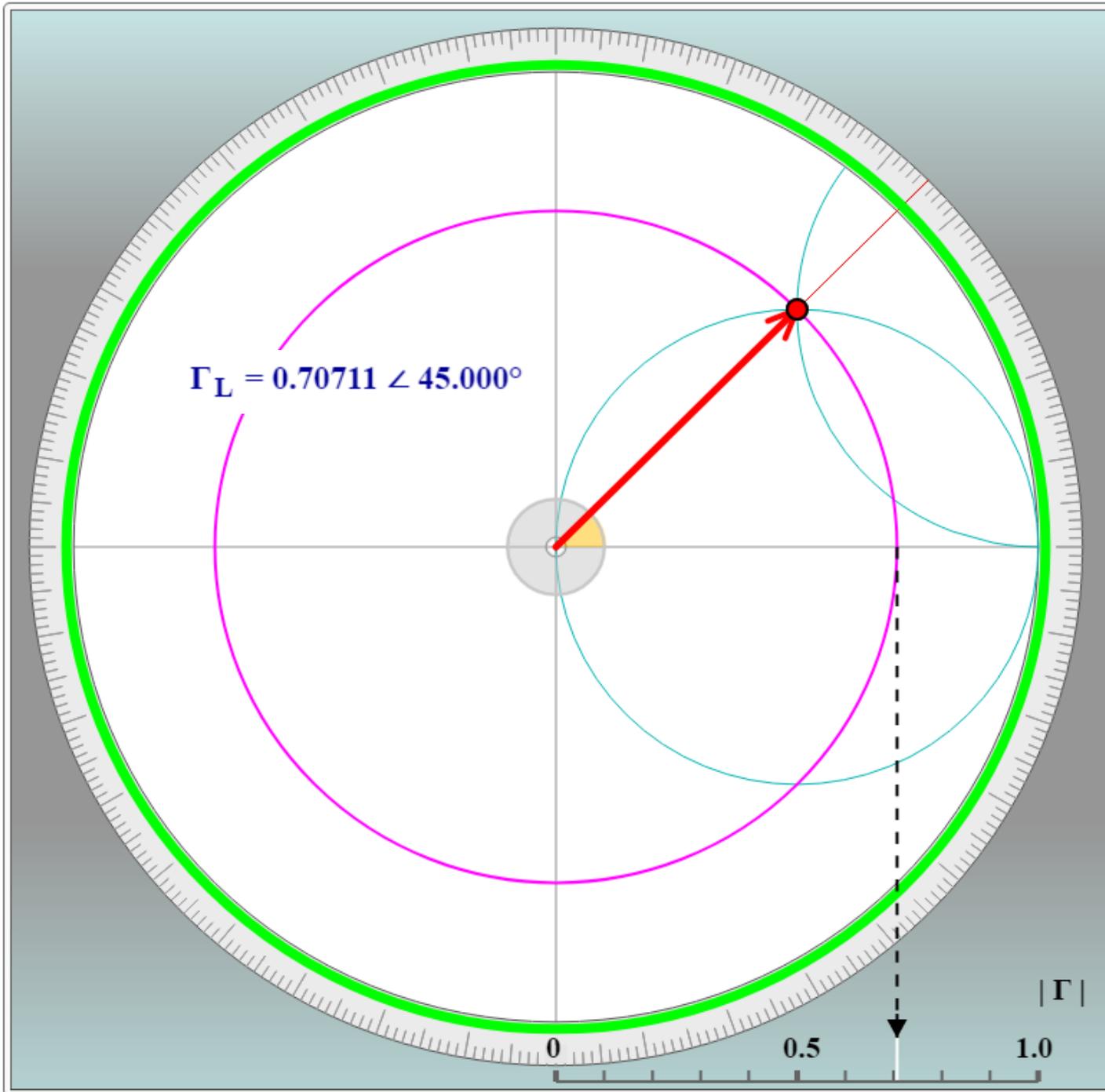


The five basic techniques of the Smith Chart


- 1) Given a reflection coefficient, obtain the corresponding impedance
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line**
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) Given an impedance find the corresponding admittance

$$Z_L = 100.000 + j 100.000 \Omega$$

$$Z_0 = 50.00 \Omega$$

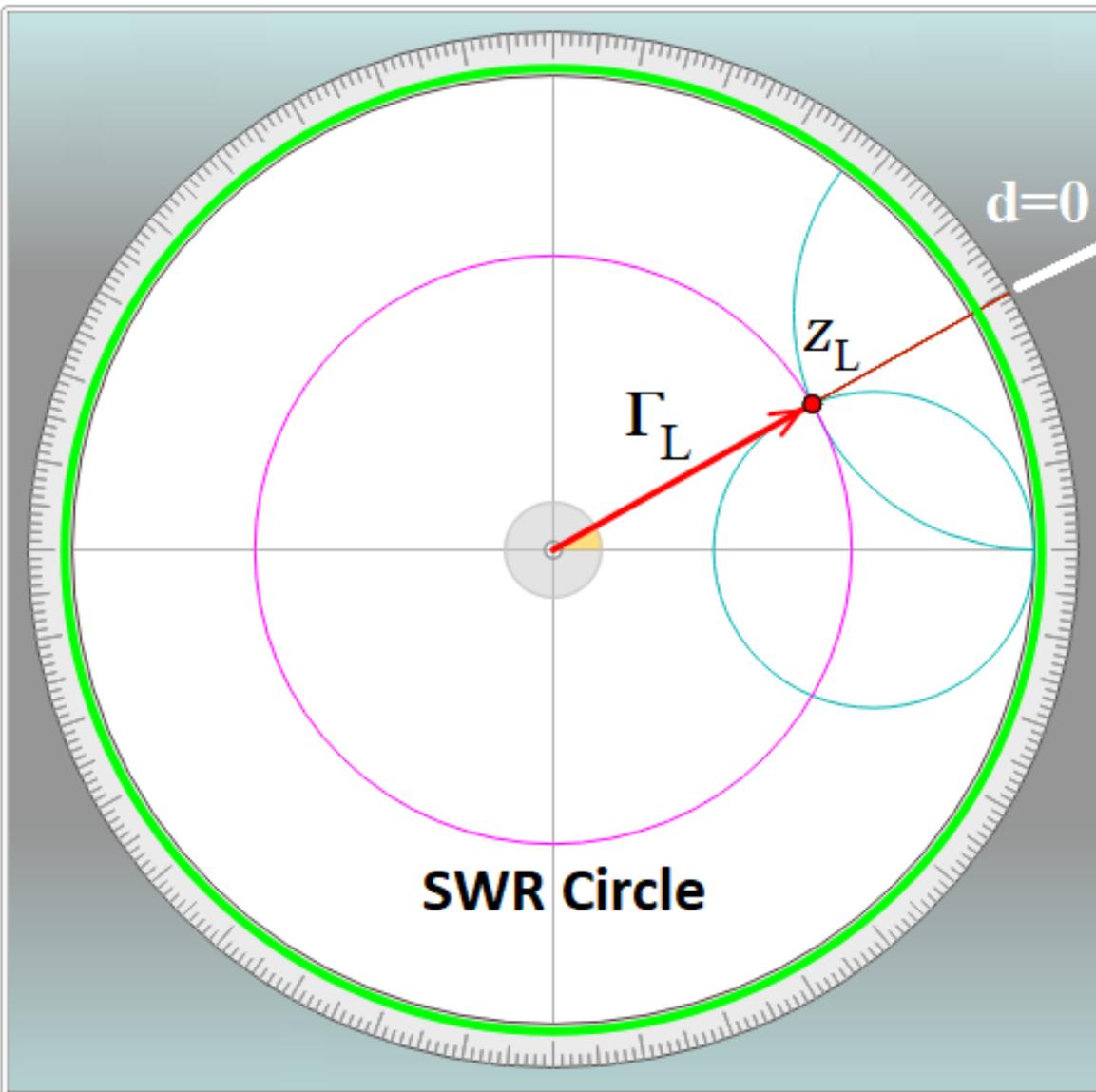

*Space reference for
load location*

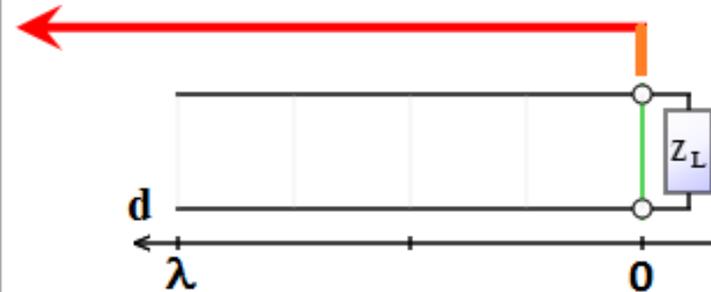

$$Z(0) = 100.000 + j 100.000 \Omega$$

$$z(0) = 2.000 + j 2.000$$

$$\Gamma(0) = 0.62017 \angle 29.745^\circ$$

$$d = 0.10000 \lambda$$

$$\Delta \theta = -2 \beta d = -4\pi d / \lambda = -72.000^\circ$$

$$Z_L = 100.000 + j 100.000 \Omega$$

$$Z_0 = 50.00 \Omega$$


$$Z(d) = 65.949 - j 89.383 \Omega$$

$$z(d) = 1.319 - j 1.788$$

$$\Gamma(d) = 0.62017 \angle 317.745^\circ$$

$$d = 0.10000 \lambda$$

when **d** moves from
load to generator

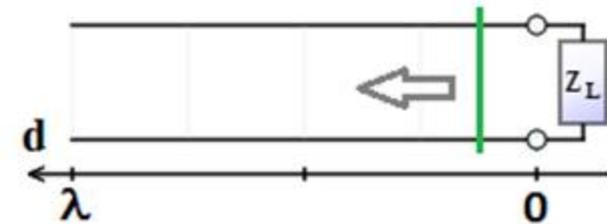


Γ rotates clockwise
on SWR Circle

angle of
rotation

$$\Delta\theta = \begin{matrix} \text{CW} \\ \downarrow \\ - \\ \uparrow \\ \text{CCW} \end{matrix} \frac{4\pi}{\lambda} d$$
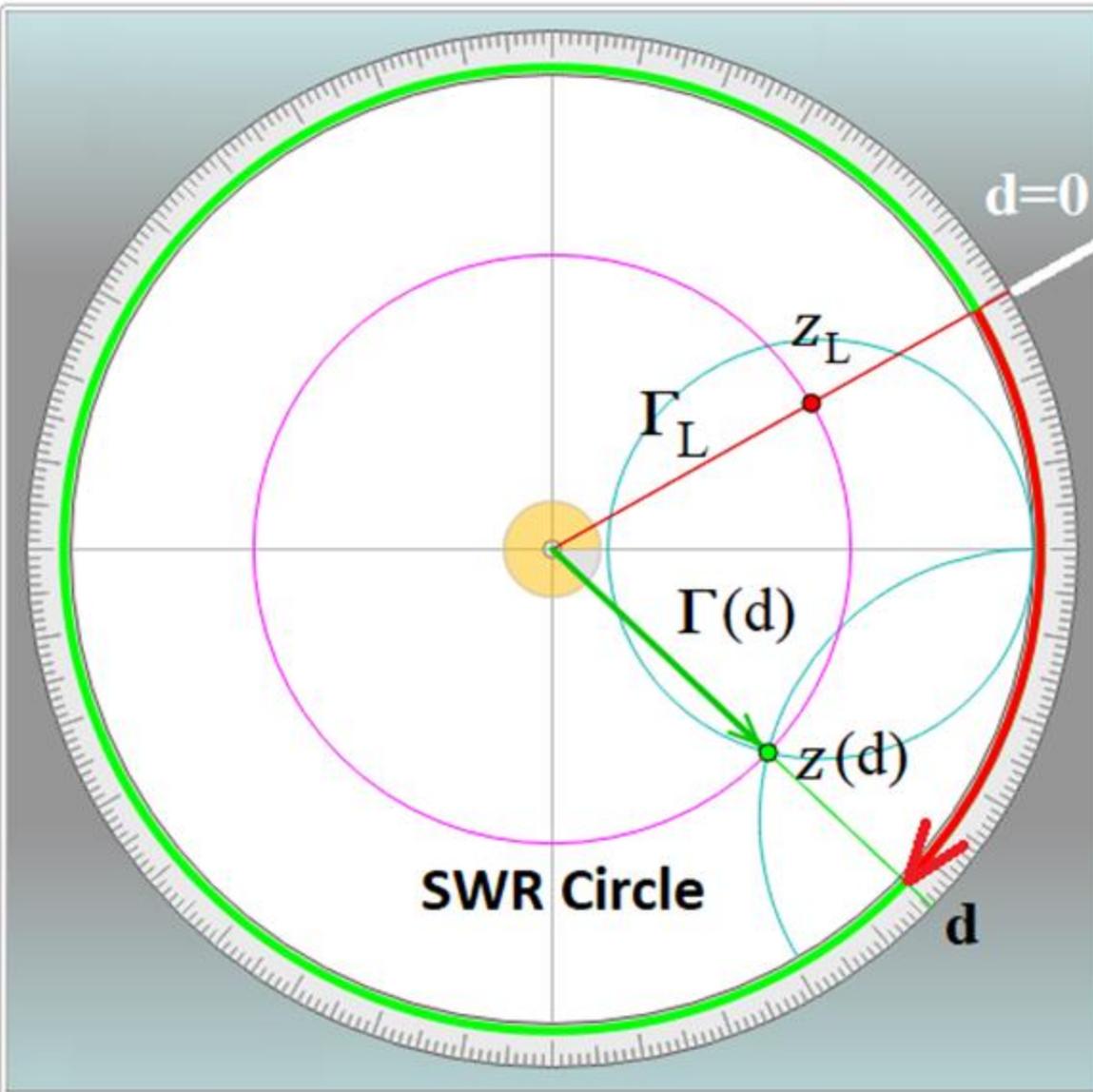
$$\Delta\theta = -2\beta d = -4\pi d / \lambda = -72.000^\circ$$



The five basic techniques of the Smith Chart

- 1) Given a reflection coefficient, obtain the corresponding impedance
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern**
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) Given an impedance find the corresponding admittance

Standing Wave Patterns

In practical applications it is very convenient to plot the **magnitude** of **phasor voltage** and **phasor current** along the transmission line. These are the **standing wave patterns**:

$$\text{Loss - less line} \left\{ \begin{array}{l} |V(\mathbf{d})| = |V^+| \cdot |\mathbf{1} + \Gamma(\mathbf{d})| \\ |I(\mathbf{d})| = \left| \frac{V^+}{Z_0} \right| \cdot |\mathbf{1} - \Gamma(\mathbf{d})| \end{array} \right.$$

The **voltage standing wave pattern** has a **maximum** at locations where the generalized reflection coefficient is **real and positive**

$$\Gamma(\mathbf{d}) = |\Gamma_{\mathbf{L}}|$$

$$\exp(j\phi) \exp(-j2\beta \mathbf{d}) = 1 \quad \Rightarrow \quad |\phi - 2\beta \mathbf{d}| = 2n\pi$$

At these locations we have

$$|1 + \Gamma(\mathbf{d})| = 1 + |\Gamma_{\mathbf{L}}|$$

$$\Rightarrow V_{\max} = |V(\mathbf{d}_{\max})| = |V^+| \cdot (1 + |\Gamma_{\mathbf{L}}|)$$

The phase angle $\phi - 2\beta \mathbf{d}$ changes by an amount 2π , when moving from one maximum to the next. This corresponds to a distance between successive maxima of $\lambda/2$.

The **voltage standing wave pattern** has a **minimum** at locations where the generalized reflection coefficient is **real and negative**

$$\Gamma(\mathbf{d}) = -|\Gamma_{\mathbf{L}}|$$

$$\exp(j\phi)\exp(-j2\beta\mathbf{d}) = -1 \quad \Rightarrow \quad |\phi - 2\beta\mathbf{d}| = (2n + 1)\pi$$

At these locations we have

$$|1 + \Gamma(\mathbf{d})| = 1 - |\Gamma_{\mathbf{L}}|$$

$$\Rightarrow V_{\min} = |V(\mathbf{d}_{\min})| = |V^+| \cdot (1 - |\Gamma_{\mathbf{L}}|)$$

Also when moving from one minimum to the next, the phase angle $\phi - 2\beta\mathbf{d}$ changes by an amount 2π . This again corresponds to a distance between successive minima of $\lambda/2$.

The voltage standing wave pattern provides immediate information on the transmission line circuit

- ❑ If the load is matched to the transmission line ($Z_L = Z_0$) the voltage standing wave pattern is flat, with value $|V^+|$.
- ❑ If the load is real and $Z_L > Z_0$, the voltage standing wave pattern starts with a maximum at the load.
- ❑ If the load is real and $Z_L < Z_0$, the voltage standing wave pattern starts with a minimum at the load.
- ❑ If the load is complex and $\text{Im}(Z_L) > 0$ (inductive reactance), the voltage standing wave pattern initially increases when moving from load to generator and reaches a maximum first.
- ❑ If the load is complex and $\text{Im}(Z_L) < 0$ (capacitive reactance), the voltage standing wave pattern initially decreases when moving from load to generator and reaches a minimum first.

Since in all possible cases

$$|\Gamma(\mathbf{d})| \leq 1$$

the **voltage standing wave pattern**

$$|V(\mathbf{d})| = |V^+| \cdot |(1 + \Gamma(\mathbf{d}))|$$

cannot exceed the value **$2 |V^+|$** in a loss-less transmission line. If the load is a short circuit, an open circuit, or a pure reactance, there is total reflection with

$$|\Gamma(\mathbf{d})| = 1$$

since the load cannot consume any power. The voltage standing wave pattern in these cases is characterized by

$$V_{\max} = 2 |V^+| \quad \text{and} \quad V_{\min} = 0 .$$

The **voltage standing wave ratio (VSWR)** is an indicator of load matching which is widely used in engineering applications

$$VSWR = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

When the load is perfectly **matched** to the transmission line

$$\Gamma_L = 0 \quad \Rightarrow \quad VSWR = 1$$

When the load is **a short circuit, an open circuit or a pure reactance**


$$|\Gamma_L| = 1 \quad \Rightarrow \quad VSWR \rightarrow \infty$$

We have the following useful relation


$$|\Gamma_L| = \frac{VSWR - 1}{VSWR + 1}$$

$$Z_L = 100.000 + j 100.000 \Omega$$

$$Z_0 = 50.00 \Omega$$

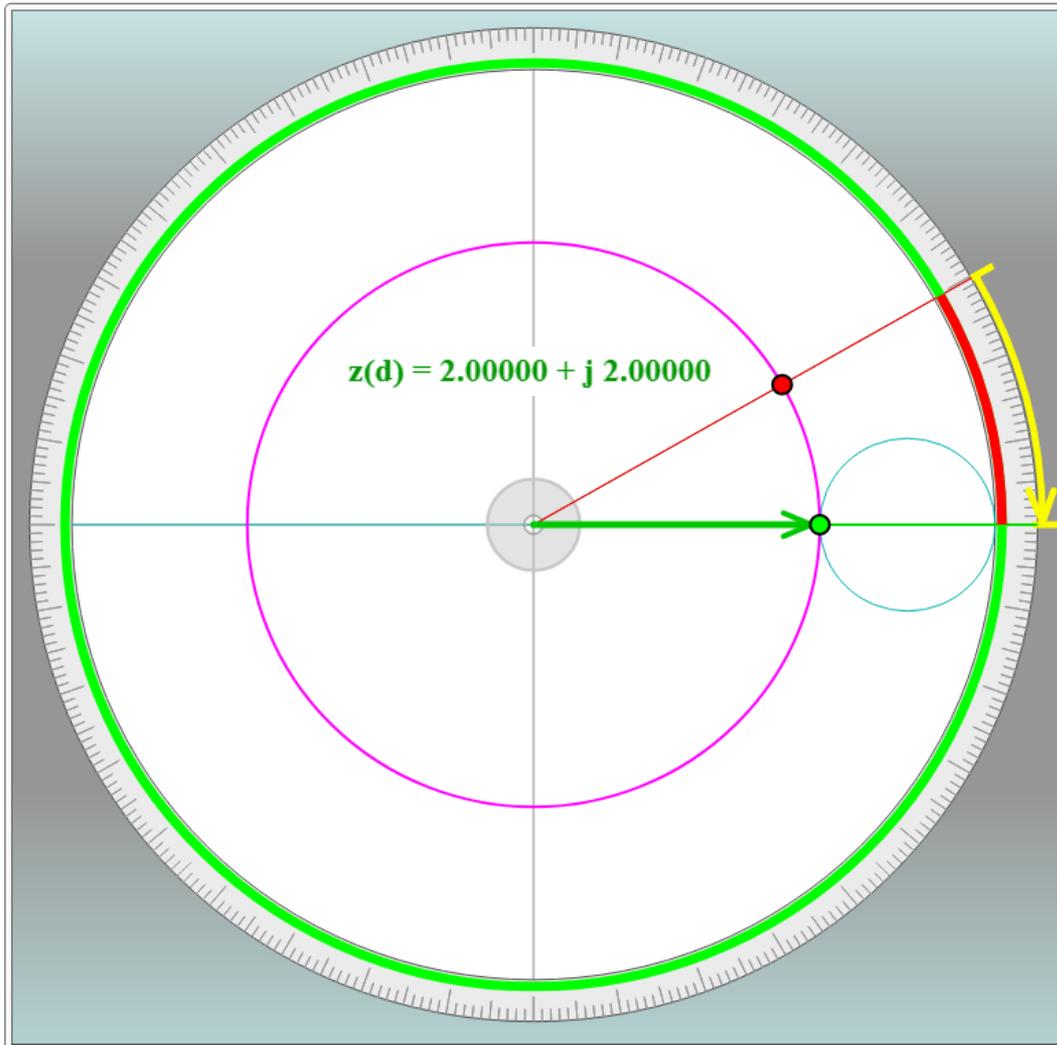

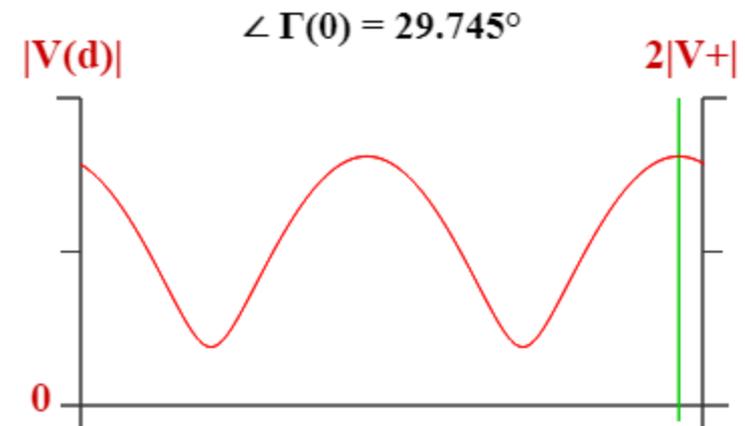When the load reactance is positive (inductive) a maximum of voltage standing wave pattern is closest to the load.




$\Gamma [d(\max)]$ is real and positive.


Location of the first maximum is
 $d(\max) = \angle \Gamma(0) \cdot \lambda / 4\pi = 0.04131 \lambda$

$$Z_L = 100.000 + j 100.000 \Omega$$

$$Z_0 = 50.00 \Omega$$

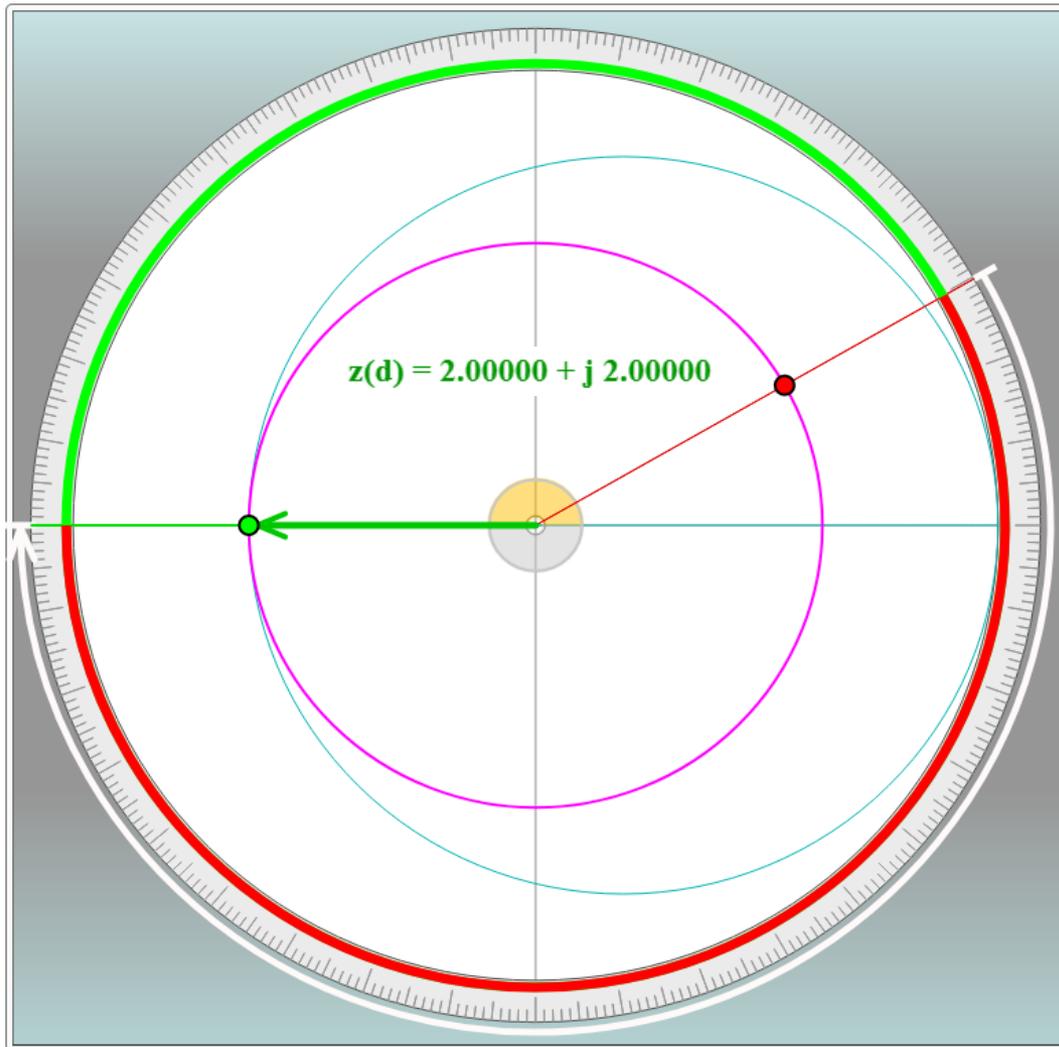

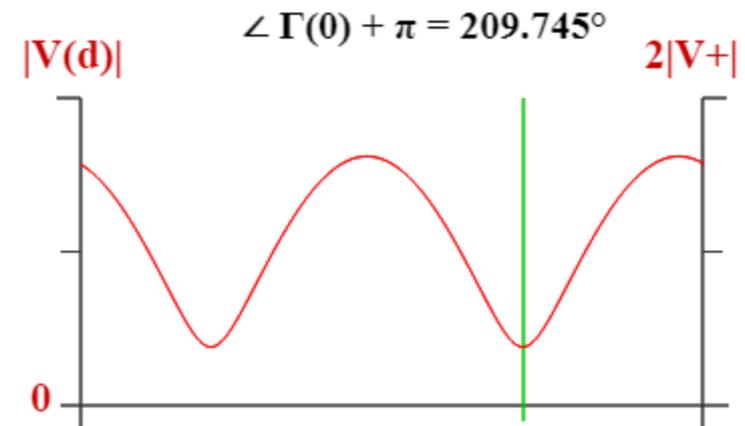When the load reactance is positive (inductive) a maximum of voltage standing wave pattern is closest to the load.




$\Gamma [d(\text{min})]$ is real and negative.

Location of the first minimum is


$$d(\text{min}) = (\angle \Gamma(0) + \pi) \cdot \lambda / 4\pi = 0.29131 \lambda$$

$$Z_L = 25.000 - j 20.000 \Omega$$

$$Z_0 = 50.00 \Omega$$

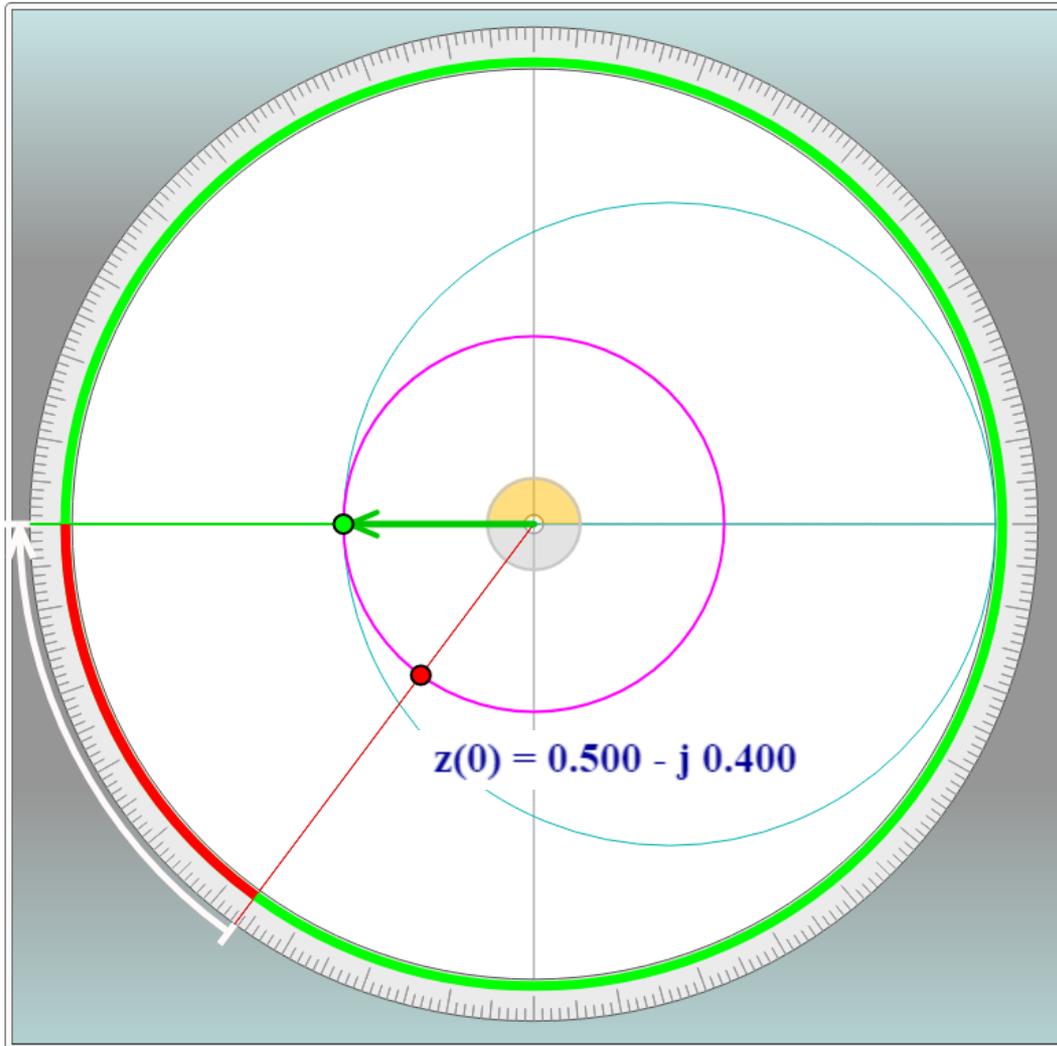

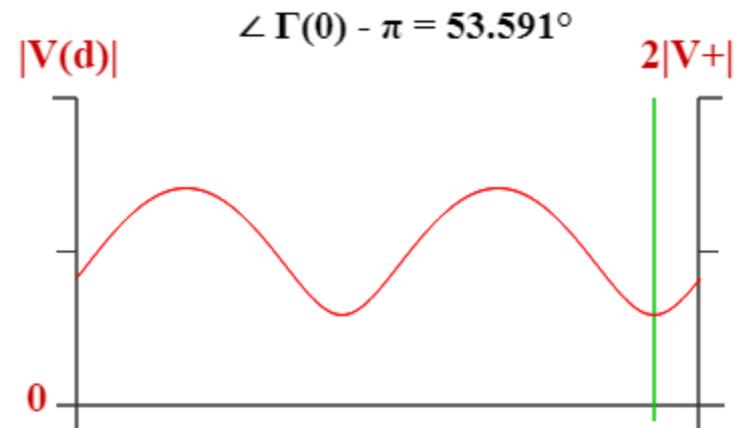When the load reactance is negative (capacitive) a minimum of voltage standing wave pattern is closest to the load.




$\Gamma [d(\text{min})]$ is real and negative.


The location of the first minimum is $d(\text{min}) = (\angle \Gamma(0) - \pi) \cdot \lambda / 4\pi = 0.07443 \lambda$.

$$Z_L = 25.000 - j 20.000 \Omega$$

$$Z_0 = 50.00 \Omega$$

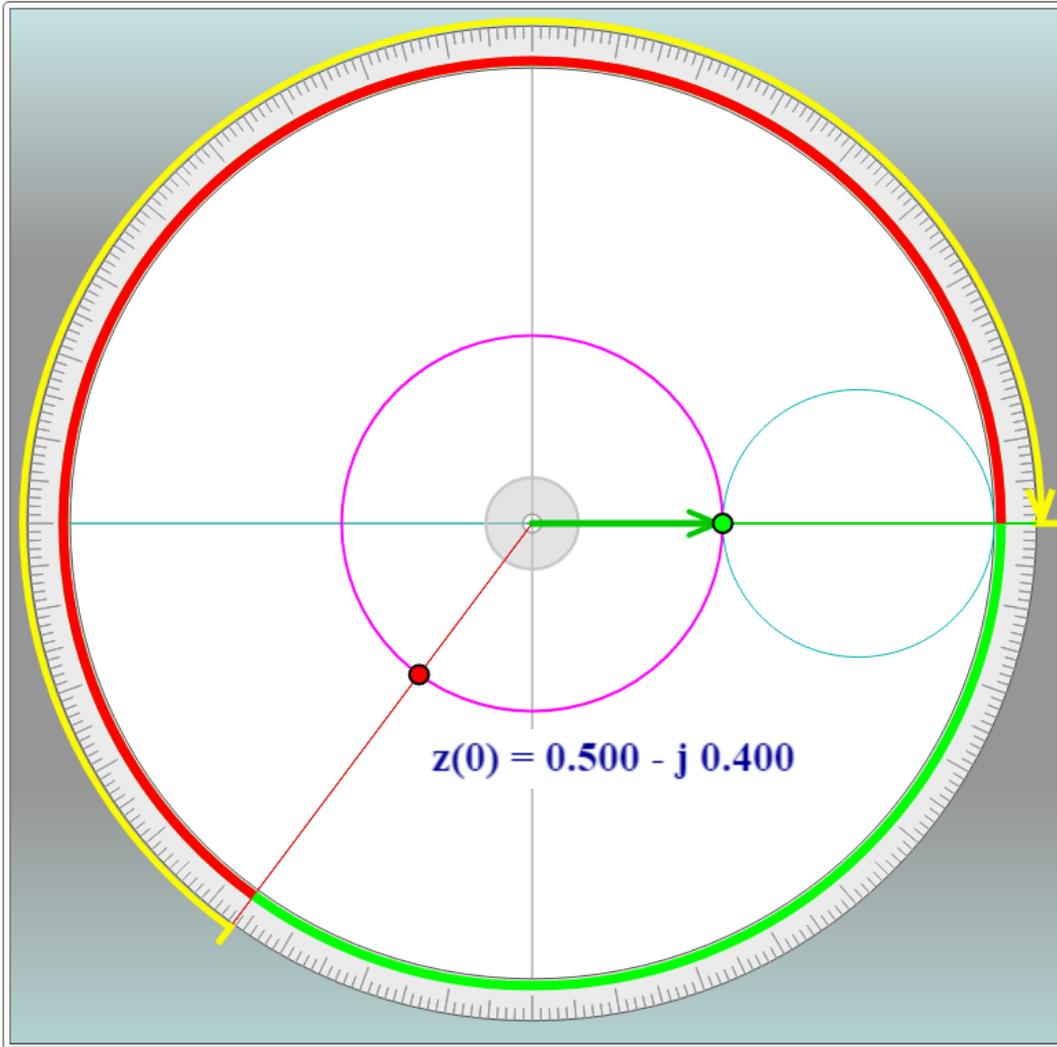

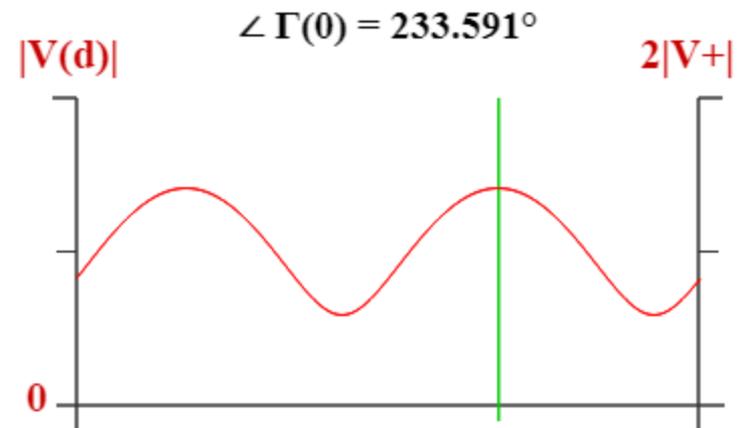When the load reactance is negative (capacitive) a minimum of voltage standing wave pattern is closest to the load.



$\Gamma [d(\max)]$ is real and positive.

The location of the first maximum is

$$d(\max) = \angle \Gamma(0) \cdot \lambda / 4\pi = 0.32443 \lambda$$

The five basic techniques of the Smith Chart

- 1) Given a reflection coefficient, obtain the corresponding impedance
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ration (VSWR)**
- 5) Given an impedance find the corresponding admittance

The reflection coefficient is real and positive at a maximum of the voltage standing wave pattern.

The normalized line impedance is also real and can be written as


$$z[d(\max)] = (1 + |\Gamma|) / (1 - |\Gamma|)$$


which is the same as the VSWR

$$\text{VSWR} = (1 + |\Gamma|) / (1 - |\Gamma|)$$

The circle of normalized resistance tangent to the SWR circle, therefore, identifies also the VSWR:

$$r = z[d(\max)] = \text{VSWR} = 4.266$$

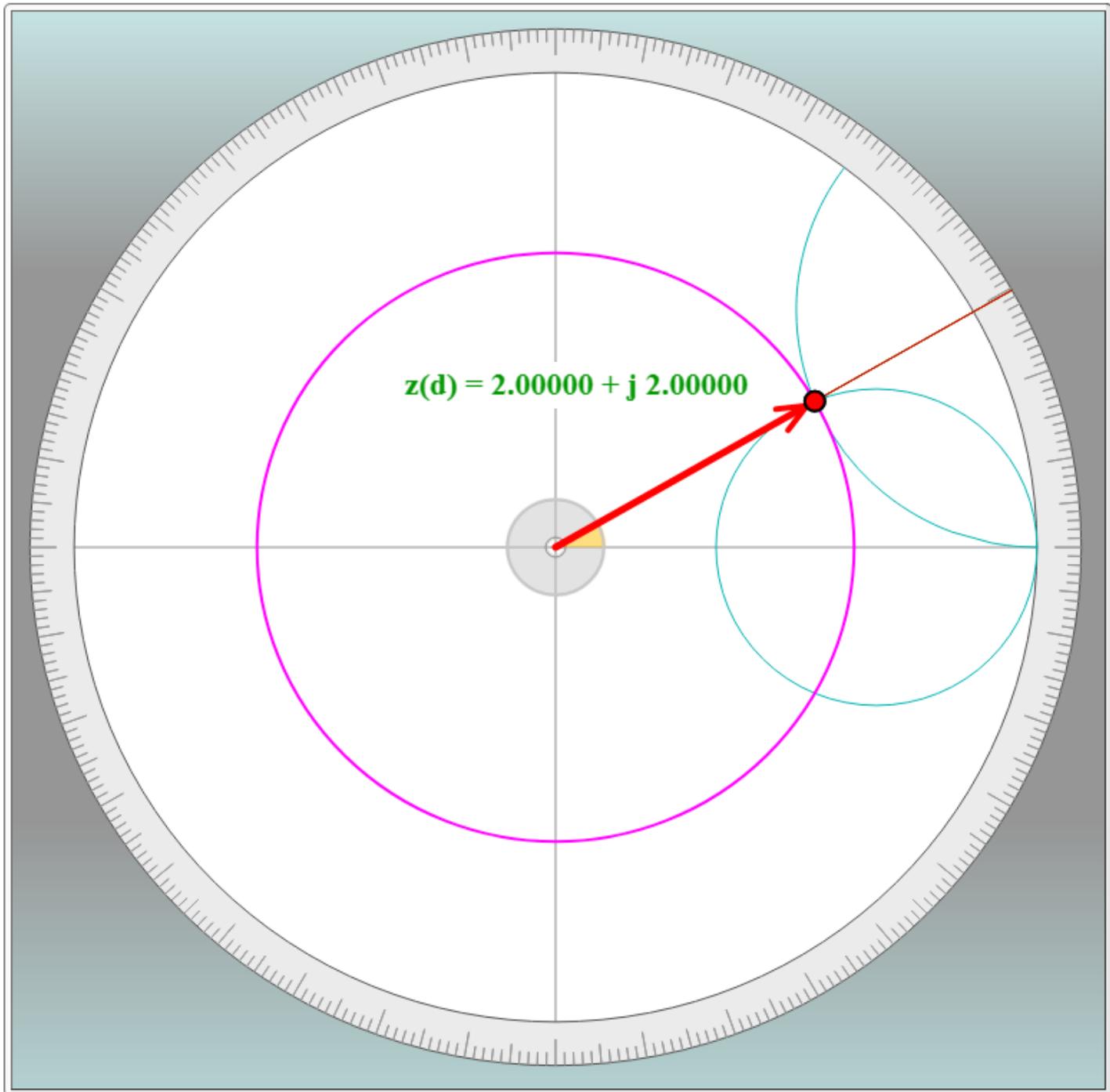

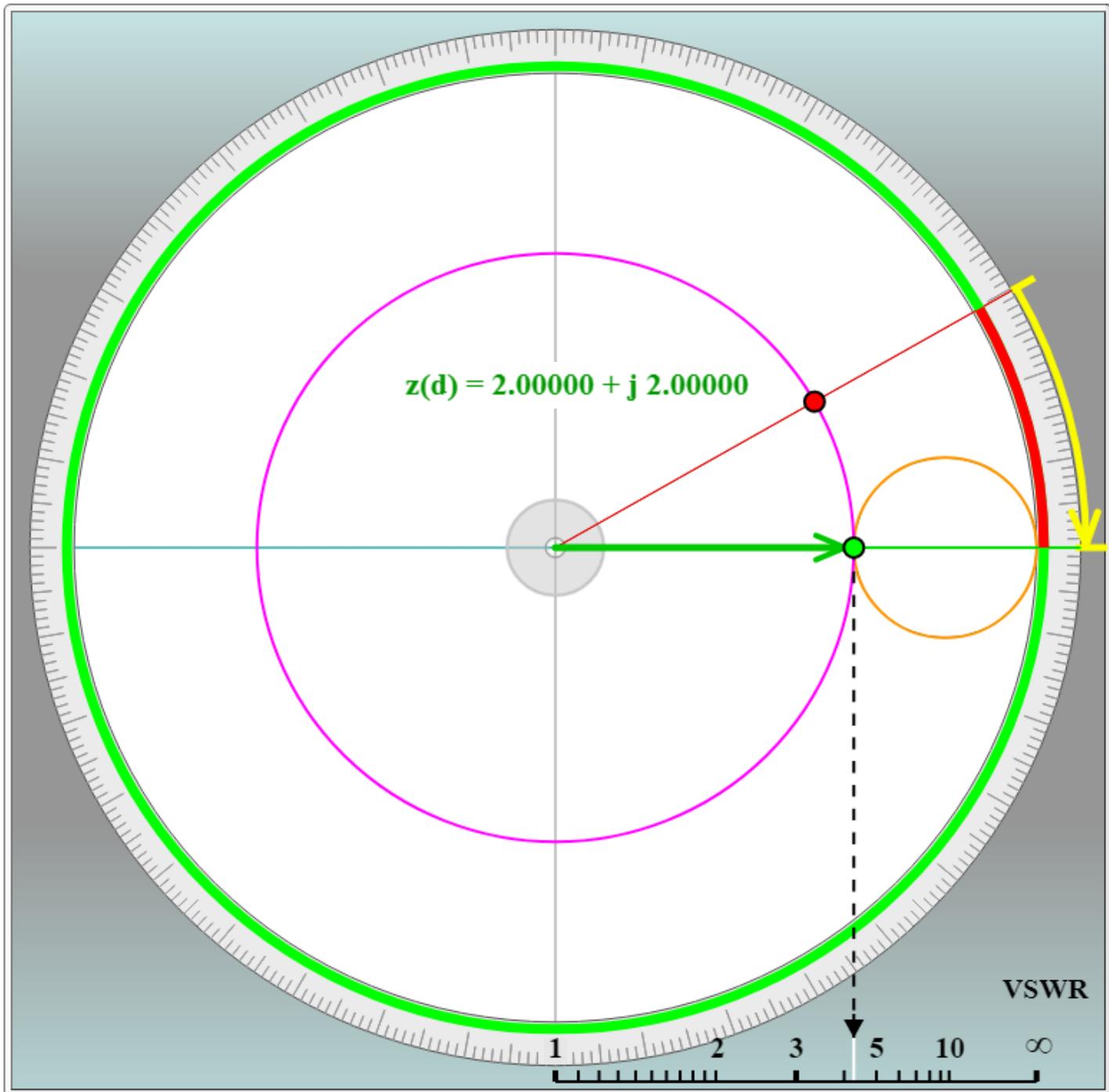

The five basic techniques of the Smith Chart

- 1) Given a reflection coefficient, obtain the corresponding impedance
- 2) Given the impedance (reflection coefficient) at one point on the line, find the impedance (reflection coefficient) at any other point on the line
- 3) Find the locations of maximum and minimum of the Standing Wave Pattern
- 4) Find the Voltage Standing Wave Ratio (VSWR)
- 5) **Given an impedance find the corresponding admittance**

Note: The normalized impedance and admittance on a lossless transmission line are defined as

$$z_n(d) = \frac{1 + \Gamma(d)}{1 - \Gamma(d)} \qquad y_n(d) = \frac{1 - \Gamma(d)}{1 + \Gamma(d)}$$

Since $\Gamma\left(d + \frac{\lambda}{4}\right) = -\Gamma(d)$

we have

$$\Rightarrow z_n\left(d + \frac{\lambda}{4}\right) = \frac{1 + \Gamma\left(d + \frac{\lambda}{4}\right)}{1 - \Gamma\left(d + \frac{\lambda}{4}\right)} = \frac{1 - \Gamma(d)}{1 + \Gamma(d)} = y_n(d)$$

Keep in mind that the equality $z_n\left(d + \frac{\lambda}{4}\right) = y_n(d)$

is only valid for normalized impedance and admittance. The actual values are given by

$$Z\left(d + \frac{\lambda}{4}\right) = Z_0 \cdot z_n\left(d + \frac{\lambda}{4}\right) \quad \Rightarrow \quad Z\left(d + \frac{\lambda}{4}\right) = Z_0^2 Y(d)$$
$$Y(d) = Y_0 \cdot y_n(d) = \frac{y_n(d)}{Z_0}$$

where $Y_0 = 1 / Z_0$ is the characteristic admittance of the line.


Let's review the *impedance-admittance* terminology:


Impedance = Resistance + j Reactance

$$Z = R + jX$$

Admittance = Conductance + j Susceptance

$$Y = G + jB$$

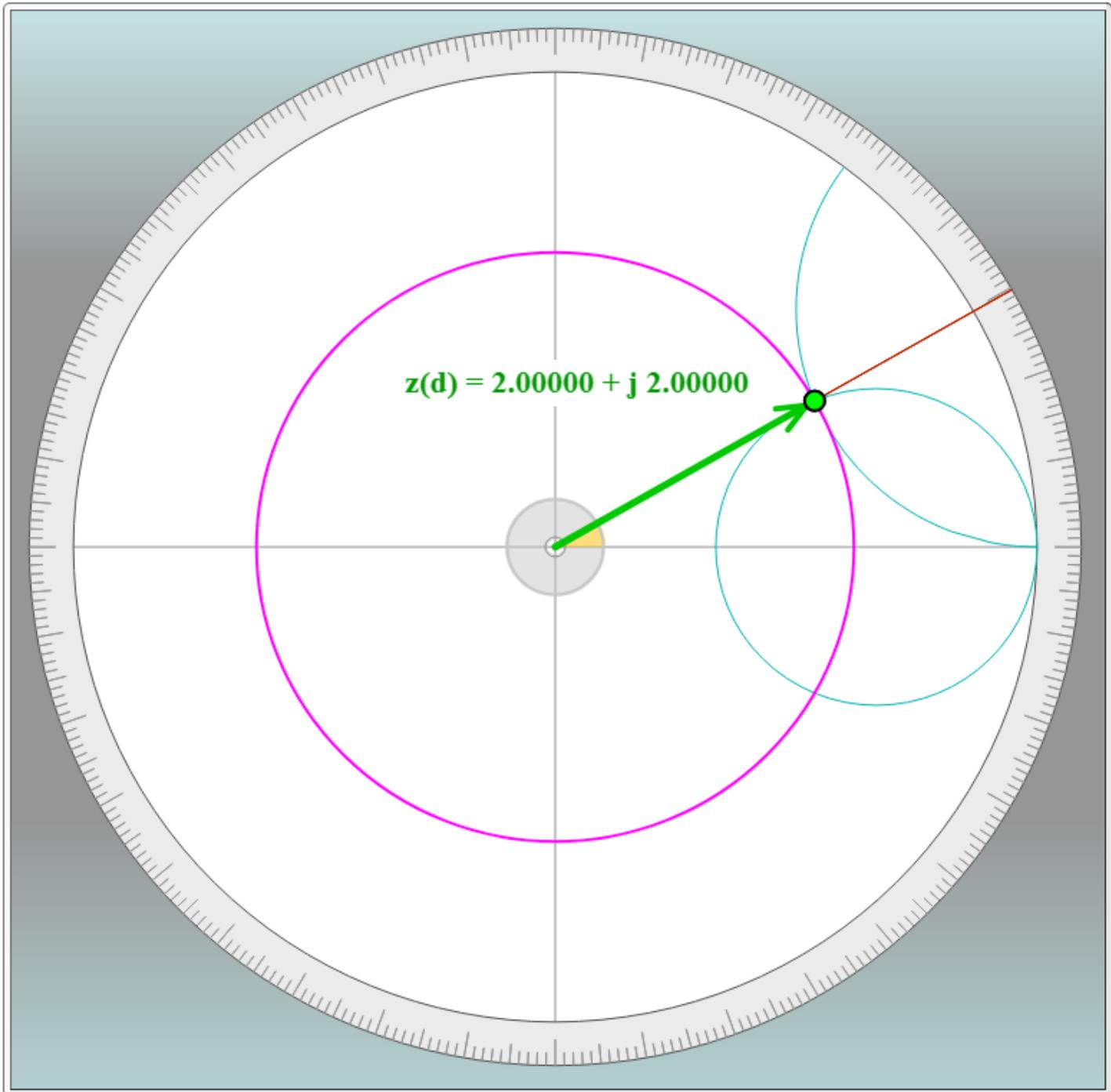

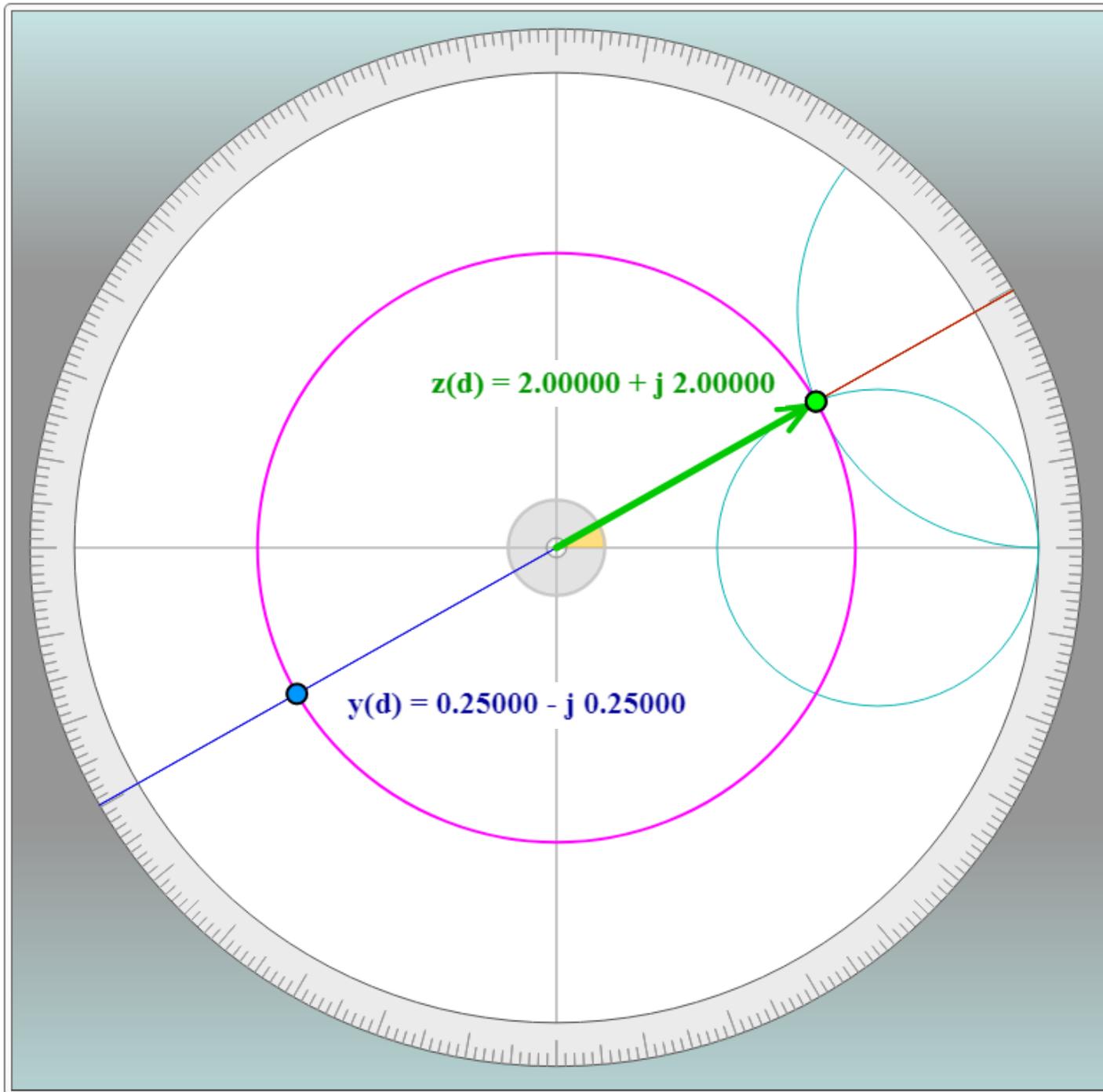

Normalized values

$$z(d) = (1 + \Gamma(d)) / (1 - \Gamma(d))$$

$$y(d) = (1 - \Gamma(d)) / (1 + \Gamma(d))$$

Since $\Gamma(d + \lambda/4) = -\Gamma(d)$, we have

$$z(d + \lambda/4) = y(d)$$

$\lambda/4$ corresponds to 180° rotation.

$$z(d) = 2.00000 + j 2.00000$$

$$y(d) = 0.25000 - j 0.25000$$

Equality $z(d + \lambda/4) = y(d)$ holds for normalized quantities, but

$$Z(d + \lambda/4) = z(d + \lambda/4) \cdot Z_0$$


$$Y(d) = y(d) / Z_0$$

d = λ

Module 2.6
Interactive Smith Chart

Instructions

Color

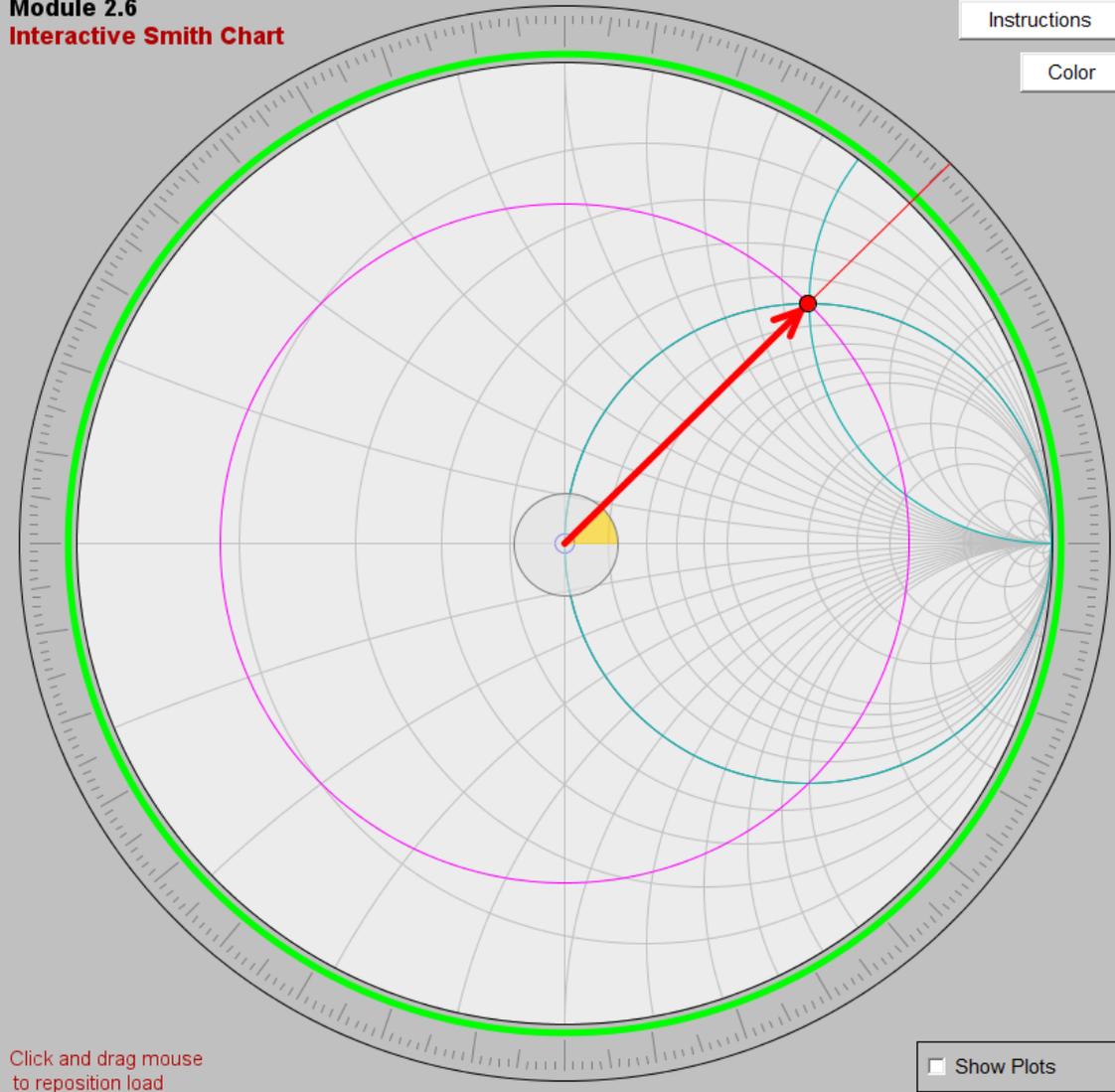

Click and drag mouse
to reposition load

Show Plots

- SWR Circle
- Show Curves
- Full Chart
- Cursor Lines
- y (d)

- Tangent SWR Circle
SWR = 5.8284
- Voltage Maximum
d(max) = 0.0625 λ
- Voltage Minimum
d(min) = 0.3125 λ

- Show Γ
- Load
- Cursor

- $z_L = 1.0 + j 2.0$
 $\Gamma_L = 0.70710678 \angle 45.0^\circ$
- $z(d) = 1.0 + j 2.0$
 $\Gamma_d = 0.70710678 \angle 45.0^\circ$
- $y(d) = 0.2 - j 0.4$

- ↷ $d = 0.0 \lambda$
 $2 \beta d = 0.0 \text{ rad} = 0.0^\circ$
- ↷ $0.5 \lambda - d = 0.5 \lambda$
 $2 \beta (0.5 \lambda - d) = 6.2832 \text{ rad} = 360.0^\circ$

Set Line
Z₀ = [Ω]


Set Load
Z_L =
< >
+ j [Ω]
< >
 Z Y Γ

$d =$ λ

Module 2.6 Interactive Smith Chart




Instructions

Color

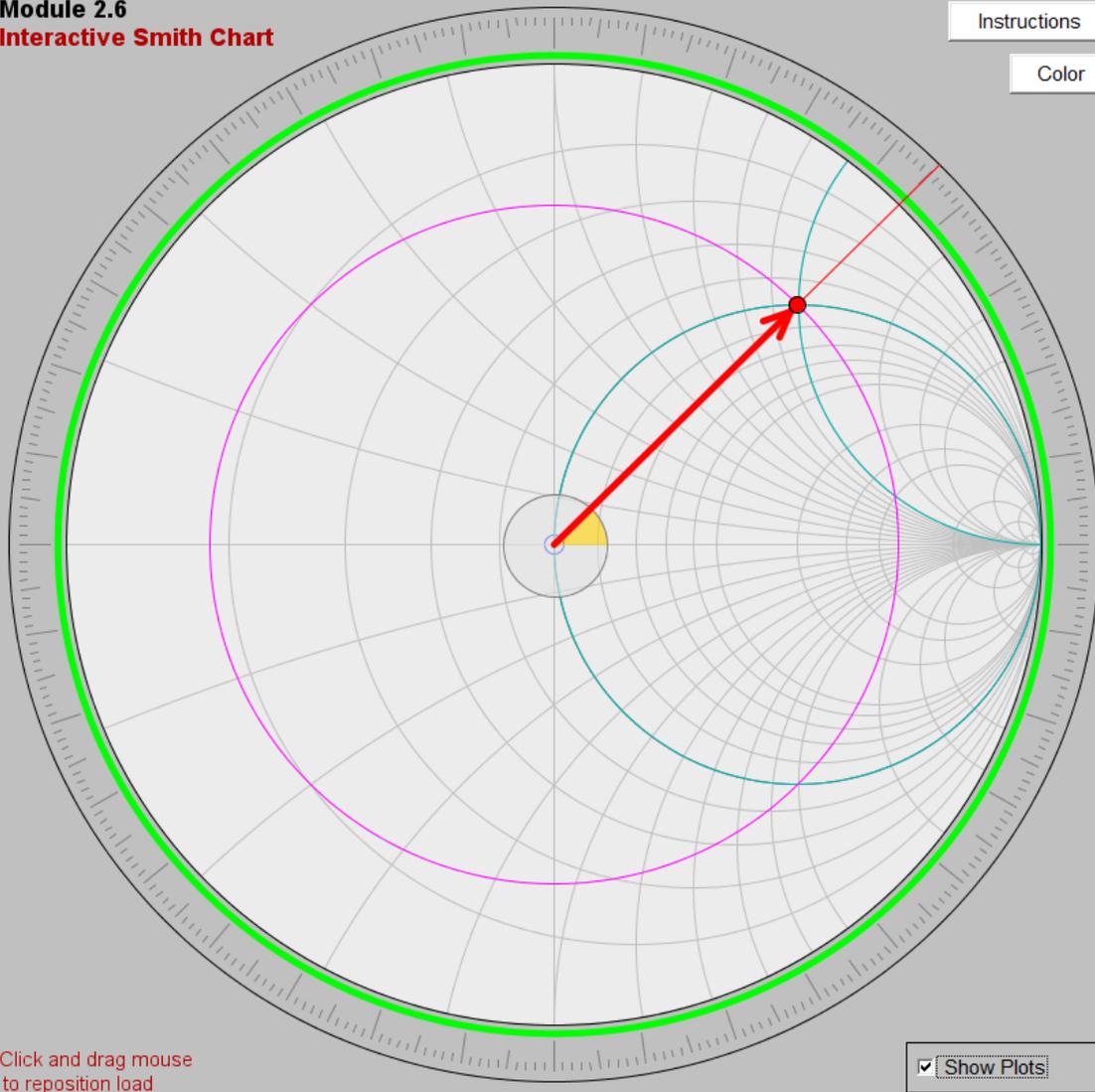

Click and drag mouse
to reposition load

Show Plots

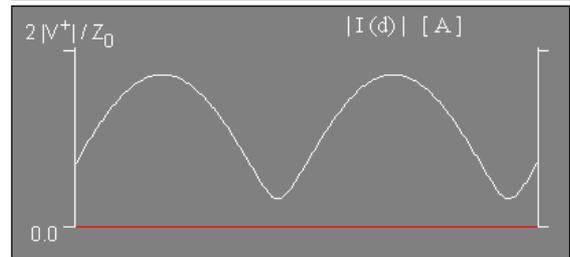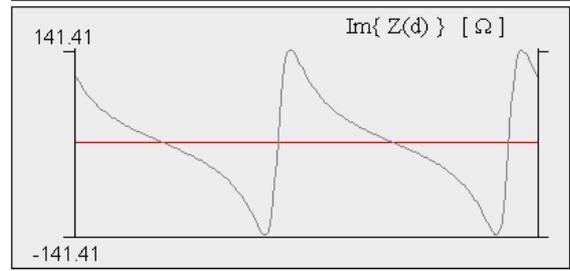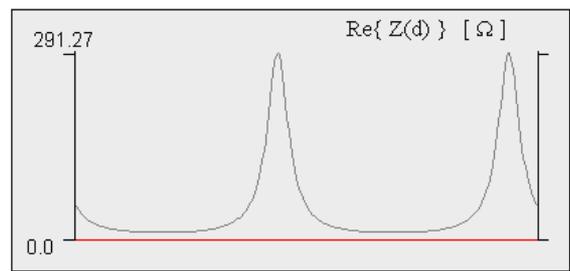


$d \quad \lambda \quad 0$

$$Z(d) = 50.0 + j 100.0 \ \Omega$$


$$d = 0.0 \ \lambda$$

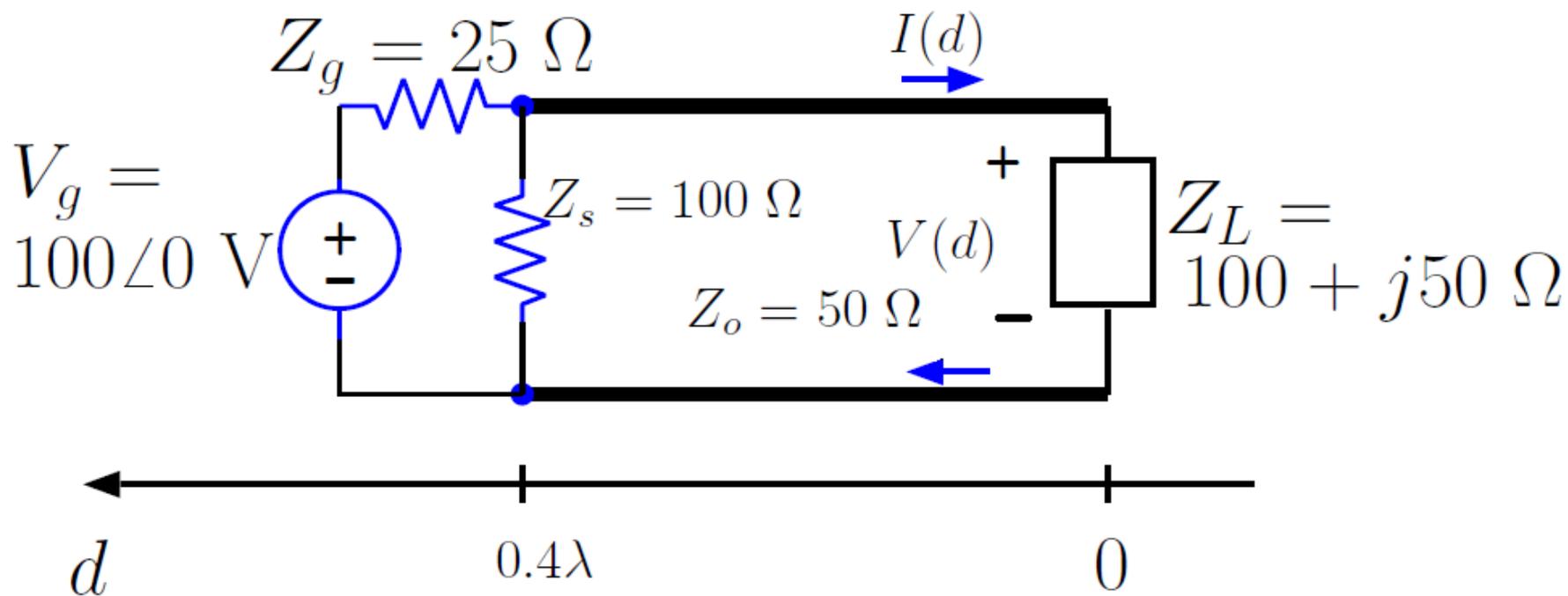Example 1: A load $Z_L = 100 + j50 \Omega$ is connected across a TL with $Z_o = 50 \Omega$ and $l = 0.4\lambda$. At the generator end, $d = l$, the line is shunted by an impedance $Z_s = 100 \Omega$. What are the input impedance Z_{in} and admittance Y_{in} of the line, including the shunt connected element.



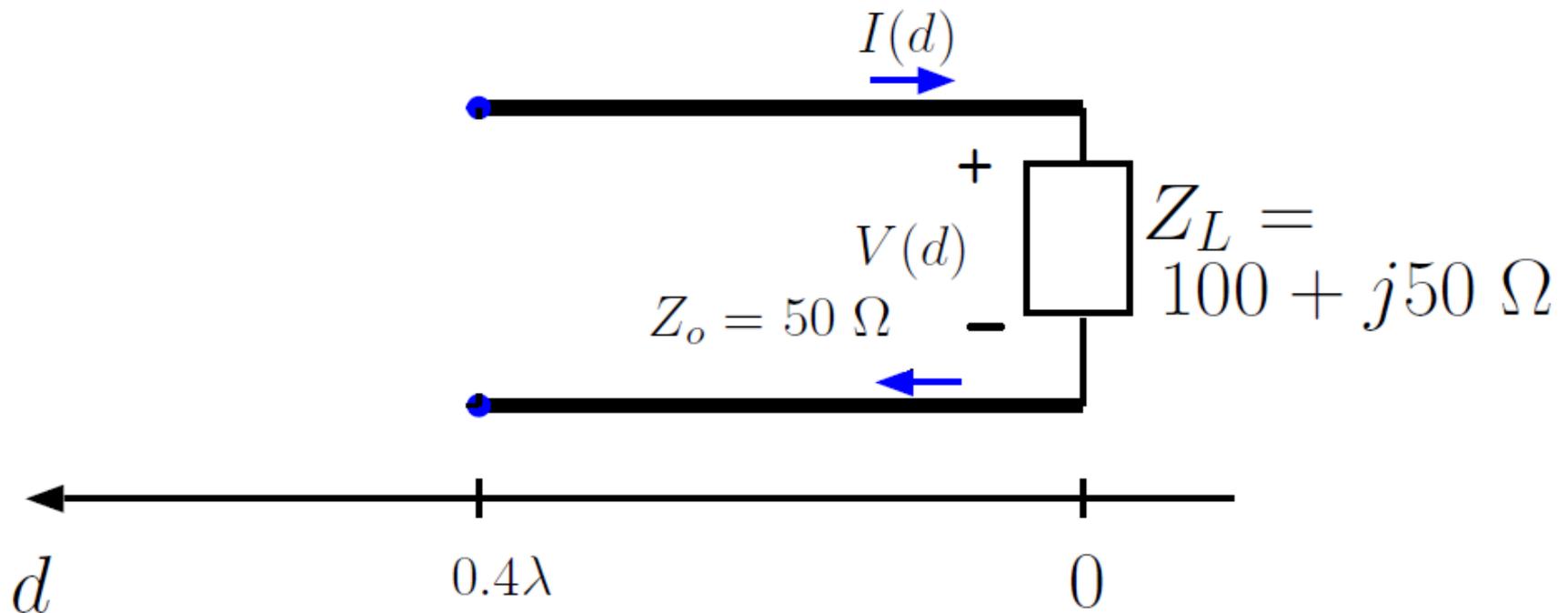Example 1: A load $Z_L = 100 + j50 \Omega$ is connected across a TL with $Z_o = 50 \Omega$ and $l = 0.4\lambda$. At the generator end, $d = l$, the line is shunted by an impedance $Z_s = 100 \Omega$. What are the input impedance Z_{in} and admittance Y_{in} of the line, including the shunt connected element.


First find the input impedance/admittance of the line



d = λ

Module 2.6 Interactive Smith Chart

Instructions
Color

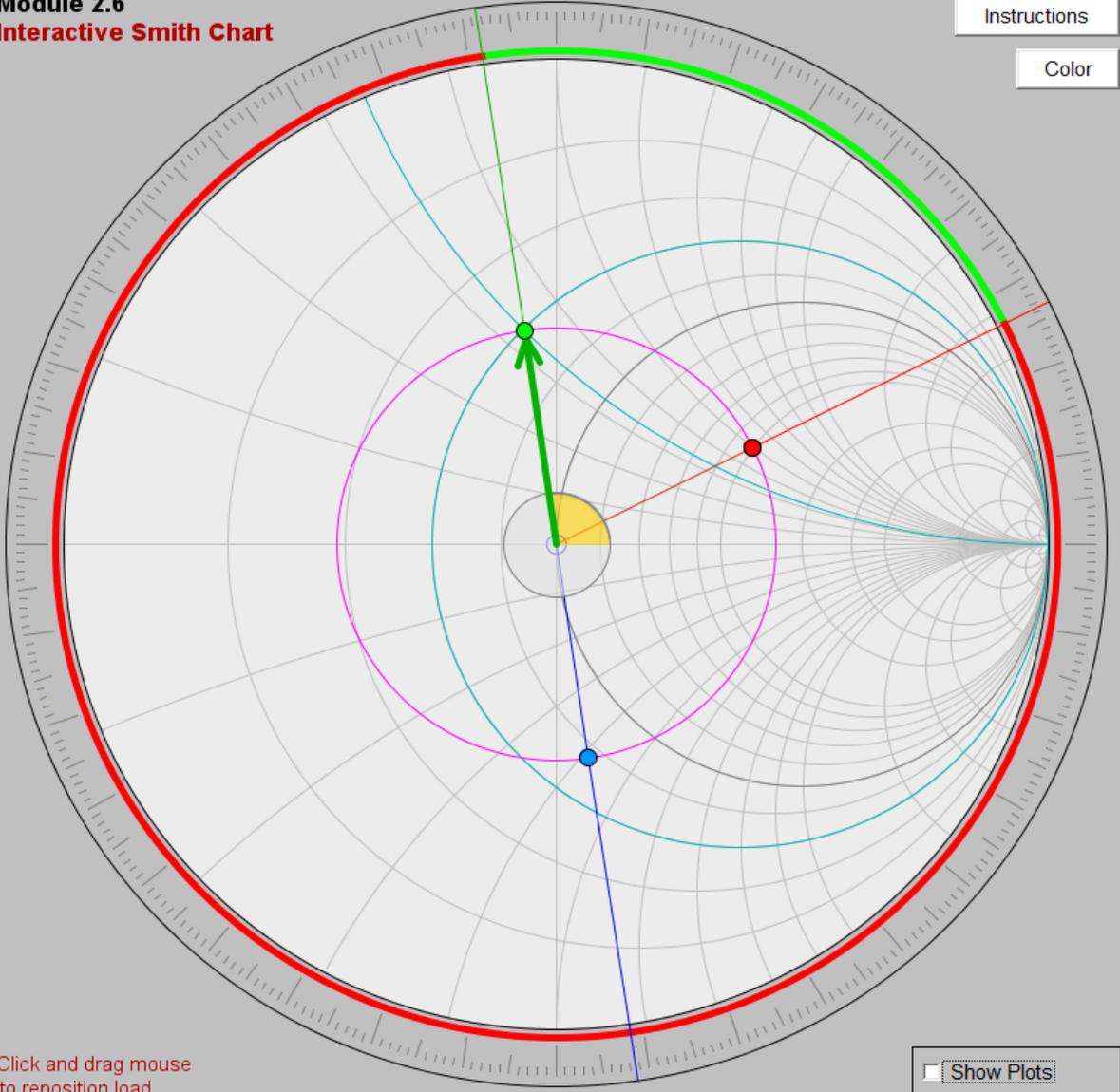

Click and drag mouse
to reposition load

Show Plots

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 2.618
- Voltage Maximum
d(max) = 0.0369 λ
- Voltage Minimum
d(min) = 0.2869 λ
- Show Γ Load Cursor

- $z_L = 2.0 + j1.0$
 $\Gamma_L = 0.4472136 \angle 26.5651^\circ$
- $z(d) = 0.600056 + j0.663401$
 $\Gamma_d = 0.4472136 \angle 98.5651^\circ$
- $y(d) = 0.749913 - j0.829077$

- 🔴 $d = 0.4\lambda$
 $2\beta d = 5.026548 \text{ rad} = 288.0^\circ$
- 🟢 $0.5\lambda - d = 0.1\lambda$
 $2\beta (0.5\lambda - d) = 1.2566 \text{ rad} = 72.0^\circ$


Set Line
 $Z_0 =$ [Ω]

Set Load
 $Z_L =$

 $+ j$ [Ω]

 Z Y Γ

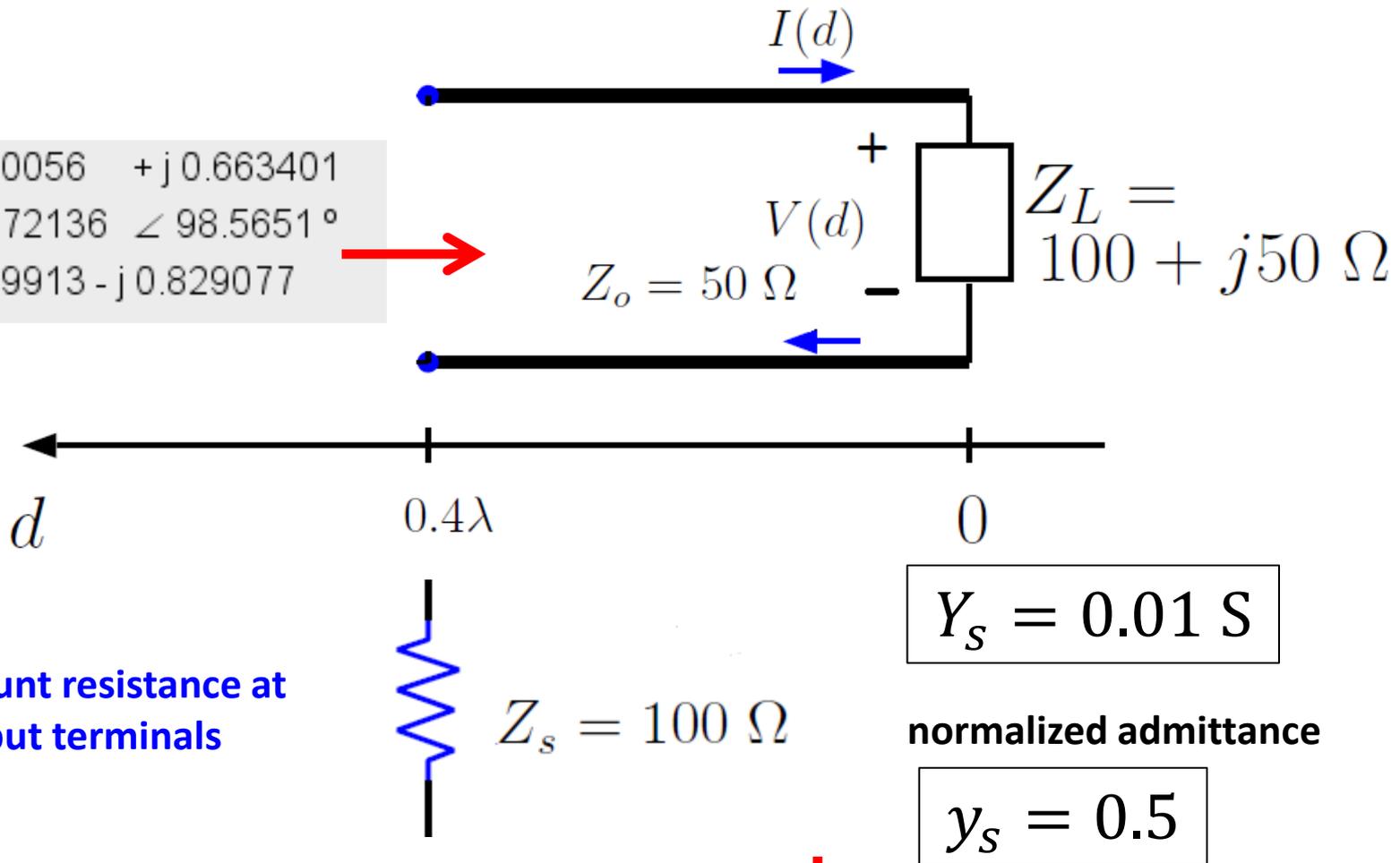- $z(d) = 0.600056 + j0.663401$
- $\Gamma_d = 0.4472136 \angle 98.5651^\circ$
- $y(d) = 0.749913 - j0.829077$



Shunt resistance at input terminals

$$Z_s = 100 \Omega$$

$$Y_s = 0.01 \text{ S}$$

normalized admittance

$$y_s = 0.5$$

$$y_{in} = y(l) + y_{si} \approx 1.25 - j0.83$$

$$Y_{in} = Y_o y_{in} \approx 0.025 - j0.017 \text{ S}$$

$$z_{in} = \frac{1}{y_i} \approx 0.56 + j0.37$$

$$Z_{in} = Z_o z_{in} \approx 27.8 + j18.4 \Omega$$

Example 3: A TL of length $l = 0.3\lambda$ has an input impedance $Z_{in} = 50 + j50 \Omega$. Determine the load impedance $Z_L = Z(0)$ and $Y_L = Y(0)$ given that $Z_o = 50 \Omega$ for the line.

Trick: To consider an input impedance in the Java app, enter it as a load but move the cursor to 1λ . This will be now your input location corresponding to an input impedance equal to what you have entered (we exploit periodicity of the impedance).

Then, move back the cursor by the length of the line (in this case 0.3λ). This means that the location $d = 0.7\lambda$ now represents a location equivalent to the load and you can read there the corresponding impedance.

d = λ

position cursor at 1λ

Module 2.6
Interactive Smith Chart

Instructions
Color

- SWR Circle
- Show Curves
- Full Chart
- Cursor Lines
- $y(d)$

- Tangent SWR Circle
SWR = 2.618
- Voltage Maximum
 $d(\max) = 0.0881 \lambda$
- Voltage Minimum
 $d(\min) = 0.3381 \lambda$
- Show Γ
- Load
- Cursor

- $z_L = 1.0 + j 1.0$
 $\Gamma_L = 0.4472136 \angle 63.4349^\circ$
- $z(d) = 1.0 + j 1.0$
 $\Gamma_d = 0.4472136 \angle 63.4349^\circ$
- $y(d) = 0.5 - j 0.5$

- ⤿ $d' = 0.5 \lambda$ ⤿ $d = 1.0 \lambda$
 $2 \beta d' = 6.283185 \text{ rad} = 360.0^\circ$
- ⤿ $0.5\lambda - d' = 0.0 \lambda$
 $2 \beta (0.5\lambda - d') = 0.0 \text{ rad} = 0.0^\circ$

Set Line Update
 $Z_0 = 50.0 \text{ } [\Omega]$

Set Load Update
 $Z_L = 50.0$
 $+ j 50.0 \text{ } [\Omega]$

this now represents
the input impedance

Click and drag mouse
to reposition load

Show Plots

d =

< [Slider] >

this location now represents the load


> [Slider] >

Module 2.6
Interactive Smith Chart

Instructions
Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

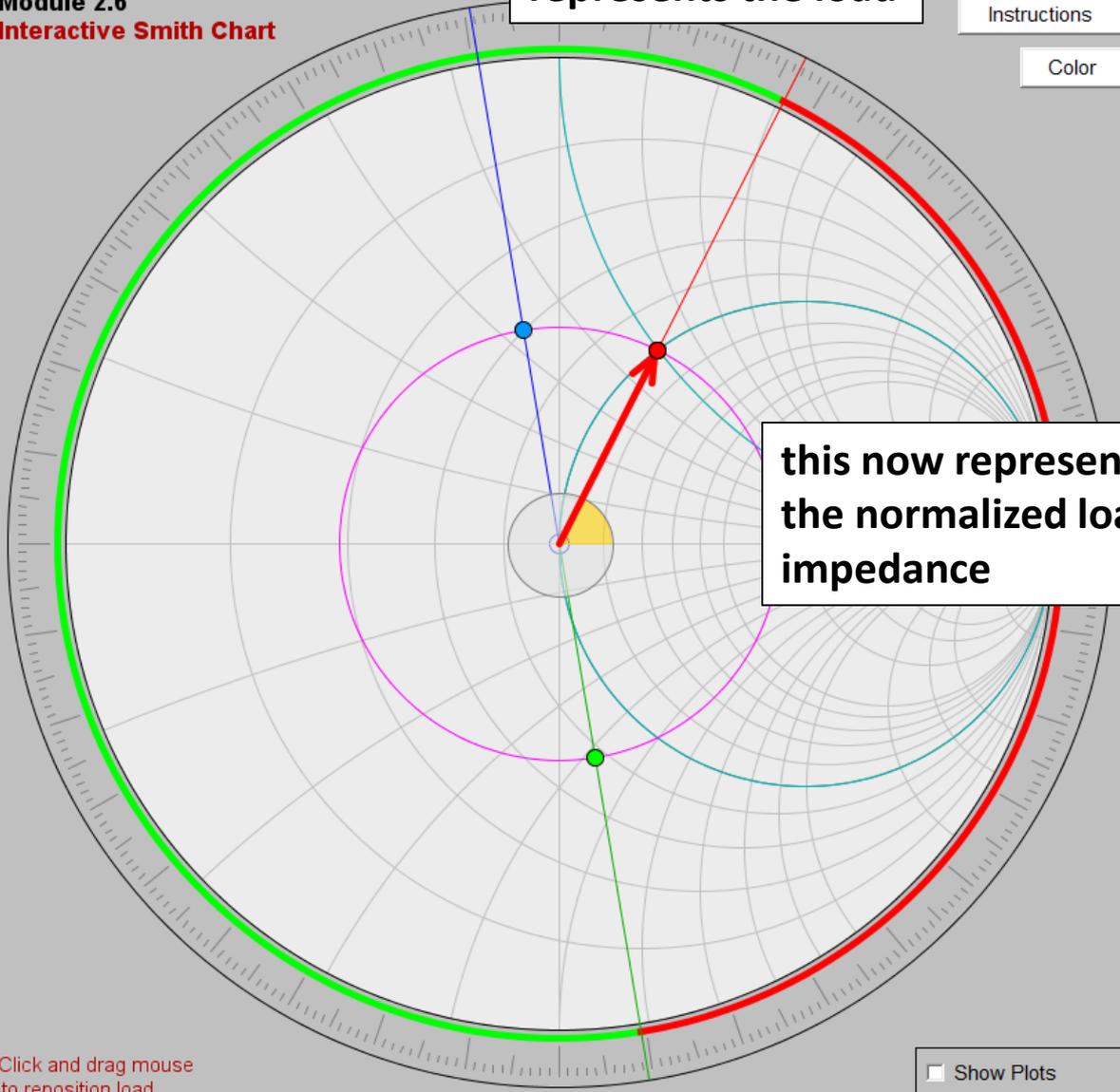- Tangent SWR Circle
SWR = 2.618
- Voltage Maximum
d(max) = 0.0881 λ
- Voltage Minimum
d(min) = 0.3381 λ
- Show Γ
- Load
- Cursor



this now represents the normalized load impedance

● $z_L = 1.0 + j1.0$
 $\Gamma_L = 0.4472136 \angle 63.4349^\circ$
 ● $z(d) = 0.759461 - j0.837617$
 $\Gamma_d = 0.4472136 \angle -80.5651^\circ$
 ● $y(d) = 0.594079 + j0.655216$

● $d' = 0.2 \lambda$
 $2 \beta d' = 2.513274 \text{ rad} = 144.0^\circ$

● $0.5\lambda - d' = 0.3 \lambda$
 $2 \beta (0.5\lambda - d') = 3.769911 \text{ rad} = 216.0^\circ$

Set Line [Update]
 $Z_0 = 50.0 [\Omega]$

Set Load [Update]
 $Z_L = 50.0$
 + j 50.0 [Ω]
 Z Y Γ

Click and drag mouse to reposition load

Show Plots

d =

Input field for distance d, with a red box highlighting the current value.





this location now represents the load

Input field for wavelength lambda.

Module 2.6 Interactive Smith Chart

Instructions

Color

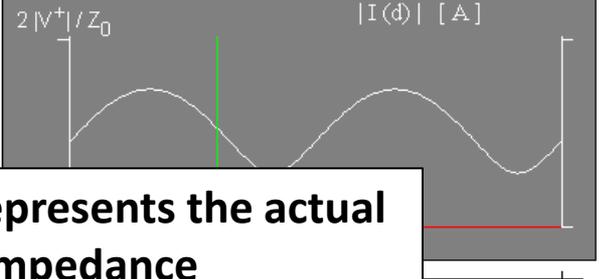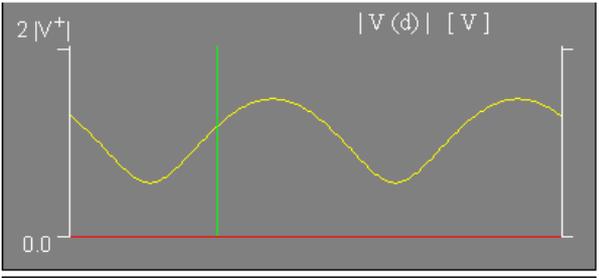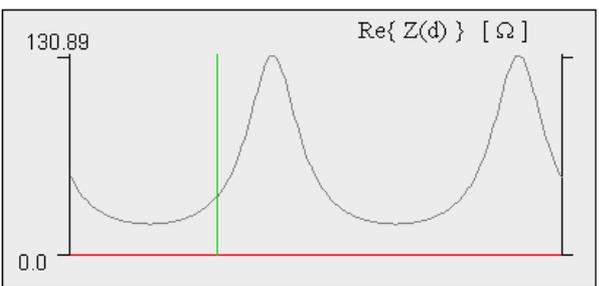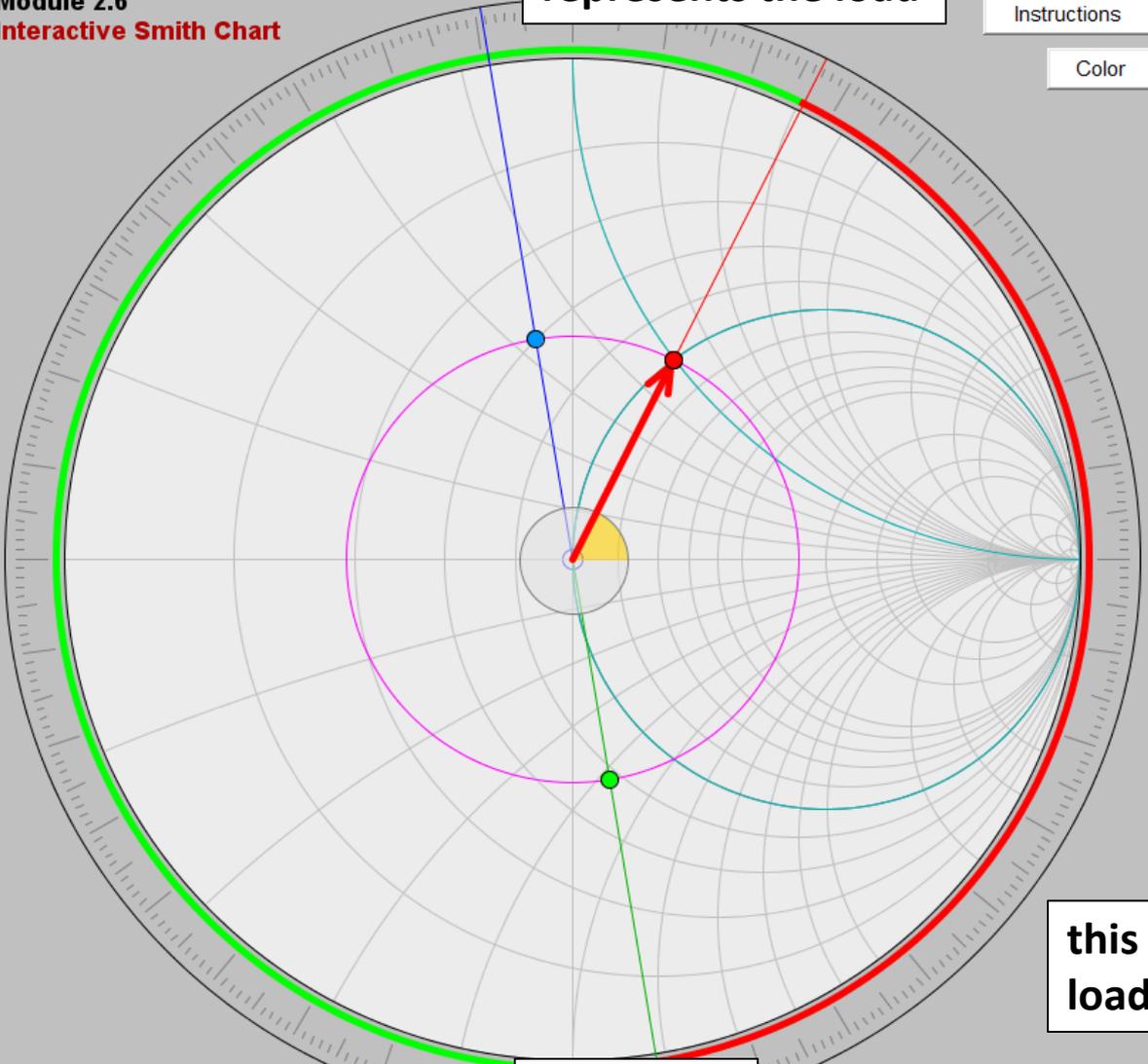

this represents the actual load impedance

$Z(d) = 37.973052 - j 41.880844 \ \Omega$
 $d = 0.7 \lambda$


Click and drag mouse to reposition load

click here



Show Plots

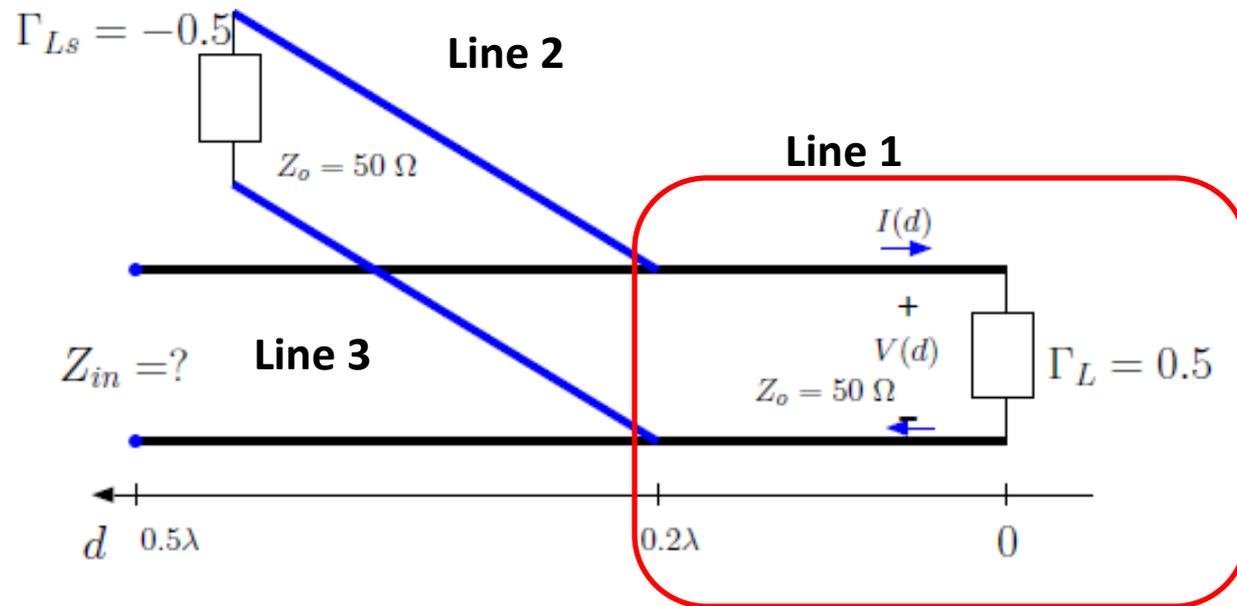Example 4: A TL of length $l = 0.5\lambda$ and $Z_o = 50 \Omega$ has a load reflection coefficient $\Gamma_L = 0.5$ and a shunt connected TL at $d = 0.2\lambda$. The shunt connected TL has $l = 0.3\lambda$, $Z_o = 50 \Omega$, and a load reflection coefficient $\Gamma_L = -0.5$. Determine the input impedance of the line.



d = λ

Module 2.6 Interactive Smith Chart

Instructions
Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 3.0
- Voltage Maximum
d(max) = 0.5 λ
- Voltage Minimum
d(min) = 0.25 λ
- Show Γ Load Cursor

- $z_L = 3.0 + j0.0$
 $\Gamma_L = 0.5 \angle 0.0^\circ$
- $z(d) = 3.0 + j0.0$
 $\Gamma_d = 0.5 \angle 0.0^\circ$
- $y(d) = 0.333333 + j0.0$

- 🔴 $d = 0.0 \lambda$
 $2\beta d = 0.0 \text{ rad} = 0.0^\circ$
- 🟢 $0.5\lambda - d = 0.5\lambda$
 $2\beta(0.5\lambda - d) = 6.2832 \text{ rad} = 360.0^\circ$

Set Line
 $Z_0 =$ $[\Omega]$

Set Load
 $\Gamma_L =$

 \angle $^\circ$

 Z Y Γ

enter


select

Click and drag mouse to reposition load

Show Plots

d = λ

Module 2.6 Interactive Smith Chart

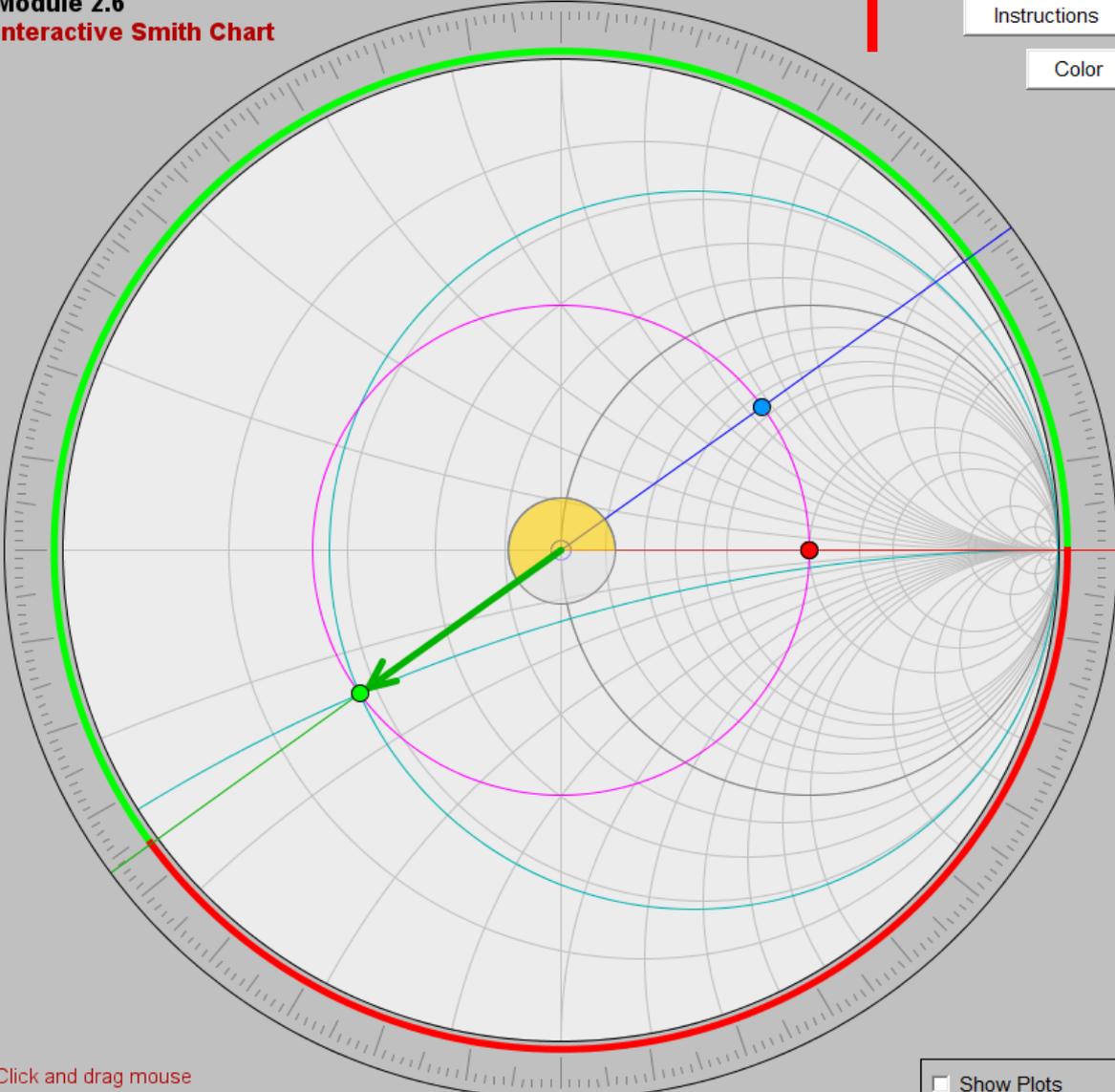

Instructions
Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 3.0
- Voltage Maximum
d(max) = 0.5 λ
- Voltage Minimum
d(min) = 0.25 λ
- Show Γ
- Load
- Cursor

● $z_L = 3.0 + j0.0$
 $\Gamma_L = 0.5 \angle 0.0^\circ$
● $z(d) = 0.364251 - j0.285469$
 $\Gamma_d = 0.5 \angle -144.0^\circ$
● $y(d) = 1.700746 + j1.332898$

Line 1 input
d = 0.2 λ
 $2\beta d = 2.513274 \text{ rad} = 144.0^\circ$
0.5λ - d = 0.3λ
 $2\beta (0.5\lambda - d) = 3.7699 \text{ rad} = 216.0^\circ$


Set Line
 $Z_0 =$ $[\Omega]$

Set Load
 $\Gamma_L =$
 \angle °
 Z Y Γ

Click and drag mouse
to reposition load

Show Plots

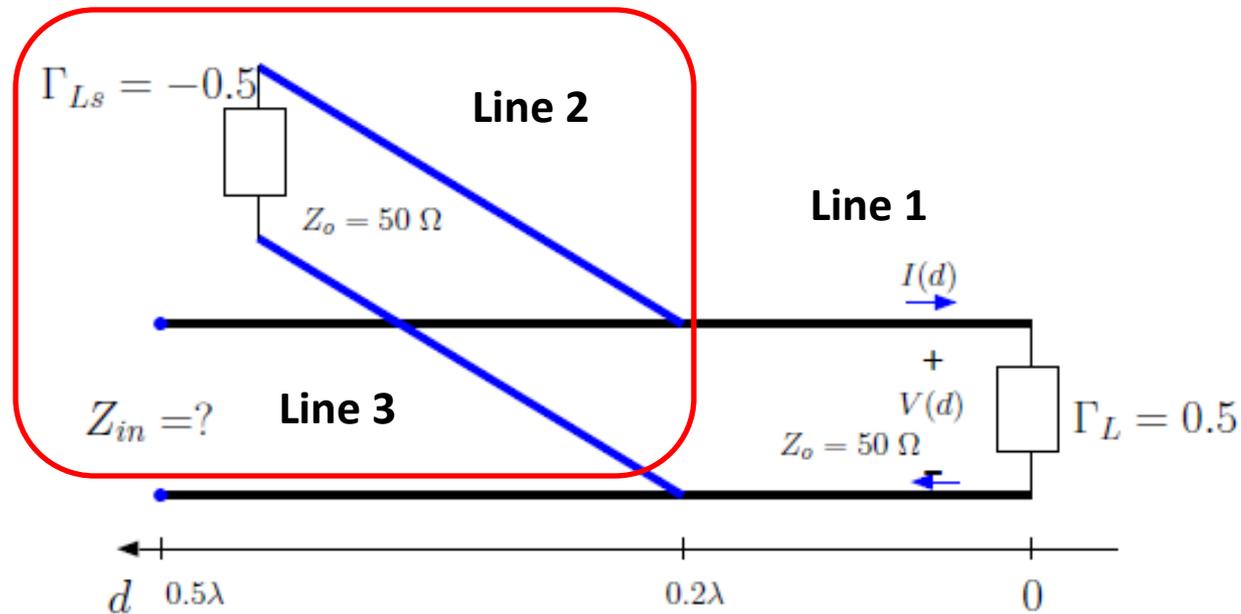Example 4: A TL of length $l = 0.5\lambda$ and $Z_o = 50 \Omega$ has a load reflection coefficient $\Gamma_L = 0.5$ and a shunt connected TL at $d = 0.2\lambda$. The shunt connected TL has $l = 0.3\lambda$, $Z_o = 50 \Omega$, and a load reflection coefficient $\Gamma_L = -0.5$. Determine the input impedance of the line.



d = λ

Module 2.6 Interactive Smith Chart

Instructions

Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 3.0
- Voltage Maximum
d(max) = 0.25 λ
- Voltage Minimum
d(min) = 0.5 λ

Show Γ Load Cursor

- $z_L = 0.333333 + j0.0$
 $\Gamma_L = 0.5 \angle 180.0^\circ$
- $z(d) = 0.333333 + j0.0$
 $\Gamma_d = 0.5 \angle 180.0^\circ$
- $y(d) = 3.0 + j0.0$

- ⤿ $d = 0.0 \lambda$
 $2\beta d = 0.0 \text{ rad} = 0.0^\circ$
- ⤿ $0.5\lambda - d = 0.5\lambda$
 $2\beta(0.5\lambda - d) = 6.2832 \text{ rad} = 360.0^\circ$

Set Line
 $Z_0 =$ $[\Omega]$

Set Load
 $\Gamma_L =$

 Z Y Γ

enter


select

Click and drag mouse
to reposition load

Show Plots

d = λ

Module 2.6
Interactive Smith Chart

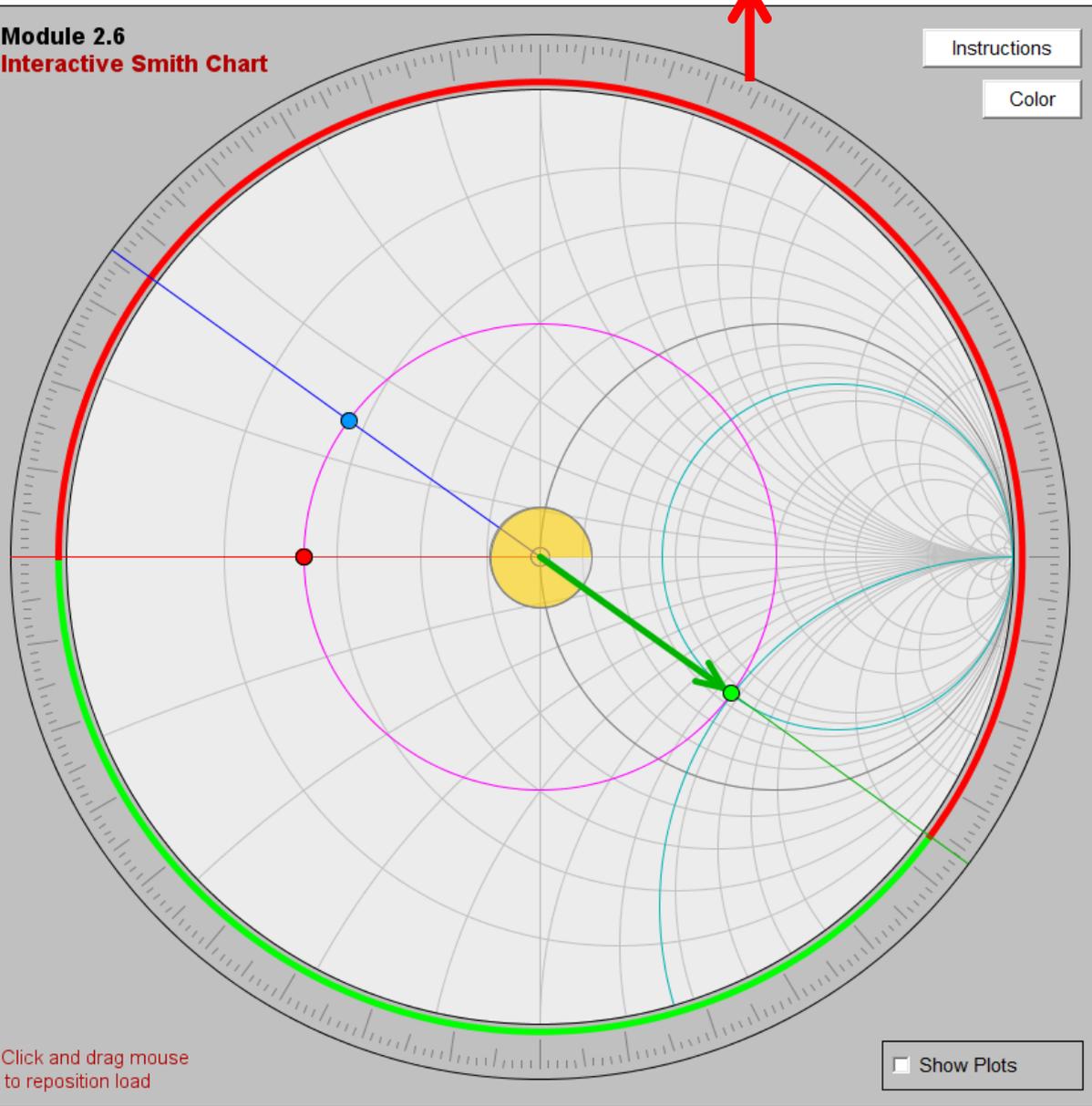

Instructions
Color

- SWR Circle
- Show Curves
- Full Chart
- Cursor Lines
- $y(d)$

- Tangent SWR Circle
 $SWR = 3.0$
- Voltage Maximum
 $d(max) = 0.25 \lambda$
- Voltage Minimum
 $d(min) = 0.5 \lambda$
- Show Γ
- Load
- Cursor

- $z_L = 0.333333 + j0.0$
 $\Gamma_L = 0.5 \angle 180.0^\circ$
- $z(d) = 1.700746 - j1.332898$
- $y(d) = 0.364251 + j0.285469$

- ⤿ $d = 0.3 \lambda$
 $2\beta d = 3.769911 \text{ rad} = 216.0^\circ$
- ⤿ $0.5\lambda - d = 0.2\lambda$
 $2\beta(0.5\lambda - d) = 2.5133 \text{ rad} = 144.0^\circ$


Set Line
 $Z_0 =$ $[\Omega]$

Set Load
 $\Gamma_L =$
 $^\circ$
 Z Y Γ

Click and drag mouse to reposition load

Show Plots

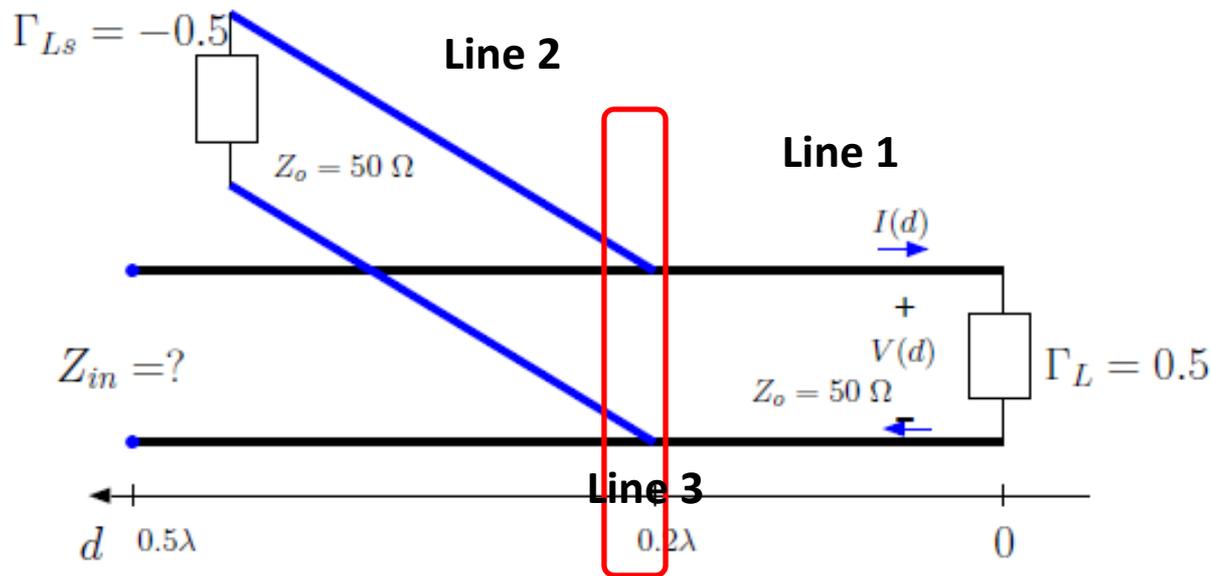Example 4: A TL of length $l = 0.5\lambda$ and $Z_o = 50 \Omega$ has a load reflection coefficient $\Gamma_L = 0.5$ and a shunt connected TL at $d = 0.2\lambda$. The shunt connected TL has $l = 0.3\lambda$, $Z_o = 50 \Omega$, and a load reflection coefficient $\Gamma_L = -0.5$. Determine the input impedance of the line.



input admittance Line 1

$$y(d) = 1.700746 + j 1.332898$$

input admittance Line 2

$$y(d) = 0.364251 + j 0.285469$$

parallel of Line 1 and Line 2 input admittances is simply the sum

$$y_c = y(0.2\lambda) + y_s(0.3\lambda) \approx (1.7 + j1.33) + (0.36 + j0.29) = 2.065 + j1.61837$$


(actual admittance is obtained dividing by $Z_o = 50 \Omega$ or multiplying by $Y_o = 1/50 \text{ S}$)

d = λ

Module 2.6 Interactive Smith Chart





Instructions

Color

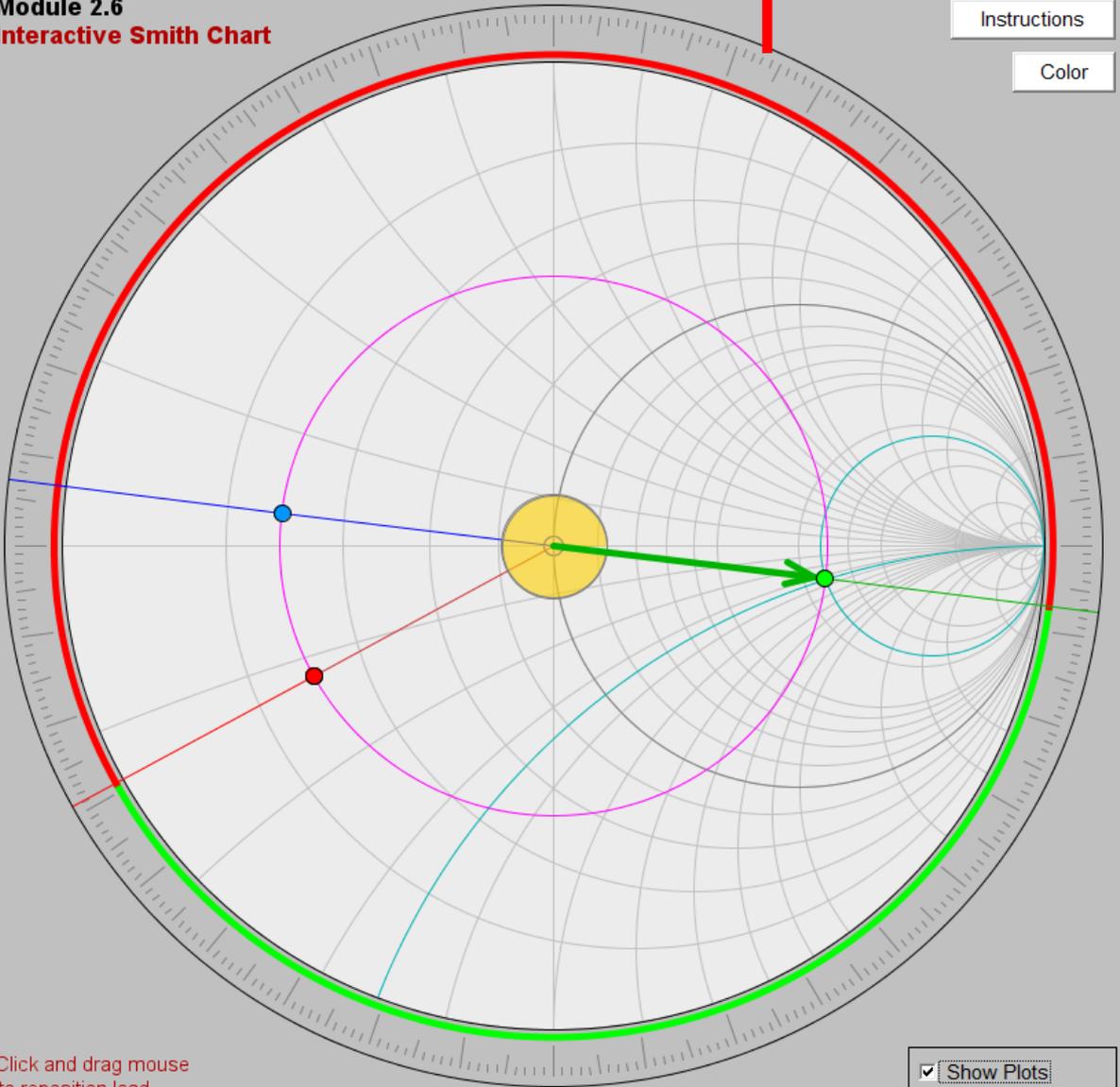

Click and drag mouse
to reposition load

Show Plots

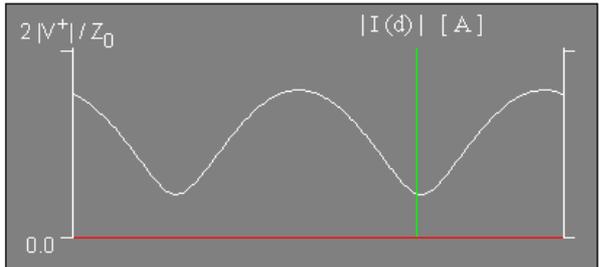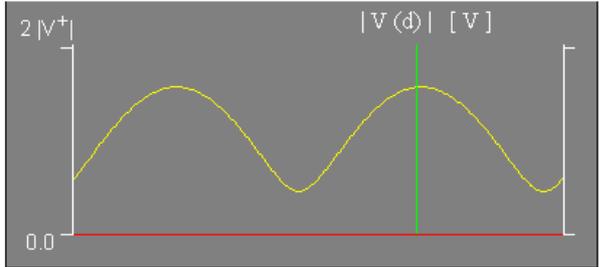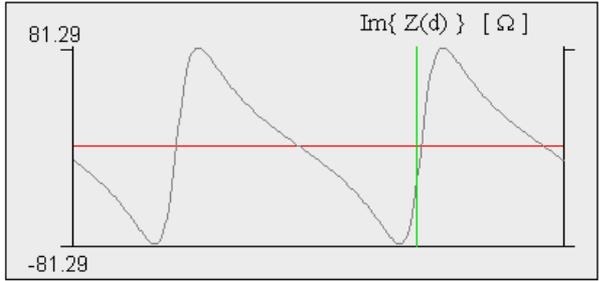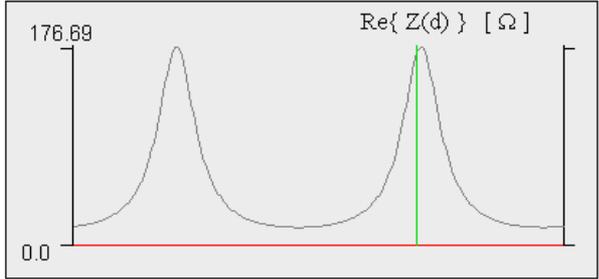

d λ 0

$Z(d) = 169.108275 - j 34.377158 \Omega$
 $d = 0.3 \lambda$

Example 5: What is the load impedance Z_{L_s} terminating the shunt connected stub in Example 4?

Solution: Given that the corresponding reflection coefficient is


$$\Gamma_{L_s} = -0.5,$$

it follows from the bilinear transformation linking z_{L_s} and Γ_{L_s} that

$$z_{L_s} = \frac{1 + \Gamma_{L_s}}{1 - \Gamma_{L_s}} = \frac{1 - 0.5}{1 + 0.5} = \frac{1}{3}.$$

Hence, the impedance is
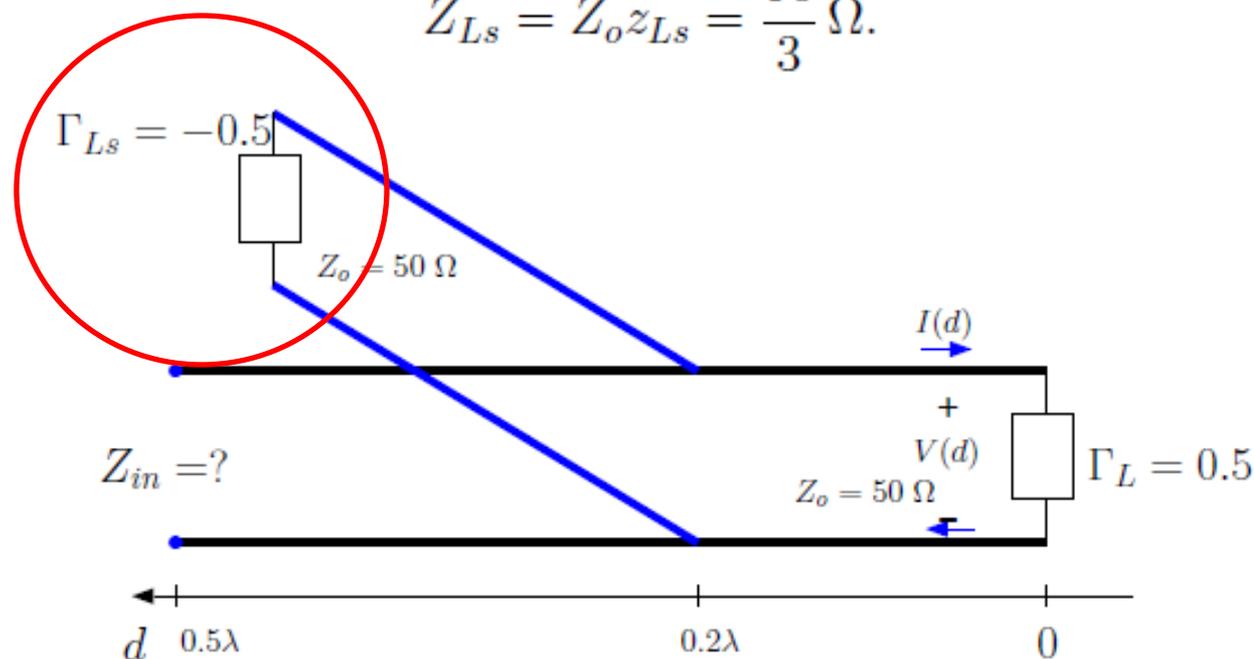
$$Z_{L_s} = Z_o z_{L_s} = \frac{50}{3} \Omega.$$



d = λ

Module 2.6
Interactive Smith Chart

Instructions

Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 3.0
- Voltage Maximum
d(max) = 0.25 λ
- Voltage Minimum
d(min) = 0.5 λ

- Show Γ
- Load
- Cursor

$z_L = 0.333333 + j0.0$
 $\Gamma_L = 0.5 \angle 180.0^\circ$

$z(d) = 0.333333 + j0.0$

$\Gamma_d = 0.5 \angle 180.0^\circ$

$y(d) = 3.0 + j0.0$

$d = 0.0 \lambda$
 $2\beta d = 0.0 \text{ rad} = 0.0^\circ$

$0.5\lambda - d = 0.5\lambda$
 $2\beta(0.5\lambda - d) = 6.2832 \text{ rad} = 360.0^\circ$

Set Line

Update

$Z_0 = 50.0 [\Omega]$

Set Load

Update

$\Gamma_L = 0.5$

$\angle 180$

- Z
- Y
- Γ

$Z(d) = 16.666667 + j0.0 \Omega$
 $d = 0.0 \lambda$

enter

Show Plots

Click and drag mouse
to reposition load

select

Example 6: What is the load impedance Z_L in Example 4?

Solution: This is similar to Example 5. Given that the load reflection coefficient is


$$\Gamma_L = 0.5,$$

it follows from the bilinear transformation linking z_L and Γ_L that

$$z_L = \frac{1 + \Gamma_L}{1 - \Gamma_L} = \frac{1 + 0.5}{1 - 0.5} = 3.$$

Hence, the impedance is

$$Z_L = Z_o z_L = 150 \Omega.$$

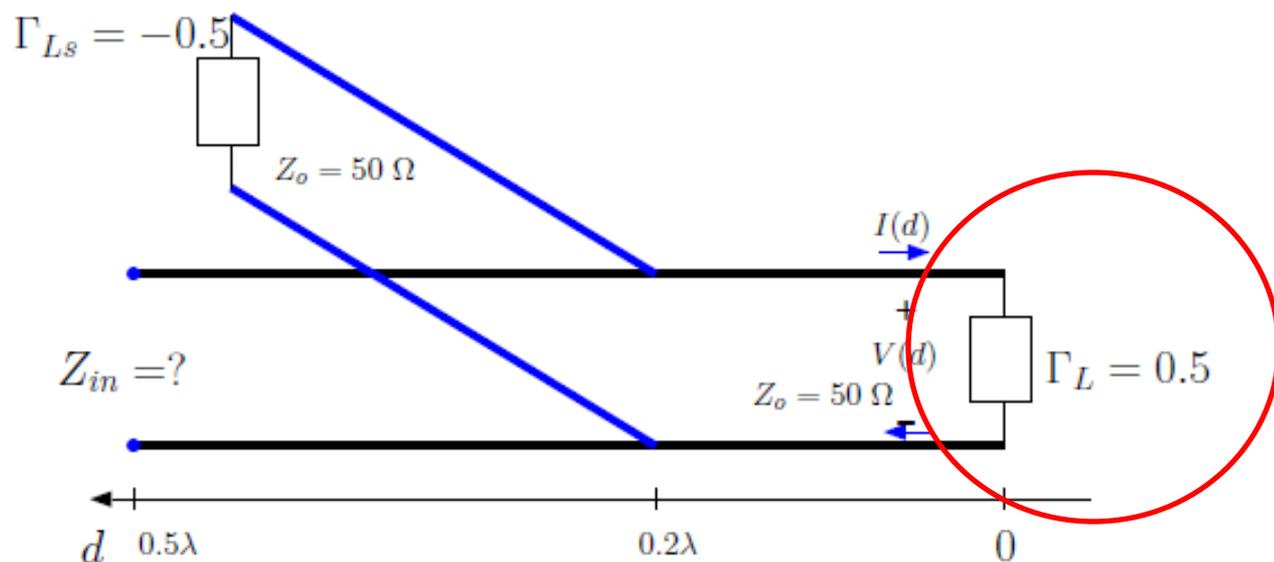

d = λ

Module 2.6 Interactive Smith Chart

Instructions

Color

- SWR Circle
- Cursor Lines
- Show Curves
- y (d)
- Full Chart

- Tangent SWR Circle
SWR = 3.0
- Voltage Maximum
d(max) = 0.5 λ
- Voltage Minimum
d(min) = 0.25 λ
- Show Γ Load Cursor

● $z_L = 3.0 + j0.0$
 $\Gamma_L = 0.5 \angle 0.0^\circ$

● $z(d) = 3.0 + j0.0$
 $\Gamma_d = 0.5 \angle 0.0^\circ$

● $y(d) = 0.333333 + j0.0$

⤿ $d = 0.0 \lambda$
 $2 \beta d = 0.0 \text{ rad} = 0.0^\circ$

⤿ $0.5\lambda - d = 0.5\lambda$
 $2 \beta (0.5\lambda - d) = 6.2832 \text{ rad} = 360.0^\circ$

Set Line
 $Z_0 =$ $[\Omega]$

Set Load
 $\Gamma_L =$

 \angle $^\circ$

 Z Y Γ

$Z(d) = 150.0 + j0.0 \Omega$
 $d = 0.0 \lambda$

enter

select

Click and drag mouse to reposition load

Show Plots